

Seat No.: _____
No. _____

Enrolment

GUJARAT TECHNOLOGICAL UNIVERSITY

Diploma Engineering - SEMESTER-III • EXAMINATION – SUMMER • 2014

Subject Code: 331103

Date: 19-06-2014

Subject Name: Electronics Network and Lines

Time: 10:30 am - 01:00 pm

Total Marks: 70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is Authentic.

- Q.1** (a) Compare active and passive filters. **07**
(b) Derive equation of anti-resonant frequency of parallel resonant circuit. **07**
- Q.2** (a) Write short note on symmetrical π -type attenuator. **07**
(b) Define Quality Factor. Derive the equations of it for an inductor & a capacitor. **07**
OR
(b) Derive equations to convert T-type network into π -type network. **07**
- Q.3** (a) Define following terms for Transmission line : (i) V.S.W.R. (ii) Reflection coefficient **07**
Establish relationship between V.S.W.R. and Reflection coefficient
(b) Explain Kirchoff's current & voltage laws with examples. **07**
OR
- Q.3** (a) State and prove Norton's theorem. **07**
(b) Derive general equation for voltage and current of a transmission line. **07**
- Q.4** (a) Derive the equation of characteristic impedance for symmetrical T-network. **07**
(b) What are the advantages of m-derived filters? Draw m-derived T and π sections for high pass filters. **07**
OR
- Q. 4** (a) Design symmetrical T-type Attenuator having attenuation of 60 dB and load impedance of 600 Ω . **07**
(b) Obtain equations for designing a constant-K type low pass filters. **07**
- Q.5** (a) Explain mutual inductance & derive the equation for coefficient of coupling. **07**
(b) Write a short note on – Phase Equalizer. **07**
OR
- Q.5** (a) State and prove Thevenin's Theorem. **07**
(b) Explain loading of telephone cable. **07**

ગુજરાતી

- પ્રશ્ન. ૧ અ એક્ટીવ અને પેસીવ ફિલ્ટરની સરખામણી કરો. ૦૭
બ પેરેલલ રેઝોનન્સ સર્કીટ માટે એન્ટી રેઝોનન્સ ફ્રીક્વન્સીનું સમીકરણ તારવો. ૦૭
- પ્રશ્ન. ૨ અ સિમેટ્રીકલ પાઇ-ટાઇપ એટેન્યુએટર વિશે ટૂંકનોંધ લખો. ૦૭
બ ક્વોલિટી ફેક્ટરની વ્યાખ્યા લખો. ઇન્ડક્ટર અને કેપેસિટર માટે તેના સમીકરણ તારવો. ૦૭

અથવા

- બ ટી-ટાઇપ નેટવર્કને પાઇ-ટાઇપ નેટવર્કમાં ફેરવવા માટેના સૂત્રો મેળવો. ૦૭
- પ્રશ્ન. ૩ અ ટ્રાન્સમીશન લાઇન માટે નીચેના પદો વ્યાખ્યાયિત કરો.: (૧)વી.એસ.ડબ્લ્યુ.આર. ૦૭
(૨)રીફ્લેક્શન કોએફિશીયન્ટ. વી.એસ.ડબ્લ્યુ.આર. અને રીફ્લેક્શન કોએફિશીયન્ટ વચ્ચેનો સંબંધ તારવો. ૦૭
બ કિર્યોફના વોલ્ટેજ અને કરન્ટ લો ઉદાહરણ સાથે સમજાવો. ૦૭

અથવા

- પ્રશ્ન. ૩ અ નોર્ટોન થિયેરમ લખો અને સાબિત કરો. ૦૭
બ ટ્રાન્સમીશન લાઇન માટે વોલ્ટેજ અને કરન્ટના સમીકરણ તારવો. ૦૭
- પ્રશ્ન. ૪ અ સિમેટ્રીકલ ટી-ટાઇપ નેટવર્ક માટે તેના કેરેક્ટરીસ્ટીક ઇમ્પીડન્સનું સમીકરણ તારવો. ૦૭
બ એમ-ડીરાઇવ્ડ ફીલ્ટરના ફાયદા શું છે? હાઇપાસ ફીલ્ટર માટે એમ-ડીરાઇવ્ડ ટી તથા પાઇ સેક્શન દોરો. ૦૭

અથવા

- પ્રશ્ન. ૪ અ ૬૦ ડેસીબલ એટેન્યુએશન તથા ૬૦૦ ઓહમ લોડ ઇમ્પીડન્સ હોય તેવા સિમેટ્રીકલ ટી-ટાઇપ એટેન્યુએટરની ડીઝાઇન કરો. ૦૭
બ કોન્સ્ટન્ટ-કે ટાઇપ લો પાસ ફીલ્ટરના ડીઝાઇન સમીકરણ તારવો. ૦૭
- પ્રશ્ન. ૫ અ મ્યુચ્યુઅલ ઇન્ડક્ટન્સ સમજાવો. કોએફિસીયન્ટ ઓફ કપલીંગનું સમીકરણ તારવો. ૦૭
બ ફેઝ ઇક્વલાઇઝર વિશે ટૂંકનોંધ લખો. ૦૭

અથવા

- પ્રશ્ન. ૫ અ થેવેનીન થિયેરમનું સ્ટેટમેન્ટ લખો અને સાબિત કરો. ૦૭
બ ટેલિફોન કેબલ લોડીંગ વિશે સમજાવો. ૦૭
