

GUJARAT TECHNOLOGICAL UNIVERSITY**Diploma Engineering - SEMESTER-II • EXAMINATION – SUMMER • 2014****Subject Code: 3321102****Date: 18-06-2014****Subject Name: Electronic Networks****Time: 10:30 am - 01:00 pm****Total Marks: 70****Instructions:**

1. Attempt any five questions.
2. Make Suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Use of programmable & Communication aids are strictly prohibited.
5. Use of only simple calculator is permitted in Mathematics.
6. English version is authentic.

- Q.1** Answer any seven out of ten. **14**
1. Write statement of Super position Theorem.
 2. Define Bandwidth.
 3. Define the Reciprocity Theorem.
 4. Define Driving point Impedance.
 5. Define Decibel and Neper
 6. Give limitation of constant K- type filter.
 7. Define quality factor Q.
 8. Define Mutual inductance.
 9. Define Characteristic Impedance.
 10. Define Self inductance.
- Q.2** (a) Describe Mesh analysis **03**
- OR
- (a) Describe Nodal analysis. **03**
- (b) Explain Kirchhoff's current law (KCL). **03**
- OR
- (b) Explain Kirchhoff's voltage law (KVL) **03**
- (c) Explain Thevenin's Theorem **04**
- OR
- (c) Explain Norton Theorem **04**
- (d) Discuss principal of duality **04**
- OR
- (d) Explain how to convert T network in to equivalent π Network **04**
- Q.3** (a) Find the resonance frequency of Parallel resonance circuit with Resistance of 10Ω , an inductor 100 mH and capacitor of $60\mu\text{F}$ **03**
- OR
- (a) Find the resonance frequency of Series resonance circuit with Resistance of 50Ω , an inductor 100 mH and capacitor of $80\mu\text{F}$. **03**
- (b) Write Short Note On Phase Equalizer. **03**
- OR
- (b) Describe symmetrical and asymmetrical Network. **03**
- (c) Design a Constant-k type low pass filter with T section, having cut-off frequency of 2 kHz and Characteristic Impedance of 400Ω **04**
- OR
- (c) Obtain the equation of cut-off frequency for Constant-k type T & π **04**

sections— Low Pass filter.

- (d) Give differences between single tuned air core transformer and double tuned air core transformer. **04**
- .OR
- (d) Explain maximum power transfer theorem. **04**
- Q.4** (a) Explain Series equalizer **03**
- OR
- (a) Explain Shunt equalizer. **03**
- (b) Design symmetrical π attenuator with a load of 100Ω and attenuation of 40dB. **04**
- OR
- (b) Design symmetrical T attenuator with a load of 400Ω and attenuation of 20dB. **04**
- (c) Explain classification of attenuators based on the circuit configuration. **07**
- Q.5** (a) Classify the various passive filter circuits. **04**
- (b) Find the condition for maximum power transfer. **03**
- (c) Explain various term used for Network Topology. **07**

ગુજરાતી

- પ્રશ્ન. ૧** દશમાંથી કોઇપણ સાતના જવાબ આપો. **૧૪**
૧. સુપર પોસીસન થીયરમ નું સ્ટેટમેન્ટ લખો
 ૨. બેન્ડ વીડ્થ ને વ્યાખ્યાયિત કરો
 ૩. રેસીપ્રોસીટી થીયરમ ને વ્યાખ્યાયિત કરો
 ૪. ડ્રાઇવીંગ પોઇન્ટ ઇંપીડન્સ ને વ્યાખ્યાયિત કરો
 ૫. ડેસીબલ અને નેપીયર ને વ્યાખ્યાયિત કરો
 ૬. કોન્સ્ટન્ટ -k ટાઇપ ના ફીલ્ટર ના લેમીટેસન આપો
 ૭. ક્વોલીટી ફેક્ટર ને વ્યાખ્યાયિત કરો
 ૮. મ્યુચલ ઇન્ડક્ટન્સ ને વ્યાખ્યાયિત કરો
 ૯. કેરેક્ટરીસ્ટીક ઇંપીડન્સ ને વ્યાખ્યાયિત કરો
 - ૧૦ સેલ્ફ ઇન્ડક્ટન્સ ને વ્યાખ્યાયિત કરો
- પ્રશ્ન. ૨** અ મેશ એનાલીસીસ વર્ણવો **૦૩**
- અથવા
- અ નોડ એનાલીસીસ વર્ણવો **૦૩**
- બ કીરોફ્ફ નો કરંટ નો નીયમ સમજાવો (KCL). **૦૩**
- અથવા
- બ કીરોફ્ફ નો વોલ્ટેજ નો નીયમ સમજાવો(KVL). **૦૩**
- ક થેવેનીયન થીયરમ સમજાવો **૦૪**

અથવા

	ક	નોર્ટન થીયરમ સમજાવો	0૪
	ડ	ડૂયાલીટી પ્રિન્સિપલ ની ચર્ચા કરો	0૪
		અથવા	
	ડ	T પ્રકાર ના નેટવર્ક નું π પ્રકાર ના નેટવર્ક માં રૂપાંતર કેવી રીતે થાય તે સમજાવો	0૪
પ્રશ્ન. ૩	અ	રેસીસ્ટન્સ 10Ω , ઈન્ડક્ટન્સ 100 mH અને કેપેસીટર $60\mu\text{F}$ ના પેરેલલ પ્રકાર ની રેસોનન્સ સર્કિટ માટે રેસોનન્સ ફ્રીક્વન્સી શોધો	0૩
		અથવા	
	અ	રેસીસ્ટન્સ 50Ω , ઈન્ડક્ટન્સ 100 mH અને કેપેસીટર $80\mu\text{F}$ ના સીરીઝ પ્રકાર ની રેસોનન્સ સર્કિટ માટે રેસોનન્સ ફ્રીક્વન્સી શોધો	0૩
	બ	ફેઝ ઈકવીલાઇઝર વીશે ટુકનોંધ લખો	0૩
		અથવા	
	બ	સીમેટ્રીકલ અને એસીમેટ્રીકલ નેટવર્ક વર્ણવો.	0૩
	ક	કટ ઓફ ફ્રીક્વન્સી 2 kHz અને કેરેક્ટરીસ્ટીક ઇમ્પીડન્સ 400Ω માટે કોન્સ્ટન્ટ $-k$ ટાઈપ ના લો પાસ ફીલ્ટર T સેકસન માટે ડીઝાઇન કરો	0૪
		અથવા	
	ક	કોન્સ્ટન્ટ $-k$ ટાઈપ ના લો પાસ ફીલ્ટર T અને π સેકસન માટે કટ ઓફ ફ્રીક્વન્સી નું સૂત્ર મેળવો	0૪
	ડ	સીન્ગલ ટ્યુન્ડ અને ડબલ ટ્યુન્ડ એર કોર ટ્રાન્સફોર્મર ના તફાવતો આપો.	0૪
		અથવા	
	ડ	મેક્સીમમ પાવર ટ્રાન્સફર થીયરમ સમજાવો	0૪
પ્રશ્ન. ૪	અ	સીરીઝ ઈકવીલાઇઝર સમજાવો	0૩
		અથવા	
	અ	શન્ટ ઈકવીલાઇઝર સમજાવો	0૩
	બ	લોડ 100Ω અને અટેન્યુએસન 40Db માટે સીમેટ્રીકલ π અટેન્યુએટર ની ડીઝાઇન કરો	0૪
		અથવા	
	બ	લોડ 400Ω અને અટેન્યુએસન 20Db માટે સીમેટ્રીકલ T અટેન્યુએટર ની ડીઝાઇન કરો	0૪
	ક	સર્કિટ કન્ફીગરેસન ના આધારે અટેન્યુએટર નું વર્ગીકરણ સમજાવો	0૭
પ્રશ્ન. ૫	અ	જુદા જુદા પેસીવ ફીલ્ટર ને વર્ગીકૃત કરો	0૩
	બ	મેક્સીમમ પાવર ટ્રાન્સફર માટે ની શરત શોધો.	0૪
	ક	નેટવર્ક ટોપોલોજી માટે વપરાતી જુદી જુદી ટર્મ સમજાવો	0૭
