

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY

Diploma Engineering - SEMESTER-IV • EXAMINATION – SUMMER • 2014

Subject Code: 341103

Date: 29-05-2014

Subject Name: Industrial Electronics

Time: 10:30 am - 01:00 pm

Total Marks: 70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is considered to be Authentic.

- Q.1** (a) Explain the construction, working and characteristic of TRIAC. **07**
(b) Explain Light Operated photo Relay using LDR. **07**
- Q.2** (a) Draw and explain block diagram of PLC. **07**
(b) Explain construction and working of stepper motor with diagram. **07**
- OR
- (b) Explain construction and working of Synchro transmitter. **07**
- Q.3** (a) Describe Forced Commutation technics for SCR. **07**
(b) Explain circuit of UJT Relaxation oscillator with waveforms. State component selection criteria for desired frequency setting. **07**
- OR
- Q.3** (a) State principle of Inverter . Explain single phase Series Inverter with necessary circuit diagram and waveforms. **07**
(b) Compare Open loop and Closed loop control system. **07**
- Q.4** (a) Draw and explain the working of three phase full wave rectifier circuit. **07**
(b) Define Induction Heating. Explain it's applications. **07**
- OR
- Q. 4** (a) Explain principle of Di-electric heating. List out the points to be considered in selection of frequency and voltage. **07**
(b) Explain types of Resistance Welding. **07**
- Q.5** (a) Define cycloconverter. Explain single phase center tapped step up cycloconverter. **07**
(b) Explain block diagram of 'ECG machine'. **07**
- OR
- Q.5** (a) Explain with circuit diagram the electronic speed control of DC Motor. **07**
(b) Explain construction, working and application of endoscope. **07**

ગુજરાતી

- પ્રશ્ન. ૧ અ ટ્રાયેક ની રચના, કાર્ય અને લાક્ષણિકતા સમજાવો. ૦૭
બ એલ ડી આર. ના ઉપયોગથી લાઇટ ઓપરેટેડ ફોટો રિલે સમજાવો. ૦૭

- પ્રશ્ન. ૨ અ પી એલ સી. ખંડીય આકૃતિ દોરો અને સમજાવો. ૦૭
બ સ્ટેપર મોટર ની રચના અને કાર્યપદ્ધતિ આકૃતિ દોરી ને સમજાવો. ૦૭

અથવા

- બ સિંક્રો ટ્રાંસમિટર ની રચના અને કાર્યપદ્ધતિ આકૃતિ દોરી ને સમજાવો. ૦૭
- પ્રશ્ન. ૩ અ એસ સી આર માટે ફોર્સડ કોમ્યુટેસન પદ્ધતિઓ વર્ણવો. ૦૭
બ યુ જે ટી રિલેક્શન ઓસ્સિલેટરની સર્કિટ તરંગો દોરી સમજાવો. જરૂરી ફિક્વેન્સી મેળવવા માટે સર્કિટમાં કઇ રીતે કમ્પોનન્ટની કિંમત નક્કી કરવી તે જણાવો. ૦૭

અથવા

- પ્રશ્ન. ૩ અ ઇંવર્ટર્ નો સિદ્ધાંત લખો. સિંગલ ફેઝ સિરીઝ ઇંવર્ટર્ આકૃતિ દોરીને સમજાવો. ૦૭
બ ઓપન લૂપ અને ક્લોસ્ડ લૂપ કંટ્રોલ સિસ્ટમ સરખાવો. ૦૭
- પ્રશ્ન. ૪ અ સ્વચ્છ આકૃતિ અને તરંગો દોરી ૩ ફેઝ પુર્ણ તરંગ રેક્ટિફાયર સમજાવો. ૦૭
બ ઇંડક્શન હિટીંગ વ્યાખ્યાયિત કરી તેના ઉપયોગો વર્ણવો. ૦૭

અથવા

- પ્રશ્ન. ૪ અ ડાઇ ઇલેક્ટ્રિક હિટીંગ નો સિદ્ધાંત સમજાવો. અને જરૂરી ફિક્વેન્સી અને વોલ્ટેજ મેળવવા માટે ધ્યાને લેવા પડતા મુદ્દાઓ લખો. ૦૭
બ રેસિસ્ટન્સ વેલ્ડિંગ ના પ્રકારો સમજાવો. ૦૭
- પ્રશ્ન. ૫ અ સાયક્લોકંવર્ટર વ્યાખ્યાયિત કરી સિંગલ ફેઝ સેન્ટર ટેપ્ડ સ્ટેપ- અપ સાયક્લોકંવર્ટર સમજાવો. ૦૭
બ ઇ સી જી મશીન ખંડીય આકૃતિ દોરી ને સમજાવો. ૦૭

અથવા

- પ્રશ્ન. ૫ અ ડી સી મોટર નું સ્પીડ નિયંત્રણ ઇલેક્ટ્રોનિક કંટ્રોલ સર્કિટ દોરી ને સમજાવો. ૦૭
બ એંડોસ્કોપ ની રચના, કાર્ય પદ્ધતિ અને ઉપયોગો સમજાવો. ૦૭
