

GUJARAT TECHNOLOGICAL UNIVERSITY**Diploma Engineering - SEMESTER-IV • EXAMINATION – SUMMER • 2014****Subject Code: 342402****Date: 31-05-2014****Subject Name: Electrical Network and Circuits****Time: 10:30 am - 01:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is considered to be Authentic.

- Q.1** (a) Give the comparison between voltage source and current source. **07**
(b) Explain mesh analysis. **07**
- Q.2** (a) Discuss types of impedance in detail and connect them in delta connection. **07**
(b) What is the difference between passive and active element? Discuss active element in detail. **07**
- OR
- (b) Explain node analysis. **07**
- Q.3** (a) Discuss in detail about self induction, mutual induction and coupled circuit. **07**
(b) Draw appropriate circuit for DC source with R-C Load and discuss transient. **07**
- OR
- Q.3** (a) Draw appropriate circuit for DC source with R-L Load and discuss transient. **07**
(b) Discuss initial conditions in Resistor, Inductor and Capacitor with waveform and equations. **07**
- Q.4** (a) Discuss KVL along with proper circuit diagram. **07**
(b) Discuss KCL along with proper circuit diagram. **07**
- OR
- Q. 4** (a) Explain two port networks in detail. **07**
(b) Discuss Y-parameter in detail **07**
- Q.5** (a) Write short note on Superposition theorem. **07**
(b) Write short note on Parallel Resonance. **07**
- OR
- Q.5** (a) Write short note on Norton's theorem. **07**
(b) Write short note on Series resonance. **07**

ગુજરાતી

- પ્રશ્ન. ૧ અ વોલ્ટેજ સોર્સ અને કરંટ સોર્સ ની કમ્પેરીજન કરો. ૦૭
બ મેશ એનાલીસીસ નુ વર્ણન કરો. ૦૭

- પ્રશ્ન. ૨ અ ઇમ્પીડંસ ના ટાઇપ્સ ને વિગત મા ચર્ચા કરો અને તેને ડેલ્ટા મા કનેક્ટ કરો. ૦૭
બ પેસીવ અને એક્ટીવ ઇલીમેંટ નો તફાવત શુ છે? એક્ટીવ એલીમેંટ ને ડીટેલ મા ચર્ચા કરો. ૦૭

અથવા

- બ નોડ એનાલીસીસ નુ વર્ણન કરો. ૦૭
- પ્રશ્ન. ૩ અ Self induction, mutual induction અને coupled circuit ની વીગત મા ચર્ચા કરો. ૦૭
બ યોગ્ય સર્કીટ સાથે DC સોર્સ ની R-C Load ટ્રાન્સીયંટ માટે ચર્ચા કરો ૦૭

અથવા

- પ્રશ્ન. ૩ અ યોગ્ય સર્કીટ સાથે DC સોર્સ ની R-L Load ટ્રાન્સીયંટ માટે ચર્ચા કરો ૦૭
બ Resistor, Inductor અને capacitor ને વેવફોર્મ અને સુત્રો સાથે initial condition માટે ચર્ચા કરો. ૦૭

- પ્રશ્ન. ૪ અ KVL ને યોગ્ય સર્કીટ સાથે ચર્ચા કરો. ૦૭
બ KCL ને યોગ્ય સર્કીટ સાથે ચર્ચા કરો ૦૭

અથવા

- પ્રશ્ન. ૪ અ 2-પોર્ટ નેટવર્ક નુ વિગત મા વર્ણન કરો. ૦૭
બ Y-પેરામીટર ની વીગત મા ચર્ચા કરો. ૦૭

- પ્રશ્ન. ૫ અ Superposition theorem પર ટુકનોધ લખો. ૦૭
બ Parallel resonance પર ટુકનોધ લખો. ૦૭

અથવા

- પ્રશ્ન. ૫ અ Norton's theorem પર ટુકનોધ લખો. ૦૭
બ Series resonance પર ટુકનોધ લખો. ૦૭
