

GUJARAT TECHNOLOGICAL UNIVERSITY
DIPLOMA ENGINEERING – SEMESTER – V • EXAMINATION – SUMMER • 2014

Subject Code: 352402**Date: 27-05-2014****Subject Name: Applied Power Electronics****02:30 pm - 05:00 pm****Total Marks: 70****Instructions:**

1. Attempt any five questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Each question carry equal marks (14 marks)

- Q.1** (a) Discuss time delay relay using SCR and UJT. **07**
(b) Explain Battery along with classification and technological development. **07**
- Q.2** (a) Explain VCO (voltage controlled oscillator). **07**
(b) Explain A/D converter. **07**
- Or**
- (b) Explain D/A converter. **07**
- Q.3** (a) List types of resistance welding and explain spot welding. **07**
(b) Explain capacitor type charging storage welding. **07**
- Or**
- Q.3** (a) Discuss 1-phase DC Welder circuit. **07**
(b) Explain inductor type energy storage welding. **07**
- Q.4** (a) Explain induction heating with advantages and disadvantages. **07**
(b) Explain piezo-electric crystal generator. **07**
- Or**
- Q. 4** (a) Explain dielectric heating with applications, advantages and disadvantages. **07**
(b) Explain ultrasonic welding. **07**
- Q.5** (a) Write short note on LASCR. **07**
(b) Write short note on Photo Transistor. **07**
- Or**
- (a) Write short note on Photo Voltic cell. **07**
(b) Write short note on LDR. **07**

પ્રશ્ન-૧	અ	SCR and UJT ને ટાઇમ ડીલે રીલે માટે ચર્ચા કરો.	૦૭
	બ	Classification (વર્ગીકરણ) અને ટેકનોલોજીકલ વિકાસ સાથે બેટરી નું વર્ણન કરો.	૦૭
પ્રશ્ન-૨	અ	VCO (voltage controlled oscillator) નું વર્ણન કરો.	૦૭
	બ	A/D converter નું વર્ણન કરો.	૦૭
	અથવા		
	બ	D/A converter નું વર્ણન કરો.	૦૭
પ્રશ્ન-૩	અ	રેજીસ્ટર વેલ્ડીંગ ના ટાઇપ્સ નું લીસ્ટ બનાવો અને સ્પોટ વેલ્ડીંગ નું વર્ણન કરો.	૦૭
	બ	કેપેસિટર ટાઇપ ચાર્જીંગ સ્ટોરેજ વેલ્ડીંગ નું વર્ણન કરો.	૦૭
	અથવા		
પ્રશ્ન-૩	અ	1-ફેઝ ડીસી વેલ્ડર સર્કીટ ની ચર્ચા કરો	૦૭
	બ	Inductor ટાઇપ એનર્જી સ્ટોરેજ વેલ્ડીંગ નું વર્ણન કરો.	૦૭
પ્રશ્ન-૪	અ	ઇંડક્શન હીટીંગ નું ફાયદા અને ગેરફાયદા સાથે વર્ણન કરો.	૦૭
	બ	પીજો ઇલેક્ટ્રિક ક્રીસ્ટલ જનરેટર નું વર્ણન કરો.	૦૭
	અથવા		
પ્રશ્ન-૪	અ	ડાય-ઇલેક્ટ્રિક હીટીંગ નું એપ્લિકેશન, ફાયદા અને ગેરફાયદા સાથે વર્ણન કરો.	૦૭
	બ	અલ્ટ્રાસોનીક વેલ્ડીંગ નું વર્ણન કરો.	૦૭
પ્રશ્ન-૫	અ	LASCR પર ટુકનોધ લખો.	૦૭
	બ	Photo Transistor પર ટુકનોધ લખો.	૦૭
	અથવા		
પ્રશ્ન-૫	અ	Photo Voltic cell પર ટુકનોધ લખો.	૦૭
	બ	LDR પર ટુકનોધ લખો.	૦૭
