

GUJARAT TECHNOLOGICAL UNIVERSITY
DIPLOMA ENGINEERING - SEMESTER-VI • EXAMINATION – SUMMER • 2014

Subject Code: 362401**Date: 22-05-2014****Subject Name: Electrical Drives and Control-II****Time: 10:30 am - 01:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is considered to be Authentic.

- Q.1** (a) List equations for Induction motor drive like P_{su} , P_{ru} , P_c , P_g , P_d , T_d , P_i , P_o , η , I_r , T_s , T_m . **07**
- (b) List advantages of electrical drive and draw equivalent circuit of I.M. **07**
- Q.2** (a) Draw three modes of Torque-Speed characteristics of I.M. and explain braking mode. **07**
- (b) Draw basic circuit for constant volts/hertz control of synchronous motor using VSI and explain it in brief. **07**
- OR
- (b) A 3- Φ .460V, 60Hz, 4-pole Y-connected induction motor has following equivalent circuit parameters: $R_s=0.42\Omega$, $R_r=0.23\Omega$, $X_s=X_r=0.82\Omega$, and $X_m=22\Omega$. $Z_i=7.732 \angle -30.8^\circ$, $P_{no-load}=60W$, may be assumed constant. The rotor speed is 1750rpm. Determine (a) the synchronous speed ω_s (b) slip S , (c) input current I_i (d) input power P_i (e) power factor (f) gap power P_g (g) developed torque T_d . **07**
- Q.3** (a) Draw various thyristor circuit configurations of AC voltage controller for 3- Φ induction motor. **07**
- (b) Explain close loop control of induction motor using voltage/hertz control. **07**
- OR
- Q.3** (a) Draw circuit diagram of cycloconverter fed synchronous motor drive. **07**
- (b) Explain stator voltage control method for induction motor. **07**
- Q.4** (a) Discuss conventional slip control method in phase wound I.M. **07**
- (b) Explain cylindrical rotor motors. **07**
- OR
- Q.4** (a) Discuss slip power control method using GTO chopper circuit. **07**
- (b) Give comparison between VSI and CSI. **07**
- Q.5** (a) Discuss frequency control method for induction motor drive. **07**
- (b) Write short note on self controlled synchronous motors. **07**
- OR
- Q.5** (a) Discuss static Kramer drive. **07**
- (b) Write short note on switched reluctance motors. **07**

ગુજરાતી

- પ્રશ્ન. ૧ અ ઇંડક્શન મોટર ના સુત્રો ની યાદી બનાવો જેમકે: $P_{su}, P_{ru}, P_c, P_g, P_d, T_d, P_i, P_o, \eta, I_r, T_s, T_m$. ૦૭
- બ ઇલેક્ટ્રીકલ ડ્રાઇવ ના ફાયદા ની યાદી બનાવો અને ઇંડક્શન મોટર ની ઇક્વીવેલન્ટ સર્કીટ દોરો. ૦૭

- પ્રશ્ન. ૨ અ ઇંડક્શન મોટર માટે ત્રણેય મોડ ની ટોર્ક-સ્પીડ કેરેક્ટરીસ્ટીક દોરો અને બ્રેકીંગ મોડ નુ વર્ણન કરો. ૦૭
- બ સીકોનસ મોટર માટે કોન્સ્ટન્ટ વોલ્ટેજ / ફ્રીક્વેન્સી કંટ્રોલ વાળી VSI ને ઉપયોગ મા લઈ ને સર્કીટ દોરો અને ટુંક મા વર્ણન કરો. ૦૭

અથવા

- બ 3- Φ .460V, 60Hz, 4-pole Y-connected ઇંડક્શન મોટર ની ઇક્વીવેલન્ટ સર્કીટ ના પેરામીટર નીચે મુજબ છે. $R_s=0.42\Omega, R_r=0.23\Omega, X_s=X_r=0.82\Omega$, and $X_m=22\Omega$. $Z_i=7.732 \angle -30.8^\circ$ $P_{no-load}=60W$, કે જે કોન્સ્ટન્ટ ધારો. રોટર ની ઝડપ 1750rpm છે. ઉપર માટે ગણતરી કરો (a) સીકોનસ ઝડપ ω_s (b) સ્લીપ s (c) ઇનપુટ કરન્ટ I_i (d) ઇનપુટ પાવર P_i (e) પાવર ફેક્ટર (f) ગેપ પાવર P_g (g) ડેવલોપડ પાવર T_d . ૦૭
- પ્રશ્ન. ૩ અ ૩-ફેઝ ઇંડક્શન મોટર માટે Thyristor વાળી જુદી-જુદી સર્કીટ ના કંફીગરેશન થી એ.સી વોલ્ટેજ કંટ્રોલર દોરો. ૦૭
- બ ઇંડક્શન મોટર ની વોલ્ટેજ / ફ્રીક્વેન્સી કંટ્રોલ વાળી ક્લોજ -લૂપ સીસ્ટમ દોરો. ૦૭

અથવા

- પ્રશ્ન. ૩ અ સાયક્લો કંવર્ટર થી જોડેલ સીકોનસ મોટર ડ્રાઇવ ની સર્કીટ દોરો. ૦૭
- બ ઇંડક્શન મોટર માટે સ્ટેટર વોલ્ટેજ કંટ્રોલ પદ્ધતી નુ વર્ણન કરો. ૦૭
- પ્રશ્ન. ૪ અ ફેજ-વાઉડ ઇંડક્શન મોટર માટે કંવેશનલ સ્લીપ કંટ્રોલ પદ્ધતી ની ચર્ચા કરો. ૦૭
- બ સીલીન્ડરીકલ રોટર મોટર્સ નુ વર્ણન કરો. ૦૭

અથવા

- પ્રશ્ન. ૪ અ સ્લીપ કંટ્રોલ પદ્ધતી ને GTO ચોપર સર્કીટ ના ઉપયોગ થી ચર્ચા કરો. ૦૭
- બ VSI અને CSI ની સરખામણી કરો. ૦૭
- પ્રશ્ન. ૫ અ ઇંડક્શન મોટર ડ્રાઇવ માટે ફ્રીક્વેન્સી કંટ્રોલ પદ્ધતી ની ચર્ચા કરો. ૦૭
- બ સ્વયમ સંચાલીત સીકોનસ મોટર્સ પર ટુંકનોંધ લખો. ૦૭

અથવા

- પ્રશ્ન. ૫ અ સ્ટેટીક કેમર ડ્રાઇવ ની ચર્ચા કરો. ૦૭
- બ સ્વીચડ રીલક્ટેન્સ મોટર્સ પર ટુંકનોંધ લખો. ૦૭
