

GUJARAT TECHNOLOGICAL UNIVERSITY**Diploma Sem-II examination June 2009****Subject code:320017****Subject Name: Electronic Devices & Circuit-1****Date:30/06/2009****Time: 10:30am-1:00pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- | | | |
|------------|---|-----------|
| Q.1 | (a) Explain working of bridge rectifier with circuit diagram and waveforms. State its applications. | 05 |
| | (b) What is the requirement of filter circuit? Explain π - filter. | 05 |
| | (c) Explain drift current and diffusion current in brief. | 04 |
| Q.2 | (a) Write a detailed note on h-parameters. | 07 |
| | (b) Draw and explain different clipping circuits using diode. | 07 |
| | OR | |
| | (b) What is zener effect? Draw characteristics of zener diode and explain its working as a voltage regulator. | 07 |
| Q.3 | (a) Explain full wave and half wave voltage doublers. | 05 |
| | (b) Describe tunnel diode with its principle, characteristics and applications. | 05 |
| | (c) Define α_{dc} and β_{dc} . Derive relationship between them. | 04 |
| | OR | |
| Q.3 | (a) Draw and explain diode clamping circuits with waveforms. | 05 |
| | (b) Derive expression for ripple factor. Show value of ripple factor for half wave and full wave rectifiers. | 05 |
| | (c) Compare CB, CE and CC amplifiers. | 04 |
| Q.4 | (a) Explain working of CE amplifier and define its voltage gain, current gain and power gain. | 05 |
| | (b) List various methods of biasing a transistor. Explain voltage divider bias. | 05 |
| | (c) State and explain reasons for change in operating point. | 04 |
| | OR | |
| Q.4 | (a) State different methods of cascading amplifiers. Explain RC coupling. | 05 |
| | (b) Explain frequency response of RC coupled amplifier. | 05 |
| | (c) Define stability factor. Derive expression for stability factor of CE amplifier. | 04 |
| Q.5 | (a) Explain shunt voltage regulator using transistor. | 05 |
| | (b) Write a short note on SMPS. | 05 |
| | (c) Draw h-parameter equivalent circuits for CB, CE and CC amplifiers. | 04 |
| | OR | |
| Q.5 | (a) Explain series voltage regulator using transistor. | 05 |
| | (b) What is a Darlington pair? Explain Darlington amplifier. | 05 |
| | (c) Derive h- parameters for CE amplifier. | 04 |

સૂચના:

1. બધાજ પ્રશ્નોના જવાબ આપવા ફરજિયાત છે.
2. જરૂર જણાય ત્યાં યોગ્ય ધારણાઓ કરો.
3. જમણી બાજુ દર્શાવેલા આંકડા પ્રશ્નોના પૂરા ગુણ દર્શાવે છે.

પ્રશ્ન. ૧

- (અ) સર્કીટ ડાયાગ્રામ દોરીને બ્રીજ રેકિટફાયરનું કાર્ય સમજાવો. તેના ફાયદા અને ગેરફાયદા જણાવો. **05**
- (બ) ફીલ્ટરની જરૂર કેમ પડે છે ? π ફીલ્ટર સમજાવો. **05**
- (ક) ડ્રીફ્ટ કરંટ અને ડીફ્યુઝન કરંટ ટૂંકમાં સમજાવો. **04**

પ્રશ્ન. ૨

- (અ) એચ પેરામીટર વિશે વિગતવાર નોંધ લખો. **07**
- (બ) ડાયોડનો ઉપયોગ કરીને જુદી જુદી કલીપીંગ સર્કીટ દોરીને સમજાવો. **07**

અથવા

- (ક) ઝેનર અસર એટલે શું ? ઝેનર ડાયોડની લાક્ષણિકતાઓ દોરો અને તેનું વોલ્ટેજ રેગ્યુલેટર તરીકેનું કાર્ય સમજાવો. **07**

પ્રશ્ન. ૩

- (અ) ફુલવેવ અને હાફવેવ વોલ્ટેજ ડબલર્સ સમજાવો. **05**
- (બ) ટનલ ડાયોડનું તેના સિધ્ધાંત, લાક્ષણિકતાઓ અને ઉપયોગો સહિત વર્ણન કરો. **05**
- (ક) α_{dc} અને β_{dc} ની વ્યાખ્યાઓ આપો. તેમની વચ્ચેનો સંબંધ તારવો. **04**

અથવા

પ્રશ્ન. ૩

- (અ) ડાયોડ કલેમ્પીંગ સર્કીટ વેવફોર્મ સાથે દોરીને સમજાવો. **05**
- (બ) રીપલ ફેક્ટરનું સૂત્ર તારવો. હાફવેવ અને ફુલવેવ રેકિટફાયર માટે રીપલ ફેક્ટરની કિંમતો જણાવો. **04**
- (ક) કોમન બેઝ, કોમન એમીટર અને કોમન કલેક્ટર એમ્પ્લીફાયરની સરખામણી કરો. **04**

પ્રશ્ન. ૪

- (અ) કોમન એમીટર એમ્પ્લીફાયરનું કાર્ય સમજાવો તેમજ તેના વોલ્ટેજ ગેઈન, કરંટ ગેઈન અને પાવર ગેઈનની વ્યાખ્યાઓ આપો. **05**
- (બ) ટ્રાન્ઝીસ્ટરને બાયસ કરવાની વિવિધ રીતો જણાવો. વોલ્ટેજ ડીવાઈડર બાયસ સમજાવો. **05**
- (ક) ઓપરેટીંગ પોઈન્ટમાં ફેરફાર થવાનાં કારણો લખો અને સમજાવો. **04**

અથવા

પ્રશ્ન. ૪

- (અ) એમ્પ્લીફાયરને કાસ્કેડ કરવાની વિવિધ રીતો જણાવો. આર સી કપલીંગ સમજાવો. **05**
- (બ) આર સી કપલ્ડ એમ્પ્લીફાયરનો ફીક્વેન્સી રીસ્પોન્સ સમજાવો. **05**
- (ક) સ્ટેબીલીટી ફેક્ટરની વ્યાખ્યા આપો. કોમન એમીટર એમ્પ્લીફાયર માટે સ્ટેબીલીટી ફેક્ટરનું સૂત્ર તારવો. **04**

પ્રશ્ન. ૫

- (અ) ટ્રાન્ઝીસ્ટરનો ઉપયોગ કરીને શંટ વોલ્ટેજ રેગ્યુલેટર સમજાવો. **05**
- (બ) સ્વીચ મોડ પાવર સપ્લાય વિશે ટૂંક નોંધ લખો. **05**
- (ક) કોમન બેઝ, કોમન એમીટર અને કોમન કલેક્ટર એમ્પ્લીફાયરની એચ પેરામીટર ઇકવીવેલન્ટ સર્કીટ દોરો. **04**

અથવા

પ્રશ્ન. ૫

- (અ) ટ્રાન્ઝીસ્ટરનો ઉપયોગ કરીને સીરીઝ વોલ્ટેજ રેગ્યુલેટર સમજાવો. **05**
- (બ) ડાલ્ફીંગ્ટન પેર એટલે શું ? ડાલ્ફીંગ્ટન એમ્પ્લીફાયર સમજાવો. **05**
- (ક) કોમન એમીટર એમ્પ્લીફાયર માટે એચ પેરામીટર તારવો. **04**
