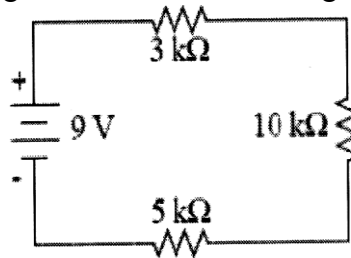



GUJARAT TECHNOLOGICAL UNIVERSITY**Diploma Engineering - SEMESTER-IV • EXAMINATION – SUMMER • 2014****Subject Code: 3342403****Date: 29-05-2014****Subject Name: Electrical Network and Circuits****Time: 10:30 am - 01:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is considered to be Authentic.

- Q.1** (a) Define Kirchhoff's voltage law and find out voltage across $10\text{k}\Omega$ resistor. **07**




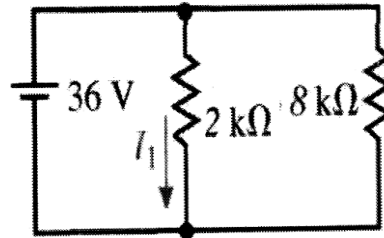- (b) Define Kirchhoff's current law and find out " I_1 " using current divider rule. **07**




- Q.2** (a) Discuss A.C Voltage applied to R-L series circuit with phasor diagram and waveform. **07**

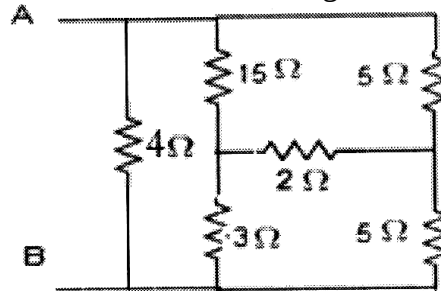- (b) Find out equivalent resistance across A-B using Delta-Wye Transformation. **07**



OR

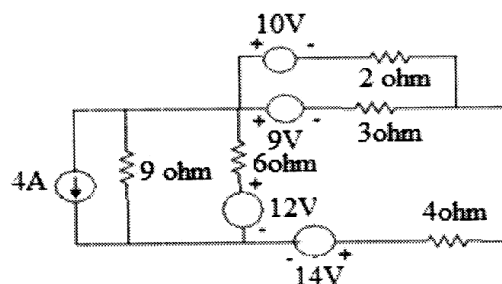- (b) Reduce the network shown in fig. to a single voltage source using source transformation. **07**




- Q.3** (a) Define resonance. Find out resonance frequency for series resonance and also **07**

draw phasor diagram for series resonance circuit.

- (b) Find out current through 3 ohm resistor using nodal analysis technique.

07

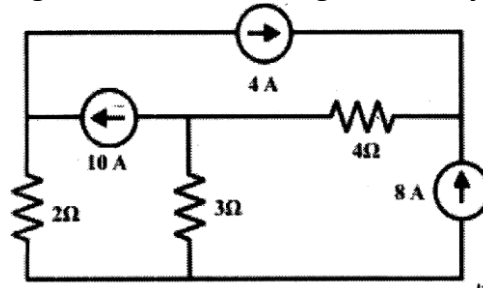


OR

- Q.3 (a) Find out resonance frequency in case of parallel RLC circuit and only draw RLC parallel circuit susceptance variation.
- (b) Find out current “I” using mesh(loop) analysis technique.


07

07

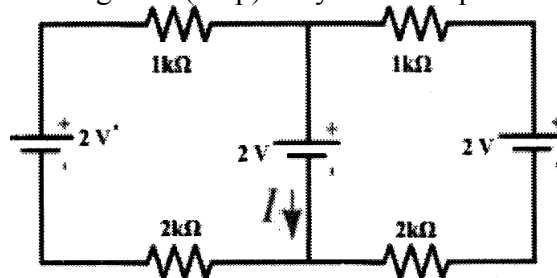


- Q.4 (a) Find current through 16 ohm resistance using Thevenin’s theorem

07

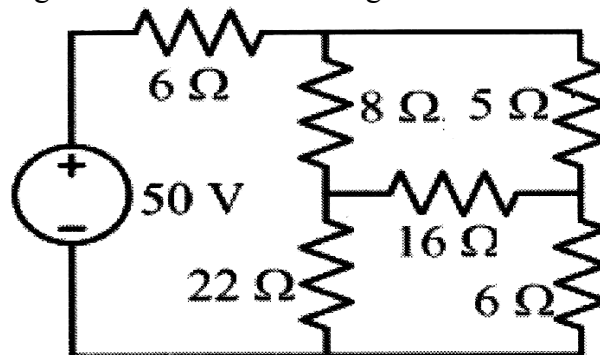

- (b) Use Norton’s theorem to find the “I” through resistor $R=2\Omega$.


07

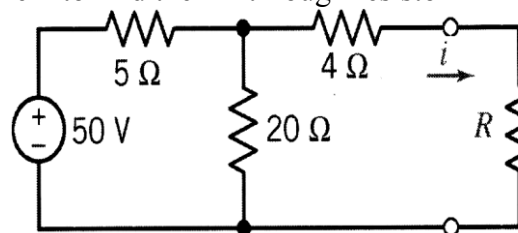

OR

- Q.4 (a) Find “ I_0 ” using super position theorem.

07

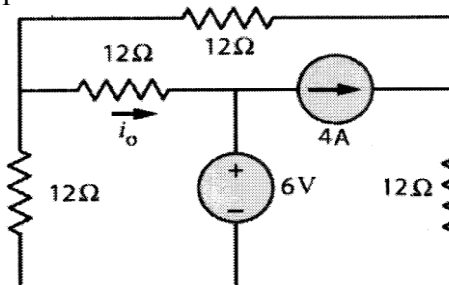

- (b) Explain Millman’s theorem and find out equivalent impedance using Millman’s theorem

07


- Q.5 (a) Explain maximum power transfer theorem in D.C. circuit and find out

07

maximum power flow condition.

- (b) Determine Y-parameter for 2-port network shown in figure.

07

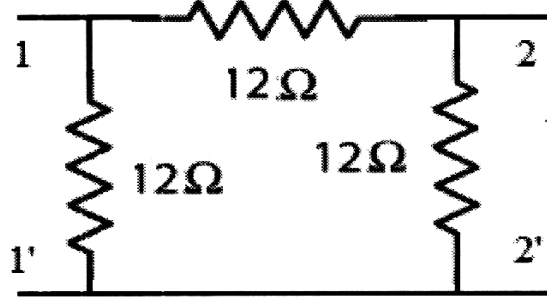


OR

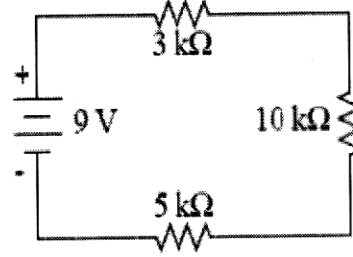
- Q.5 (a) Find out Z parameter in terms of Y parameter 07
(b) Find out equivalent inductance of series connected mutually coupled coils. 07

ગુજરાતી

- પ્રશ્ન. ૧ અ કીર્યોફ નો વોલ્ટેજ નો નિયમ વ્યાખ્યાયિત કરી ને 10kΩ રજિસ્ટર આરપાર વોલ્ટેજ શોધો. 09




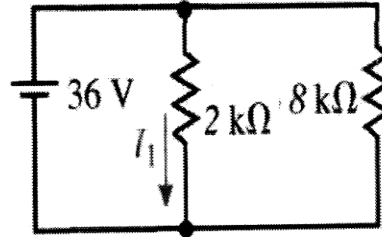- બ કીર્યોફ નો કરંટ નો નિયમ વ્યાખ્યાયિત કરો. અને કરંટ ડીવાયડર ના નિયમ ની મદદ થી "I1" શોધો. 09



- પ્રશ્ન. ૨ અ ફેસર ડાયાગ્રામ અને વેવફોર્મ સાથે A.C વોલ્ટેજ વાળી R-L સીરીઝ સર્કિટ ની ચર્ચા કરો. 09

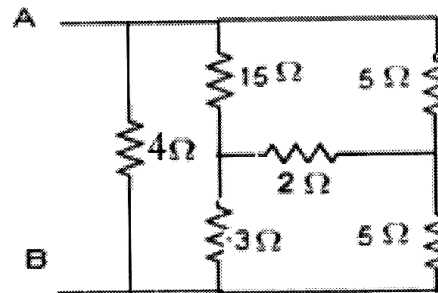
- બ ડેલ્ટા-વાય ટ્રાન્સફોર્મેશન ની મદદ થી સમકક્ષ રસિસ્ટન્સ મેળવો. 09



અથવા


- બ સોર્સ ટ્રાન્સફોર્મેશન ની મદદ થી આપેલ નેટવર્ક ને સિંગલ વોલ્ટેજ સોર્સ માં 09

ફેરવો.

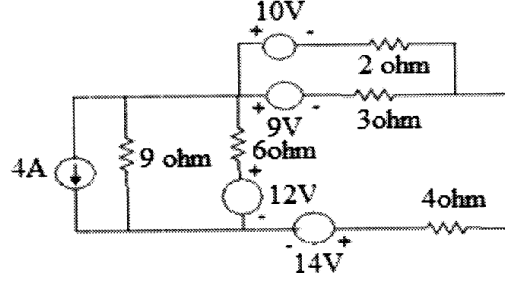

પ્રશ્ન. ૩ અ રેઝોનન્સ વ્યાખ્યાયિત કરો. સીરીઝ રેઝોનન્સ માટે રેઝોનન્સ ફ્રિક્વન્સી મેળવો અને ફેસર ડાયાગ્રામ દોરો. ૦૭

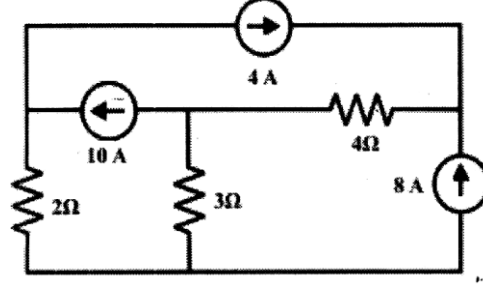
બ નોડલ એનાલીસીસ ની મદદ થી ૩ ઓહ્મ રેસિસ્ટર માં પસાર થતો કરંટ મેળવો. ૦૭




અથવા

પ્રશ્ન. ૩ અ પેરેલલ RLC સર્કિટ માટે રેઝોનન્સ ફ્રિક્વન્સી મેળવો અને સસપ્ટન્સ વેરીએશન ગ્રાફ ફક્ત દોરો. ૦૭

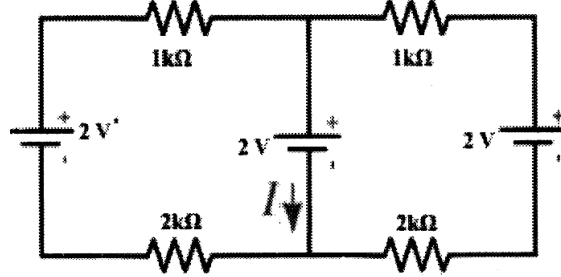
બ મેશ એનાલીસીસ ની મદદ થી કરંટ “I” મેળવો. ૦૭



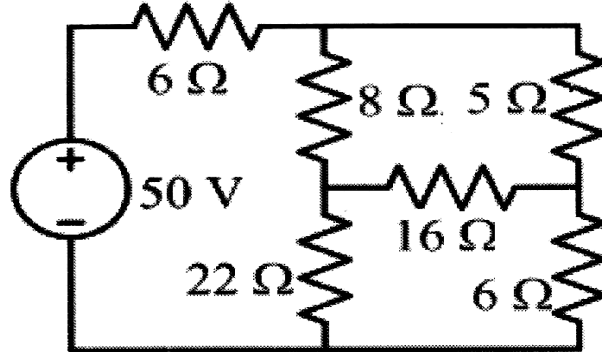પ્રશ્ન. ૪ અ થેવીનીન ના થીયરમ ની મદદ થી 16 ઓહ્મ માંથી પસાર થતો કરંટ મેળવો. ૦૭



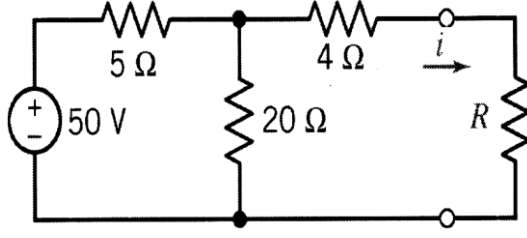
બ નોર્ટન ના થીયરમ ની મદદ થી રેસિસ્ટર $R=2$ ઓહ્મ માંથી પસાર થતો કરંટ “i” શોધો. ૦૭



અથવા

પ્રશ્ન. ૪ અ સુપર પોઝીશન ના નિયમ ની મદદ થી “ i_0 ” મેળવો.

૦૭

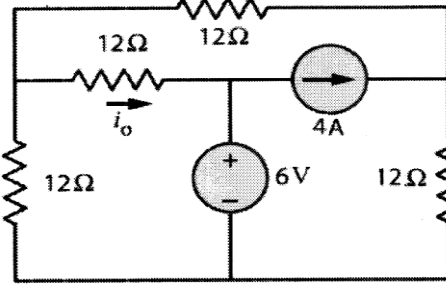

બ મીલમેન નું થીયરમ સમજાવો અને તેના પરથી સમકક્ષ ઈમ્પીડંસ મેળવો.


૦૭

પ્રશ્ન. ૫ અ D.C. સર્કિટ માટે મહત્તમ પાવર ટ્રાન્સફર થીયરમ સમજાવી ને મહત્તમ પાવર ની સરત મેળવો.

૦૭

બ આપેલ ૨ -પોર્ટ નેટવર્ક માટે Y પેરામીટર મેળવો.

૦૭

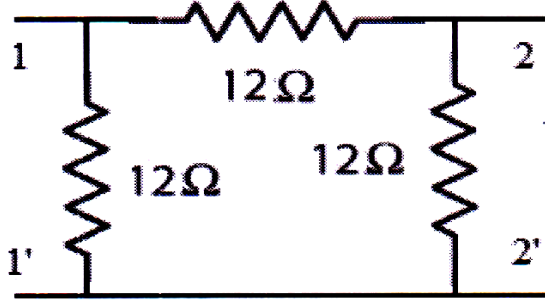

અથવા

પ્રશ્ન. ૫ અ Y પેરામીટર ના સંદર્ભ માં Z પેરામીટર મેળવો.

૦૭

બ સીરીઝ માં જોડેલી મ્યુચ્યુઅલી કપલ્ડ કોઈલ માટે સમકક્ષ ઇન્ડક્ટન્સ મેળવો.

૦૭
