

GUJARAT TECHNOLOGICAL UNIVERSITY
Diploma Engineering - SEMESTER-II (CtoD) • EXAMINATION – SUMMER • 2014

Subject Code: C321102**Date: 26-06-2014****Subject Name: Electronic Networks****Time: 10:30 am - 12:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumption wherever necessary.
3. Each question is of 1 mark.
4. Use of SIMPLE CALCULATOR is permissible. (Scientific/Higher Version not allowed)
5. English version is authentic.

No.	Question Text and Option			
1.	Unit of resistance is			
	A.	Ohm	B.	Faraday
	C.	Henry	D.	Volt
2.	Unit of capacitance is			
	A.	Ohm	B.	Faraday
	C.	Henry	D.	Volt
3.	Unit of energy is			
	A.	Volt	B.	Watt
	C.	Ampere	D.	Faraday
4.	As the number of resistors increase in series, the total resistance is			
	A.	Increase	B.	Constant
	C.	Decrease	D.	Increase and decrease
5.	As the number of capacitor increase in series, the total capacitance is			
	A.	Increase	B.	Constant
	C.	Decrease	D.	Increase and decrease
6.	As the number of resistors increase in parallel, the total resistance is			
	A.	Increase	B.	Constant
	C.	Decrease	D.	Increase and decrease
7.	As the number of capacitor increase in parallel, the total capacitance is			
	A.	Increase	B.	Constant
	C.	Decrease	D.	Increase and decrease
8.	When $R_1=10\ \Omega$ and $R_2=10\ \Omega$ connected in series, what is total resistance?			
	A.	20 k Ω	B.	5 Ω
	C.	20 Ω	D.	15 Ω
9.	When $R_1=10\ \Omega$ and $R_2=10\ \Omega$ connected in parallel, what is total resistance?			
	A.	20 k Ω	B.	5 Ω
	C.	20 Ω	D.	15 Ω
10.	In a network $R=10\ \Omega$ and current across R is 10 A. What is power dissipated at R?			
	A.	1000 V	B.	1000 W
	C.	100 W	D.	10 W
11.	In a network $R=10\ \Omega$ and voltage across R is 10 V. What is power dissipated at R?			
	A.	1000 V	B.	1000 W
	C.	100 W	D.	10 W
12.	When $C_1=10\ \text{F}$ and $C_2=10\ \text{F}$ connected in series, what is total capacitance?			
	A.	5 Ω	B.	5 F
	C.	20 F	D.	15 F
13.	When $C_1=10\ \text{F}$ and $C_2=10\ \text{F}$ connected in parallel, what is total capacitance?			
	A.	5 Ω	B.	5 F
	C.	20 F	D.	15 F

14.	In a network $C=10\text{ F}$ and voltage is 10 V . Energy stored in capacitor is			
	A.	1000 J	B.	1000 W
	C.	500 J	D.	10 W
15.	If the voltage across the capacitor is constant, current through the capacitor is			
	A.	Constant	B.	Zero
	C.	High	D.	Infinite
16.	Reactance of capacitor is increase if frequency			
	A.	Decrease	B.	Remain constant
	C.	Increase	D.	Infinite
17.	Reactance of inductor is increase if frequency			
	A.	Decrease	B.	Remain constant
	C.	Increase	D.	Infinite
18.	If dc voltage is applied across the capacitor then reactance of capacitor is			
	A.	Decrease	B.	Remain constant
	C.	Zero	D.	Infinite
19.	If dc voltage is applied across the inductor then reactance of inductor is			
	A.	Increase	B.	Remain constant
	C.	Zero	D.	Infinite
20.	In a network $L=10\text{ H}$ and current is 10 A . Energy stored in inductor is			
	A.	1000 J	B.	500 W
	C.	500 J	D.	10 J
21.	Which is active element			
	A.	Resistor	B.	Capacitor
	C.	Diode	D.	Voltage Source
22.	Which is passive element			
	A.	Resistor	B.	Capacitor
	C.	Inductor	D.	All
23.	Which is bilateral element			
	A.	Resistor	B.	Transistor
	C.	Diode	D.	None
24.	Which is unilateral element			
	A.	Resistor	B.	Transistor
	C.	Diode	D.	Option B and C
25.	Which is linear element			
	A.	Resistor	B.	Transistor
	C.	Diode	D.	None
26.	Which is non-linear element			
	A.	Resistor	B.	Capacitor
	C.	Diode	D.	All
27.	In a two port network, input current is 5 A and input voltage is 10 V . Output current is 2 A and output voltage is 10 V . Input impedance is			
	A.	$5\text{ }\Omega$	B.	$10\text{ }\Omega$
	C.	$2\text{ }\Omega$	D.	$2.5\text{ }\Omega$
28.	In a two port network, input current is 5 A and input voltage is 10 V . Output current is 2 A and output voltage is 10 V . Output impedance is			
	A.	$5\text{ }\Omega$	B.	$10\text{ }\Omega$
	C.	$2\text{ }\Omega$	D.	$2.5\text{ }\Omega$
29.	In a two port network, input current is 5 A and input impedance is $2\text{ }\Omega$. Output current is 2 A and output voltage is 10 V . Input voltage is			
	A.	5 V	B.	10 V
	C.	3 V	D.	None
30.	In a two port network, input current is 5 A and input impedance is $2\text{ }\Omega$. Output current is 2 A and output impedance is $10\text{ }\Omega$. Output voltage is			
	A.	20 V	B.	10 V
	C.	5 V	D.	None

31.	“Maximum power will be transfer from source to load if load impedance matches with source impedance.” Is a statement of which theorem?			
	A.	Thevenin’s theorem	B.	Nortan’s theorem
	C.	Maximum power transfer theorem	D.	Reciprocity theorem
32.	“Any linear bilateral network having energy sources can be replaced by equivalent circuit consisting of current source in parallel with an equivalent resistance.” Is a statement of which theorem?			
	A.	Thevenin’s theorem	B.	Nortan’s theorem
	C.	Maximum power transfer theorem	D.	Reciprocity theorem
33.	“The algebraic sum of all branch voltages around any closed path in a circuit is zero.” Is a statement of?			
	A.	KCL	B.	None
	C.	KVL	D.	All
34.	Dual of resistance is			
	A.	Resistance	B.	Inductance
	C.	Conductance	D.	KCL
35.	Dual of inductance is			
	A.	Resistance	B.	Inductance
	C.	Capacitance	D.	KCL
36.	Dual of KVL is			
	A.	Resistance	B.	Inductance
	C.	Conductance	D.	KCL
37.	Dual of current is			
	A.	Resistance	B.	Voltage
	C.	Conductance	D.	KCL
38.	Used in Mesh analysis			
	A.	KCL	B.	None
	C.	KVL	D.	All
39.	Used in Node analysis			
	A.	KCL	B.	None
	C.	KVL	D.	All
40.	Dual of mesh analysis is			
	A.	KCL	B.	Node Analysis
	C.	KVL	D.	None
41.	“The ratio of maximum energy stored per cycle to the energy dissipated per cycle” is called			
	A.	Inductance	B.	Quality factor
	C.	Capacitance	D.	Resoance
42.	The quality factor of inductor is			
	A.	$Q_L = \omega L/R$	B.	$Q_L = \omega/LR$
	C.	$Q_L = 1/\omega LR$	D.	None
43.	The quality factor of capacitor is			
	A.	$Q_C = \omega C/R$	B.	$Q_C = \omega/CR$
	C.	$Q_C = 1/\omega CR$	D.	None
44.	“The impedance offered by a complex network consisting of reactive component is purely resistive”. The phenomenon is called as?			
	A.	Quality factor	B.	Thevenin’s theorem
	C.	Resonance	D.	Maximum power transfer theorem
45.	The frequency at which resonance occurs, is known as			
	A.	Bandwidth	B.	Resonance frequency
	C.	Critical frequency	D.	None
46.	Find quality factor of inductor for $L=100\text{ H}$, $\omega=1$ and $R=10\ \Omega$.			
	A.	10	B.	30

	C.	20	D.	None
47.	Find bandwidth for given quality factor 10 and resonance frequency is 1000 Hz.			
	A.	10 Hz	B.	10 kHz
	C.	100 Hz	D.	100 kHz
48.	Find quality factor of capacitor for $C=0.01\text{ H}$, $\omega=1$ and $R=10\ \Omega$.			
	A.	10	B.	30
	C.	20	D.	None
49.	Transformer works on			
	A.	Ohm's law	B.	KCL
	C.	Faraday's law	D.	None
50.	Doubly tuned air-core transformer has			
	A.	Primary circuit has adjustable capacitive reactance	B.	Secondary circuit has adjustable capacitive reactance
	C.	Option A and B both	D.	None
51.	Attenuator is used to			
	A.	Increase power level of input signal	B.	Reduce power level of input signal
	C.	Increase frequency level of input signal	D.	None
52.	Which is phase equalizer?			
	A.	Series	B.	Shunt
	C.	Lattice	D.	Full shunt
53.	The network designed to provide compensation against distortions that occur in a signal while passing through an network is called			
	A.	Attenuator	B.	Quality factor
	C.	Resonance	D.	Equalizer
54.	Which is four terminals amplitude equalizer?			
	A.	Series	B.	Shunt
	C.	None	D.	Full shunt
55.	Which is two terminals amplitude equalizer?			
	A.	Series	B.	Full series
	C.	Lattice	D.	Full shunt
56.	It passes lower frequencies and stop high frequencies.			
	A.	High pass filter	B.	Low pass filter
	C.	Band pass filter	D.	Band stop filter
57.	It stops lower frequencies and pass high frequencies.			
	A.	High pass filter	B.	Low pass filter
	C.	Band pass filter	D.	Band stop filter
58.	It stops certain band of frequencies.			
	A.	High pass filter	B.	Low pass filter
	C.	Band pass filter	D.	Band stop filter
59.	It passes certain band of frequencies.			
	A.	High pass filter	B.	Low pass filter
	C.	Band pass filter	D.	Band stop filter
60.	Notch filter is			
	A.	High pass filter	B.	Low pass filter
	C.	Band pass filter	D.	Band stop filter
61.	For an ideal filter			
	A.	For pass band $\alpha=0$.	B.	For stop band $\alpha=\text{infinite}$.
	C.	Option A and B	D.	None
62.	Which is passive filters classification.			
	A.	Constant k filters	B.	M derived filters
	C.	Option A and B	D.	None
63.	Lower than 10000 Hz frequencies should pass and higher than 10000 should stop. Which filter should use.			

	A.	High pass filter	B.	Low pass filter
	C.	Band pass filter	D.	Band stop filter
64.	Lower than 10000 Hz frequencies should stop and higher than 10000 should pass. Which filter should use.			
	A.	High pass filter	B.	Low pass filter
	C.	Band pass filter	D.	Band stop filter
65.	Frequencies between 100 Hz to 1000 Hz should pass. All other frequencies should stop. Which filter should use.			
	A.	High pass filter	B.	Low pass filter
	C.	Band pass filter	D.	Band stop filter
66.	Frequencies between 100 Hz to 1000 Hz should stop. All other frequencies should pass. Which filter should use.			
	A.	High pass filter	B.	Low pass filter
	C.	Band pass filter	D.	Band stop filter
67.	“The characteristics impedance does not remain constant in pass band.” Is limitation of			
	A.	Constant k filters	B.	M derived filters
	C.	Option A and B	D.	None
68.	“Attenuation does not occur rapidly in the stop band.” Is limitation of			
	A.	Constant k filters	B.	M derived filters
	C.	Option A and B	D.	None
69.	Which elements use to design k-constant T type passive high pass filter?			
	A.	R	B.	L
	C.	C	D.	All
70.	Which elements use to design m-derived T type passive low pass filter?			
	A.	R	B.	L
	C.	C	D.	All

ગુજરાતી

નં.	પ્રશ્ન તેમજ વિકલ્પ			
૧.	અવરોધ નો યુનિટ			
	A.	ઓહ્મ	B.	ફેરેડે
	C.	હેરી	D.	વોલ્ટ
૨.	કેપેસિટન્સ નો યુનિટ			
	A.	ઓહ્મ	B.	ફેરેડે
	C.	હેરી	D.	વોલ્ટ
૩.	એનર્જી નો યુનિટ			
	A.	વોલ્ટ	B.	વોટ
	C.	એમ્પીયર	D.	ફેરેડે
૪.	સીરીઝ મા રજીસ્ટર ની સંખ્યા વધારવામા આવે તો કુલ રજીસ્ટન્ટ			
	A.	વધે	B.	અચળ
	C.	ઘટે	D.	વધે અને ઘટે
૫.	સીરીઝ મા કેપેસિટર ની સંખ્યા વધારવામા આવે તો કુલ કેપેસિટન્સ			
	A.	વધે	B.	અચળ
	C.	ઘટે	D.	વધે અને ઘટે

૬.	પેરેલલ મા રેજીસ્ટર ની સંખ્યા વધારવામા આવે તો કુલ રેજીસ્ટન્ટ			
	A.	વધે	B.	અચળ
	C.	ઘટે	D.	વધે અને ઘટે
૭.	પેરેલલ મા કેપેસીટર ની સંખ્યા વધારવામા આવે તો કુલ કેપેસીટન્સ			
	A.	વધે	B.	અચળ
	C.	ઘટે	D.	વધે અને ઘટે
૮.	જ્યારે $R_1=10\ \Omega$ અને $R_2=10\ \Omega$ સીરીઝ મા જોડવામા આવે તો કુલ રેજીસ્ટન્ટ શુ?			
	A.	$20\ k\Omega$	B.	$5\ \Omega$
	C.	$20\ \Omega$	D.	$15\ \Omega$
૯.	જ્યારે $R_1=10\ \Omega$ અને $R_2=10\ \Omega$ પેરેલલ મા જોડવામા આવે તો કુલ રેજીસ્ટન્ટ શુ?			
	A.	$20\ k\Omega$	B.	$5\ \Omega$
	C.	$20\ \Omega$	D.	$15\ \Omega$
૧૦.	નેટવર્ક મા $R=10\ \Omega$ પાસે કરંટ $I=10\ A$ છે. તો R પાસે પાવર વપરાય ?			
	A.	$1000\ V$	B.	$1000\ W$
	C.	$100\ W$	D.	$10\ W$
૧૧.	નેટવર્ક મા $R=10\ \Omega$ પાસે વોલ્ટ $V=10\ V$ છે. તો R પાસે પાવર વપરાય ?			
	A.	$1000\ V$	B.	$1000\ W$
	C.	$100\ W$	D.	$10\ W$
૧૨.	જ્યારે $C_1=10\ F$ અને $C_2=10\ F$ સીરીઝ મા જોડવામા આવે તો કુલ કેપેસીટન્સ શુ?			
	A.	$5\ \Omega$	B.	$5\ F$
	C.	$20\ F$	D.	$15\ F$
૧૩.	જ્યારે $C_1=10\ F$ અને $C_2=10\ F$ પેરેલલ મા જોડવામા આવે તો કુલ કેપેસીટન્સ શુ?			
	A.	$5\ \Omega$	B.	$5\ F$
	C.	$20\ F$	D.	$15\ F$
૧૪.	નેટવર્ક મા $C=10\ F$ અને વોલ્ટ $V=10\ V$ છે. તો કેપેસીટર મા એનર્જી જમા થાય?			
	A.	$1000\ J$	B.	$1000\ W$
	C.	$500\ J$	D.	$10\ W$
૧૫.	જો અચળ વોલ્ટેજ કેપેસીટર ને આપવા મા આવે તો કેપેસીટર મા કરંટ?			
	A.	અચળ રહે	B.	શુન્ય
	C.	વધે	D.	અનંત
૧૬.	કેપેસીટર નુ રિઅક્ટન્સ વધે જો ફ્રિક્વન્સિ			
	A.	ઘટે	B.	અચળ રહે
	C.	વધે	D.	અનંત
૧૭.	ઇન્ડક્ટર નુ રિઅક્ટન્સ વધે જો ફ્રિક્વન્સિ			
	A.	ઘટે	B.	અચળ રહે
	C.	વધે	D.	અનંત
૧૮.	જો ડીસી વોલ્ટેજ કેપેસીટર ને આપવા મા આવે તો કેપેસીટર નુ રિઅક્ટન્સ ?			

	A.	ઘટે	B.	અચળ રહે
	C.	શુન્ય થાય	D.	અનંત
૧૯.	જો ડીસી વોલ્ટેજ ઇન્ક્રીટ ને આપવા મા આવે તો ઇન્ક્રીટ નુ રિઅક્ટંસ ?			
	A.	વધે	B.	અચળ રહે
	C.	શુન્ય થાય	D.	અનંત
૨૦.	નેટવર્ક મા $L=10\text{ H}$ અને કરંટ $I=10\text{ A}$ છે. તો ઇન્ક્રીટ મા એનર્જી જમા થાય?			
	A.	1000 J	B.	500 W
	C.	500 J	D.	10 J
૨૧.	એક્ટીવ એલિમેન્ટ કયો?			
	A.	રેજીસ્ટર	B.	કેપેસીટર
	C.	ડાયોડ	D.	બધા
૨૨.	પેસીવ એલિમેન્ટ કયો?			
	A.	રેજીસ્ટર	B.	કેપેસીટર
	C.	ઇન્ક્રીટ	D.	બધા
૨૩.	બાય લીટરલ એલિમેન્ટ કયો?			
	A.	રેજીસ્ટર	B.	ટ્રાન્ઝીસ્ટર
	C.	ડાયોડ	D.	કોઇ નહી
૨૪.	યુનીલીટરલ એલિમેન્ટ કયો?			
	A.	રેજીસ્ટર	B.	ટ્રાન્ઝીસ્ટર
	C.	ડાયોડ	D.	B અને C
૨૫.	લીનીયર એલિમેન્ટ કયો?			
	A.	રેજીસ્ટર	B.	ટ્રાન્ઝીસ્ટર
	C.	ડાયોડ	D.	કોઇ નહી
૨૬.	નોન-લીનીયર એલિમેન્ટ કયો?			
	A.	રેજીસ્ટર	B.	કેપેસીટર
	C.	ડાયોડ	D.	બધા
૨૭.	બે પોર્ટ નેટવર્ક મા ઇનપુટ કરંટ 5 A અને ઇનપુટ વોલ્ટેજ 10 V છે. આઉટપુટ કરંટ 2 A અને આઉટપુટ વોલ્ટેજ 10 V છે. ઇનપુટ ઇમ્પિડન્સ શુ?			
	A.	5 Ω	B.	10 Ω
	C.	2 Ω	D.	2.5 Ω
૨૮.	બે પોર્ટ નેટવર્ક મા ઇનપુટ કરંટ 5 A અને ઇનપુટ વોલ્ટેજ 10 V છે. આઉટપુટ કરંટ 2 A અને આઉટપુટ વોલ્ટેજ 10 V છે. આઉટપુટ ઇમ્પિડન્સ શુ?			
	A.	5 Ω	B.	10 Ω
	C.	2 Ω	D.	2.5 Ω
૨૯.	બે પોર્ટ નેટવર્ક મા ઇનપુટ કરંટ 5 A અને ઇનપુટ ઇમ્પિડન્સ 2 Ω છે. આઉટપુટ કરંટ 2 A અને આઉટપુટ વોલ્ટેજ 10 V છે. ઇનપુટ વોલ્ટેજ શુ?			
	A.	5V	B.	10 V

	C.	3 V	D.	કોઈ નહી
30.	બે પોર્ટ નેટવર્ક મા ઇનપુટ કરંટ 5 A અને ઇનપુટ ઇમ્પેડન્સ 2 Ω છે. આઉટપુટ કરંટ 2 A અને આઉટપુટ ઇમ્પેડન્સ 10 Ω છે. આઉટપુટ વોલ્ટેજ શુ?			
	A.	20 V	B.	10 V
	C.	5 V	D.	કોઈ નહી
31.	“Maximum power will be transfer from source to load if load impedance matches with source impedance.” એ કઈ થીયરી નુ વાક્ય છે?			
	A.	Thevenin થીયરી	B.	Norton થીયરી
	C.	Maximum power transfer થીયરી	D.	Reciprocity થીયરી
32.	“Any linear bilateral network having energy sources can be replaced by equivalent circuit consisting of current source in parallel with an equivalent resistance.” એ કઈ થીયરી નુ વાક્ય છે?			
	A.	Thevenin થીયરી	B.	Norton થીયરી
	C.	Maximum power transfer થીયરી	D.	Reciprocity થીયરી
33.	“The algebraic sum of all branch voltages around any closed path in a circuit is zero.” એ કોનુ વાક્ય છે?			
	A.	KCL	B.	કોઈ નહી
	C.	KVL	D.	બધા
34.	રેજીસ્ટન્ટ નુ ડ્યુલ?			
	A.	રેજીસ્ટન્ટ	B.	ઇન્ડક્ટન્સ
	C.	કન્ડક્ટન્સ	D.	KCL
35.	ઇન્ડક્ટન્સ નુ ડ્યુલ?			
	A.	રેજીસ્ટન્ટ	B.	ઇન્ડક્ટન્સ
	C.	કેપેસિટન્સ	D.	KCL
36.	KVL નુ ડ્યુલ?			
	A.	રેજીસ્ટન્ટ	B.	ઇન્ડક્ટન્સ
	C.	કેપેસિટન્સ	D.	KCL
37.	કરંટ નુ ડ્યુલ?			
	A.	રેજીસ્ટન્ટ	B.	વોલ્ટેજ
	C.	કન્ડક્ટન્સ	D.	KCL
38.	મેસ એનાલીસીસ મા વપરાય?			
	A.	KCL	B.	કોઈ નહી
	C.	KVL	D.	બધા
39.	નોડ એનાલીસીસ મા વપરાય?			
	A.	KCL	B.	કોઈ નહી
	C.	KVL	D.	બધા

૪૦.	મેસ એનાલીસીસ નુ ડ્યુલ?			
	A.	KCL	B.	નોડ એનાલીસીસ
	C.	KVL	D.	કોઇ નહી
૪૧.	“The ratio of maximum energy stored per cycle to the energy dissipated per cycle” ને શુ કહેવાય?			
	A.	ઇન્ડક્ટન્સ	B.	કોલીટી ફેક્ટર
	C.	કેપેસીટન્સ	D.	રીઝોનન્સ
૪૨.	ઇન્ડક્ટર નો કોલીટી ફેક્ટર?			
	A.	$Q_L = \omega L/R$	B.	$Q_L = \omega/LR$
	C.	$Q_L = 1/\omega LR$	D.	કોઇ નહી
૪૩.	કેપેસીટર નો કોલીટી ફેક્ટર?			
	A.	$Q_C = \omega C/R$	B.	$Q_C = \omega/CR$
	C.	$Q_C = 1/\omega CR$	D.	કોઇ નહી
૪૪.	“The impedance offered by a complex network consisting of reactive component is purely resistive”. આ ઘટના ને શુ કહેવાય?			
	A.	કોલીટી ફેક્ટર	B.	Thevenin થીયરી
	C.	રીઝોનન્સ	D.	Maximum power transfer થીયરી
૪૫.	રીઝોનન્સ ઉદભવે તે ફ્રીક્વેન્સી ને શુ કહેવાય?			
	A.	બેંડવીથ	B.	રીઝોનન્સ ફ્રીક્વેન્સી
	C.	ક્રિટિકલ ફ્રીક્વેન્સી	D.	કોઇ નહી
૪૬.	$L=100\text{ H}$, $\omega=1$ અને $R=10\ \Omega$ માટે ઇન્ડક્ટર નો કોલીટી ફેક્ટર શોધો?			
	A.	10	B.	30
	C.	20	D.	કોઇ નહી
૪૭.	કોલીટી ફેક્ટર 10 અને રીઝોનન્સ ફ્રીક્વેન્સી 1000 Hz માટે બેંડવીથ શોધો?			
	A.	10 Hz	B.	10 kHz
	C.	100 Hz	D.	100 kHz
૪૮.	$C=0.01\text{ H}$, $\omega=1$ અને $R=10\ \Omega$ માટે કેપેસીટર નો કોલીટી ફેક્ટર શોધો?			
	A.	10	B.	30
	C.	20	D.	કોઇ નહી
૪૯.	ટ્રાંસ્ફોર્મર કામ કરે?			
	A.	Ohm's law	B.	KCL
	C.	Faraday's law	D.	કોઇ નહી
૫૦.	ડબ્લી ટ્યુન એર કોર ટ્રાંસ્ફોર્મર પાસે			
	A.	Primary circuit has adjustable capacitive reactance	B.	Secondary circuit has adjustable capacitive reactance
	C.	A અને B	D.	કોઇ નહી
૫૧.	એટેન્યુટર વપરાય?			
	A.	ઇનપુટ સીઝનલ નો પાવર લેવલ	B.	ઇનપુટ સીઝનલ નો પાવર લેવલ ઘટાડવા

		વધારવા		
	C.	ઇનપુટ સીઝનલ નો ફીક્વેન્સી લેવલ વધારવા	D.	કોઇ નહી
૫૨.	ફેઝ ઇકવલાઇઝર કયુ છે?			
	A.	Series	B.	Shunt
	C.	Lattice	D.	Full shunt
૫૩.	“The network designed to provide compensation against distortions that occur in a signal while passing through an network.” ને શુ કહેવાય?			
	A.	એટેન્યુટર	B.	કોલીટી ફેક્ટર
	C.	રીઝોનન્સ	D.	ઇકવલાઇઝર
૫૪.	૪-ટર્મીનલ એમ્પ્લિટયુડ ઇકવલાઇઝર કયુ છે?			
	A.	Series	B.	Shunt
	C.	કોઇ નહી	D.	Full shunt
૫૫.	૨-ટર્મીનલ એમ્પ્લિટયુડ ઇકવલાઇઝર કયુ છે?			
	A.	Series	B.	Full series
	C.	Lattice	D.	Full shunt
૫૬.	તે લોવર ફીક્વેન્સીસ પાસ કરે અને હાઇ ફીક્વેન્સીસ ને સ્ટોપ કરે.			
	A.	હાઇપાસ ફીલ્ટર	B.	લોપાસ ફીલ્ટર
	C.	બેન્ડપાસ ફીલ્ટર	D.	બેન્ડસ્ટોપ ફીલ્ટર
૫૭.	તે લોવર ફીક્વેન્સીસ સ્ટોપ કરે અને હાઇ ફીક્વેન્સીસ ને પાસ કરે.			
	A.	હાઇપાસ ફીલ્ટર	B.	લોપાસ ફીલ્ટર
	C.	બેન્ડપાસ ફીલ્ટર	D.	બેન્ડસ્ટોપ ફીલ્ટર
૫૮.	તે બેન્ડ ફીક્વેન્સીસ ને સ્ટોપ કરે.			
	A.	હાઇપાસ ફીલ્ટર	B.	લોપાસ ફીલ્ટર
	C.	બેન્ડપાસ ફીલ્ટર	D.	બેન્ડસ્ટોપ ફીલ્ટર
૫૯.	તે બેન્ડ ફીક્વેન્સીસ ને પાસ કરે.			
	A.	હાઇપાસ ફીલ્ટર	B.	લોપાસ ફીલ્ટર
	C.	બેન્ડપાસ ફીલ્ટર	D.	બેન્ડસ્ટોપ ફીલ્ટર
૬૦.	નોચ ફીલ્ટર છે?			
	A.	હાઇપાસ ફીલ્ટર	B.	લોપાસ ફીલ્ટર
	C.	બેન્ડપાસ ફીલ્ટર	D.	બેન્ડસ્ટોપ ફીલ્ટર
૬૧.	આદર્શ ફીલ્ટર માટે			
	A.	પાસબેન્ડ માટે $\alpha=0$	B.	સ્ટોપબેન્ડ માટે $\alpha=\infty$
	C.	A અને B	D.	કોઇ નહી
૬૨.	પેસીવ ફીલ્ટર વર્ગીકરણ કયુ?			
	A.	Constant k ફીલ્ટર્સ	B.	M derived ફીલ્ટર્સ
	C.	A અને B	D.	કોઇ નહી

૬૩.	તે 10000 Hz કરતા લોવર ફ્રીક્વેન્સીસ પાસ કરે અને તે 10000 Hz કરતા હાઇ ફ્રીક્વેન્સીસ ને સ્ટોપ કરે. કયુ ફિલ્ટર વપરાય?			
	A.	હાઇપાસ ફિલ્ટર	B.	લોપાસ ફિલ્ટર
	C.	બેન્ડપાસ ફિલ્ટર	D.	બેન્ડસ્ટોપ ફિલ્ટર
૬૪.	તે 10000 Hz કરતા લોવર ફ્રીક્વેન્સીસ સ્ટોપ કરે અને તે 10000 Hz કરતા હાઇ ફ્રીક્વેન્સીસ ને પાસ કરે. કયુ ફિલ્ટર વપરાય?			
	A.	હાઇપાસ ફિલ્ટર	B.	લોપાસ ફિલ્ટર
	C.	બેન્ડપાસ ફિલ્ટર	D.	બેન્ડસ્ટોપ ફિલ્ટર
૬૫.	તે 100 Hz અને 1000 Hz વચ્ચે ની ફ્રીક્વેન્સીસ પાસ કરે. તે સીવાય ની ફ્રીક્વેન્સીસ ને સ્ટોપ કરે. કયુ ફિલ્ટર વપરાય?			
	A.	હાઇપાસ ફિલ્ટર	B.	લોપાસ ફિલ્ટર
	C.	બેન્ડપાસ ફિલ્ટર	D.	બેન્ડસ્ટોપ ફિલ્ટર
૬૬.	તે 100 Hz અને 1000 Hz વચ્ચે ની ફ્રીક્વેન્સીસ સ્ટોપ કરે. તે સીવાય ની ફ્રીક્વેન્સીસ ને પાસ કરે. કયુ ફિલ્ટર વપરાય?			
	A.	હાઇપાસ ફિલ્ટર	B.	લોપાસ ફિલ્ટર
	C.	બેન્ડપાસ ફિલ્ટર	D.	બેન્ડસ્ટોપ ફિલ્ટર
૬૭.	“પાસબેન્ડ મા લાક્ષણીક ઇમ્પીડન્સ સ્થિર રહેતુ નથી.” તે લીમીટેશન			
	A.	કોન્સ્ટન્ટ k ફિલ્ટર	B.	M ડીરાઇવડ ફિલ્ટર
	C.	A અને B	D.	કોઇ નહી
૬૮.	“સ્ટોપબેન્ડ મા એટેન્યુશન ઝડપથી ઉદભવતુ નથી.” તે લીમીટેશન			
	A.	કોન્સ્ટન્ટ k ફિલ્ટર	B.	M ડીરાઇવડ ફિલ્ટર
	C.	A અને B	D.	કોઇ નહી
૬૯.	K કોન્સ્ટન્ટ T ટાઇપ હાઇપાસ પેસીવ ફિલ્ટર ડીઝાઇન કરવા કયા એલીમેન્ટસ વાપરવા જોઇએ?			
	A.	R	B.	L
	C.	C	D.	બધા
૭૦.	M ડીરાઇવડ T ટાઇપ લોપાસ પેસીવ ફિલ્ટર ડીઝાઇન કરવા કયા એલીમેન્ટસ વાપરવા જોઇએ?			
	A.	R	B.	L
	C.	C	D.	બધા
