

GUJARAT TECHNOLOGICAL UNIVERSITY**Diploma Engineering - SEMESTER-I/ • EXAMINATION – SUMMER 2013****Subject Code: 3310702****Date: 19-06-2013****Subject Name: Fundamentals of Digital Electronics****Time: 10:30 am - 02:30 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make Suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Use of programmable & Communication aids are strictly prohibited.
5. Use of only simple calculator is permitted in Mathematics.
6. English version is authentic.

- Q.1** Answer any seven out of ten. **14**
1. $(723)_8 = (\quad)_2 = (\quad)_{16}$
 2. What is Straight Binary code?
 3. Define: Logic Circuit, Logic Gate.
 4. Perform 1's and 2's complement on : (i) 111 (ii) 101
 5. Calculate : (i) $10110101 + 10100011$ (ii) $11001 - 10111$
 6. Write down Truth table of AND, EX-OR, NOR and NAND gate.
 7. Draw logic circuit of EX-NOR.
 8. $(11000111)_{\text{Ex-3}} = (\quad)_{10}$
 9. What is Quad and Octet?
 10. Draw block diagram of n-bit Digital Comparator.
- Q.2** (a) State and Prove De-Morgan's theorems. **06**
- OR
- (a) List and explain Non-Weighted Binary code. **06**
- (b) Simplify following Boolean function in SOP form using K-Map and implement using logic gates. **04**
- $$F(A,B,C,D) = \sum_m(1,4,6,9,10,11,14,15)$$
- OR
- (b) Minimize the following Boolean Function using K-Map. **04**
- $$F(A,B,C,D) = \pi_M(1,2,3,8,9,10,11,14) \cdot d(7,15)$$
- (c) List down Properties of Boolean Algebra. Explain Absorption property. **04**
- OR
- (c) Draw logic circuit of following Boolean expressions. **04**
- (i) $(A + B)' C + (A + C)' B$ (ii) $AD + ACD' + B'$
- Q.3** (a) Explain Half-Subtractor with its block diagram and Draw logic circuit of Full-Subtractor using two Half-Subtractor. **06**
- OR
- (a) Explain Half -Adder with its block diagram and Draw logic circuit of Full-Adder using two Half-Adder and one OR gate. **06**
- (b) Derive Logic expression of Half-Adder using Karnaugh map and Draw Logic circuit of Half-Adder using (AND-OR-INVERT) gate. **04**
- OR
- (b) Derive Logic expression of Half-Subtractor using Karnaugh map and Draw Logic circuit of Half-Subtractor using (AND-OR-INVERT) gate. **04**
- (c) Differentiate Combinational Logic Circuit and Sequential Logic Circuit. **04**
- OR
- (c) Compare Half-adder and Full adder. **04**

Q.4	(a) Define Universal Gate and realize OR and EX-OR gate using NAND gate.	06
	OR	
	(a) Explain Max term and Min term with example.	06
	(b) Prove following expression using Boolean Algebra.	04
	(i) $(A' + B)(A + B + D)D' = BD'$	
	(ii) $ABC + A'B + ABC' = B$	
	OR	
	(b) Reduce following function using K-Map	04
	$F(A,B,C,D) = \pi (0,1,2,3,8,9,10,11,12,13)$	
	(c) What is K-Map? Explain Don't-care-Condition in K-Map.	04
Q.5	(a) Draw Half-Adder circuit using only NAND gates.	03
	(b) Explain Demultiplexer with the help of block diagram and Derive logic expressions of 1-to-4 Demultiplexer using its truth table.	05
	(c) What is Encoder? Derive logic circuit of Octal to Binary encoder.	05

ગુજરાતી

પ્રશ્ન. ૧	દશમાંથી કોઇપણ સાતના જવાબ આપો.	૧૪
૧.	$(723)_8 = (\quad)_2 = (\quad)_{16}$	
૨.	સ્ટ્રેટ બાઇનરી કોડ એટલે શું?	
૩.	લોજીક સર્કિટ અને લોજીક ગેટ વ્યાખ્યાયીત કરો.	
૪.	(i) 111 (ii) 101 પર 1's અને 2's ની ગણતરી કરો.	
૫.	ગણતરી કરો : (i) $10110101 + 10100011$ (ii) $11001 - 10111$	
૬.	AND, EX-OR, NOR અને NAND ગેટ ના ટ્રુથ ટેબલ લખો.	
૭.	EX-NOR ની લોજીક સર્કિટ દોરો.	
૮.	$(11000111)_{\text{Ex-3}} = (\quad)_{10}$	
૯.	ક્વોડ અને ઓક્ટેટ એટલે શું?	
૧૦	n - બીટ ડીજીટલ કમ્પેરેટર ની બ્લોક આકૃતી દોરો.	
પ્રશ્ન. ૨	અ ડી-મોર્ગન થીયરમ લખો અને સાબીત કરો.	૦૬
	અથવા	
અ	નોન-વેઇટેડ બાઇનરી કોડ લખો અને સમજાવો.	૦૬
બ	નીચેના બુલીયન ફંક્શન નું SOP ફોર્મ માં K-મેપ ની મદદ થી સાદુરૂપ આપો.	૦૪
	$F(A,B,C,D) = \sum_m(1,4,6,9,10,11,14,15)$	
	અથવા	
બ	નીચેના બુલીયન ફંક્શન નું K-મેપ ની મદદ થી સાદુરૂપ આપો.	૦૪
	$F(A,B,C,D) = \pi_M(1,2,3,8,9,10,11,14) \cdot d(7,15)$	
ક	બુલીયન એલ્જેબ્રા ના ગુણધર્મો જણાવો. એબ્સોર્પ્શન ગુણધર્મ સમજાવો.	૦૪
	અથવા	
ક	નીચેના બુલીયન સમીકરણો ની લોજીક સર્કીટ દોરો.	૦૪
	(i) $(A + B)' C + (A + C)' B$ (ii) $AD + ACD' + B'$	

- પ્રશ્ન. ૩ અ હાફ-સબ્ટ્રેક્ટર ને તેના બ્લોક ડાયાગ્રામ સાથે સમજાવો અને બે હાફ-સબ્ટ્રેક્ટર ૦૬
નો ઉપયોગ કરી ફુલ-સબ્ટ્રેક્ટર ની લોજીક સર્કીટ દોરો.
- અથવા
- અ હાફ-એડર ને તેના બ્લોક ડાયાગ્રામ સાથે સમજાવો અને બે હાફ-એડર તથા ૦૬
એક OR ગેટ નો ઉપયોગ કરી ફુલ-એડર ની લોજીક સર્કીટ દોરો.
- બ કાર્નોફ મેપ પર થી હાફ-એડર નું લોજીક એક્સ્પ્રેશન તારવો અને (AND-OR- ૦૪
INVERT) ગેટ ની મદદ થી હાફ-એડર ની લોજીક સર્કીટ દોરો.
- અથવા
- બ કાર્નોફ મેપ પર થી હાફ-સબ્ટ્રેક્ટર નું લોજીક એક્સ્પ્રેશન તારવો અને (AND- ૦૪
OR-INVERT) ગેટ ની મદદ થી હાફ-સબ્ટ્રેક્ટર ની લોજીક સર્કીટ દોરો.
- ક કોમ્બીનેશનલ અને સીક્વન્શીયલ લોજીક સર્કીટ નો તફાવત લખો. ૦૪
- અથવા
- ક હાફ-એડર અને ફુલ-એડર ની સરખામણી કરો. ૦૪
- પ્રશ્ન. ૪ અ સાર્વત્રીક ગેટ વ્યાખ્યાયીત કરો અને NAND ગેટ ની મદદ થી OR અને EX- ૦૬
OR ગેટ મેળવો.
- અથવા
- અ મેક્ષ ટર્મ અને મીન ટર્મ ઉદાહરણ સાથે સમજાવો. ૦૬
- બ નીચેના સમીકરણો ને બુલીયન એલ્જેબ્રા ની મદદ થી સાબીત કરો. ૦૪
(i) $(A' + B)(A + B + D)D' = BD'$
(ii) $ABC + A'B + ABC' = B$
- અથવા
- બ નીચેના ફંક્શન નું K-Map ની મદદ થી સાદુરૂપ આપો. ૦૪
 $F(A,B,C,D) = \pi (0,1,2,3,8,9,10,11,12,13)$
- ક K-Map એટલે શું? K-Map માં ડોન્ટ-કેર-કંડિશન સમજાવો. ૦૪
- પ્રશ્ન. ૫ અ હાફ-એડર સર્કીટ ખાલી NAND ગેટ ના ઉપયોગ થી દોરો. ૦૩
- બ ડીમલ્ટીપ્લેક્સર તેના બ્લોક ડાયાગ્રામ ની મદદ થી સમજાવો અને તેના ટ્રુથ ૦૫
ટેબલ ની મદદ થી ૧-ટુ-૪ ડીમલ્ટીપ્લેક્સર નું લોજીક એક્સ્પ્રેશન તારવો.
- ક એનકોડર એટલે શું? ઓક્ટલ થી બાઇનરી એનકોડર ની લોજીક સર્કીટ તારવો. ૦૫
