

GUJARAT TECHNOLOGICAL UNIVERSITY**Diploma - Semester-VI- Regular Examination May 2011****Subject code:361702****Subject Name: Industrial Electronics and Control****Date:19/05/2011****Time : 2:30 pm to 5:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is Authentic

- | | | |
|-------------|---|-----------|
| Q.1 | (a) With respect to SCRs define (1) Latching current (2) Holding current (3) Turn on time (4) Turn off time | 04 |
| | (b) Draw V-I characteristics of UJT, explain it with ckt. diagram . | 05 |
| | (c) Draw V-I characteristics of DIAC, explain it with ckt. diagram. | 05 |
| Q.2 | (a) Enlist commutation methods of SCR, Explain class-D method. | 07 |
| | (b) Discuss two transistor model of SCR, derive its anode current equation. | 07 |
| | OR | |
| | (b) Draw and explain SCR snubber circuit. | 07 |
| Q.3 | (a) What is inverter? Draw and explain basic series inverter. | 07 |
| | (b) Compare power MOSFET and BJT. | 07 |
| | OR | |
| Q.3 | (a) Explain microprocessor based firing circuit for single phase semiconverter. | 07 |
| | (b) What is cycloconverter? Explain single phase to single phase step down cycloconverter. | 07 |
| Q.4 | (a) List turn-on methods of SCRs, Explain gate triggering method . | 07 |
| | (b) Draw and explain driver circuit of MOSFET. | 07 |
| | OR | |
| Q. 4 | (a) Explain working of capacitor energy storage welding ,write its application. | 07 |
| | (b) Explain speed control of D.C. motor using tachogenerator feedback method. | 07 |
| Q.5 | (a) Describe the different types of resistance welding with neat diagram. | 07 |
| | (b) Discuss operation of single phase dualconverter with the help of circuit diagram and waveforms. | 07 |
| | OR | |
| Q.5 | (a) Explain A.C. motor control with Diac and Triac. | 07 |
| | (b) What is duty cycle? Explain step down chopper. | 07 |

પ્રશ્ન-૧	અ	વ્યાખ્યા આપો (1) લેચીંગ પ્રવાહ (2) હોલ્ડીંગ પ્રવાહ (3) ટર્ન ઓન સમય (4) ટર્ન ઓફ સમય	04
	બ	યુજેટીની વોલ્ટેજ-પ્રવાહ ની લાક્ષણિકતા દોરો, પરીપથની મદદથી સમજાવો.	05
	ક	ડાયકની વોલ્ટેજ-પ્રવાહ ની લાક્ષણિકતા દોરો, પરીપથની મદદથી સમજાવો.	05
પ્રશ્ન-૨	અ	એસ.સી.આર. ને ટર્ન ઓફ કરવાની પદ્ધતિના નામ લખો. ક્લાસ ડી પદ્ધતિ પરીપથની મદદથી સમજાવો.	07
	બ	એસ.સી.આર.નું બે ટ્રાન્ઝિસ્ટર મોડેલ સમજાવો, તેના એનોડ પ્રવાહ નું સુત્ર તારવો.	07
		અથવા	
	બ	એસ.સી.આર. સ્તબ્ધ પરીપથની મદદથી સમજાવો.	07
પ્રશ્ન-૩	અ	ઈનવર્ટર એટલે શું ? શ્રેણી ઈનવર્ટર પરીપથની મદદથી સમજાવો.	07
	બ	પાવર મોસફેટ અને બીજેટી ની સરખામણી કરો.	07
		અથવા	
પ્રશ્ન-૩	અ	સીંગલ ફેઝ સેમીકન્વર્ટર ની માઈક્રોપ્રોસેસર ની મદદથી ફાયરીંગ મેથડ પરીપથ દોરી સમજાવો	07
	બ	સાયકલોકનવર્ટર એટલે શું ? સીંગલ ફેઝ થી સીંગલ ફેઝ સ્ટેપ ડાઉન સાયકલોકનવર્ટર સમજાવો.	07
પ્રશ્ન-૪	અ	એસ.સી.આર. ને ટર્ન ઓન કરવાની પદ્ધતિના નામ લખો,ગેટ ટર્ન ઓન પદ્ધતિ સમજાવો.	07
	બ	મોસફેટ ડ્રાઈવર પરીપથ દોરી સમજાવો.	07
		અથવા	
પ્રશ્ન-૪	અ	કેપેસિટર એનર્જી સ્ટોરેજ વેલ્ડીંગ આકૃતિ દોરી સમજાવો, તેની ઉપયોગીતા લખો.	07
	બ	ડી.સી. મોટર કન્ટ્રોલ ટેકોજનેરટર ફીડબેક પદ્ધતિથી સમજાવો.	07
પ્રશ્ન-૫	અ	રેઝીસ્ટનસ વેલ્ડીંગની વિવિધ પદ્ધતિઓ આકૃતિ દોરી સમજાવો.	07
	બ	સીંગલ ફેઝ ડ્યુલ કનવર્ટર આકૃતિ અને વેવફોર્મ દોરી સમજાવો.	07
		અથવા	
પ્રશ્ન-૫	અ	એ.સી. મોટર કન્ટ્રોલ ડાયક અને ટ્રાયકની મદદથી સમજાવો.	07
	બ	ડ્યુટી સાયકલ એટલે શું ? સ્ટેપ ડાઉન ચોપર આકૃતિ દોરી સમજાવો.	07
