

GUJARAT TECHNOLOGICAL UNIVERSITY**Diploma Engineering - SEMESTER-II • EXAMINATION – SUMMER 2013****Subject Code: 3320903****Date: 04-06-2013****Subject Name: D.C. Circuits****Time: 10:30 am - 01:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make Suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Use of programmable & Communication aids are strictly prohibited.
5. Use of only simple calculator is permitted in Mathematics.
6. English version is authentic.

- Q.1** Answer any seven out of ten. **14**
1. Define work & power.
 2. State Ohm's law.
 3. Three resistors 1Ω , 2Ω & 3Ω are connected in series across a 20V battery. Find equivalent resistance and current.
 4. State Kirchhoff's current law.
 5. State Reciprocity theorem.
 6. Write types of capacitor.
 7. Write the factors affecting the value of capacitor.
 8. Write equation of statically induced emf and dynamically induced emf.
 9. State Fleming's right hand rule.
 10. A coil of 600 turns produces flux of 2 mWb when it carries a current of 4A. Calculate the co-efficient of self inductance of the coil.
- Q.2** (a) Give any three name of materials used in insulators, conductors and semi-conductors each. **03**
- OR
- (a) Write effect of temperature on resistance. **03**
- (b) A length of wire has a resistance of 1.5Ω . Find the resistance of another wire of the same material, twice in length and three times big in cross-sectional area. **03**
- OR
- (b) Resistance of a conductor is 25Ω at 20°C . Its resistance becomes 27.95Ω when its temperature is raised by 30°C . Find the resistance temperature co-efficient of the conductor at 20°C . **03**
- (c) Calculate the current supplied by battery B_1 of fig. 2 using Maxwell loop current method. **04**
- OR
- (c) Using Nodal voltage analysis, determine the currents supplied by each battery of fig. 4. **04**
- (d) Three resistors of 10Ω , 20Ω & 40Ω are connected in parallel, which draw a current of 5A from the supply mains. Calculate (i) supply voltage, (ii) current flowing through each resistor. **04**
- OR
- (d) Calculate the current through each resistor for figure 3. **04**
- Q.3** (a) Find the equivalent capacitance of the circuit shown in figure 8. **03**
- OR

- (a) $2\mu\text{F}$, $4\mu\text{F}$ & $6\mu\text{F}$ capacitors are connected in series across 220V supply. Find net capacitance and charge across each capacitor. **03**
- (b) Obtain the equation for the energy stored in a capacitor. **03**
- OR
- (b) Derive the equation for charging of capacitor. **03**
- (c) Obtain the equation of coupling co-efficient $K=M/\sqrt{L_1L_2}$ between the two coils. **04**
- OR
- (c) Obtain the equation of equivalent inductance $L = L_1+L_2-2M$ when two inductors are connected in series oppositions. **04**
- (d) Resistance of an inductive coil is 100Ω . It is wound on a non-magnetic former having 1m length & 20 sq. cm. cross sectional area. There are 1600 turns in the coil. Find (i) inductance of the coil, (ii) energy stored when uniform current of 10A flows through it. **04**
- OR
- (d) A dc supply of 240V is given to a coil having resistance of 16Ω & inductance of 24H. Calculate the current at 0.3 second after the supply is given. **04**
- Q.4** (a) For the network shown in fig. 1, write the numbers of nodes, branches, loop, mesh, active elements and passive elements. **03**
- OR
- (a) For the two figures shown in fig.5, calculate the resultant value of emf. **03**
- (b) For the circuit of fig.6, obtain current through 2Ω load resistor using Norton's theorem. **04**
- OR
- (b) Find current in resistor R_3 of the network shown in fig.1 using Thevenin's theorem. **04**
- (c) Using Super position theorem, calculate current flowing through resistance R_2 in the circuit shown in fig.7. **07**
- Q.5** (a) State and explain Joule's law. **04**
- (b) A 1kW heater is used on 230V supply. Find the time taken to raise the temperature of water from 15°C to 85°C . Water equivalent of heater is 0.12kg and efficiency is 85%. **04**
- (c) Write Faraday's laws of Electromagnetic Induction. **03**
- (d) Give the difference between emf and potential difference. **03**

- પ્રશ્ન. ૧** દશમાંથી કોઇપણ સાતના જવાબ આપો. **૧૪**
૧. વર્ક અને પાવરની વ્યાખ્યા આપો.
 ૨. ઓહ્મનો નિયમ જણાવો.
 ૩. 1Ω , 2Ω અને 3Ω ના પ્રતિરોધકોને શ્રેણીમાં જોડીને તેને 20V ના વીજદબાણ સાથે જોડવામાં આવે તો તેનો સમતુલ્ય પ્રતિરોધ તથા તેમાંથી પસાર થતા વિજપ્રવાહનું મૂલ્ય શોધો.
 ૪. કિર્ચોફનો કરંટનો નિયમ જણાવો.
 ૫. રેસિપ્રોસીટી થિયરમ જણાવો.
 ૬. કેપેસિટરના પ્રકાર જણાવો.
 ૭. કેપેસિટરના મૂલ્યને અસર કરતા પરીબળો લખો.

૮. સ્ટેટીકલી ઈંડ્યુસ્ ઈએમએફ અને ડાયનેમીકલી ઈંડ્યુસ્ ઈએમએફના સુત્રો લખો.
૯. ફ્લેમીંગનો જમણા હાથનો નીચમ જણાવો.
- ૧૦ 600 આંટાવાળી એક કોઈલમાંથી 4A નો પ્રવાહ પસાર કરવાથી 2mWb નો ફ્લક્સ ઉત્પન્ન થાય છે તો કોઈલના સેલ્ફ ઈન્ડકશનનો આંક શોધો.
- પ્રશ્ન. ૨ અ અવાહક, વાહક અને અર્ધવાહક તરીકે વપરાતા પદાર્થના દરેક ના ત્રણ નામ લખો. 03
- અથવા
- અ ઉષ્ણતામાનની અવરોધ પર થતી અસર લખો. 03
- બ એકમ લંબાઈ ધરાવતા વાયરનો પ્રતિરોધ 1.5Ω છે. તેના કરતા બે ગણી લંબાઈ, ત્રણ ગણો આડછેડનો ક્ષેત્રફળ અને સરખું મટીરીયલ ધરાવતા વાયરનો પ્રતિરોધ શોધો. 03
- અથવા
- બ 20°C ઉષ્ણતામાને વાહકનો પ્રતિરોધ 25Ω છે. જ્યારે વાહકનું ઉષ્ણતામાન 30°C જેટલું વધારવામાં આવે છે ત્યારે તેનો પ્રતિરોધ 27.95Ω થાય છે તો વાહકનો 20°C ઉષ્ણતામાને રેઝીસ્ટન્સ ટેમ્પરેચર કો-એફીશીયન્ટ શોધો. 03
- ક આકૃતિ 2 માં દર્શાવેલ પરીપથમાં બેટરી B1 માંથી અપાતા પ્રવાહની કિંમત મેક્સવેલ લુપ કરંટ પદ્ધતિથી શોધો. 04
- અથવા
- ક આકૃતિ 4 માં બતાવેલ પરીપથમાં દરેક બેટરી દ્વારા આપવામાં આવતા પ્રવાહની ગણતરી નોડલ વોલ્ટેજ એનાલીસીસની મદદથી કરો. 04
- ડ 10Ω , 20Ω અને 40Ω ના ત્રણ પ્રતિરોધકોને સમાંતરમાં જોડેલ છે. કુલ પ્રવાહ સપ્લાયમાંથી 5A હોય તો (1) સપ્લાય વોલ્ટેજ (2) દરેક પ્રતિરોધમાંથી પસાર થતા પ્રવાહની ગણતરી કરો. 04
- અથવા
- ડ આકૃતિ 4 માં બતાવેલ દરેક પ્રતિરોધમાંથી પસાર થતા પ્રવાહની ગણતરી કરો. 04
- પ્રશ્ન. 3 અ આકૃતિ 8 માં બતાવેલ પરીપથના સમતુલ્ય કેપેસિટન્સની ગણતરી કરો. 03
- અથવા
- અ $2\mu\text{F}$, $4\mu\text{F}$ અને $6\mu\text{F}$ ના મૂલ્યના કેપેસિટરને શ્રેણીમાં જોડી 220V નો સપ્લાય આપવામાં આવે છે તો પરીપથનો સમતુલ્ય કેપેસિટન્સ તથા દરેક કેપેસિટર પરનો ચાર્જ શોધો. 03
- બ કેપેસિટરમાં સંગ્રહીત એનર્જીનું સૂત્ર મેળવો. 03
- અથવા

	બ	કેપેસિટરના ચાર્જીંગ માટેનું સૂત્ર મેળવો.	03
	ક	બે ગૂંચળાઓ વચ્ચેના કપલીંગ કો-એફીશીયન્ટ $K=M/\sqrt{L_1L_2}$ નું સૂત્ર મેળવો.	04
		અથવા	
	ક	બાજુ-બાજુમાં મૂકેલ બે ગૂંચળાઓને સીરીઝ ઓપોઝીશનમાં જોડવામાં આવે ત્યારે સમતુલ્ય ઈન્ડક્ટેન્સ $L = L_1 + L_2 - 2M$ નું સૂત્ર મેળવો.	04
	ડ	એક પ્રેરણ ગૂંચળાનો અવરોધ 100Ω છે અને તે ચુંબકીય ન હોય તેવા $1m$ લાંબા અને 20 sq.cm. ના આડછેદના ક્ષેત્રફળવાળા ફરમા ઉપર 1600 આંટા લપેટીને બનાવેલ છે, તો ગૂંચળાની (1) પ્રેરકતા શોધો. (2) તેમાંથી $10A$ નો એક સરખો વીજ પ્રવાહ વહેતો હોય તો તે સમયની તેમાં સંગ્રહાયેલી કાર્યશક્તિ ની ગણતરી કરો.	04
		અથવા	
	ડ	16Ω નો પ્રતિરોધ અને $24H$ પ્રેરકતા ધરાવતા ગૂંચળાને $240V$ ડી.સી. આપવામાં આવે છે. સપ્લાય ચાલુ કર્યા પછી 0.3 સેકન્ડે વીજપ્રવાહની ગણતરી કરો.	04
પ્રશ્ન. ૪	અ	આકૃતિ 1 માં બતાવેલ પરીપથ માટે નોડ, બ્રાંચ, લુપ, મેશ, એક્ટિવ એલીમેન્ટ, પેસીવ એલીમેન્ટમની સંખ્યા ગણી લખો.	03
		અથવા	
	અ	આકૃતિ 5 માં બતાવેલ બન્ને પરીપથ માટે પરીણામી ઈએમએફની ગણતરી કરો.	03
	બ	આકૃતિ 6 માં બતાવેલ પરીપથમાં 2Ω ના લોડ પ્રતિરોધમાંથી પસાર થતા પ્રવાહની ગણતરી નોર્ટન થિયરમની મદદથી કરો.	04
		અથવા	
	બ	આકૃતિ 1 માં બતાવેલ પરીપથમાં પ્રતિરોધ R_3 માંથી પસાર થતા પ્રવાહની ગણતરી થેવેનીન થિયરમની મદદથી કરો.	04
	ક	આકૃતિ 7 માં બતાવેલ પરીપથ માટે પ્રતિરોધ R_2 માંથી પસાર થતા પ્રવાહની ગણતરી સુપર પોઝીશન થિયરમની મદદથી કરો.	09
પ્રશ્ન. ૫	અ	જૂલનો નિયમ લખો અને સમજાવો.	04
	બ	$1kW$ નું હીટર $230V$ સપ્લાય પર વાપરવામાં આવે છે. 5 લીટર પાણીનું ઉષ્ણતામાન $15^\circ C$ થી $85^\circ C$ સુધી લઈ જવા માટે કેટલો સમય લાગશે તે શોધો. હીટરનો વોટર ઈફીએન્સી $0.12kg$ છે અને કાર્યદક્ષતા 85% છે.	04
	ક	ફેરાડેના ઇલેક્ટ્રોમેગ્નેટીક ઈન્ડક્શનના નિયમો લખો.	03
	ડ	ઈએમએફ અને પોટેન્શિયલ ડિફરન્સ વચ્ચેનો તફાવત લખો.	03

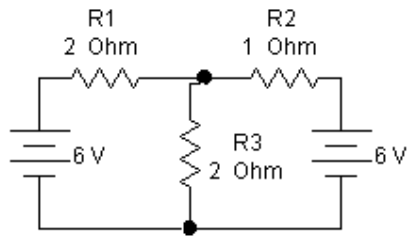


Figure 1

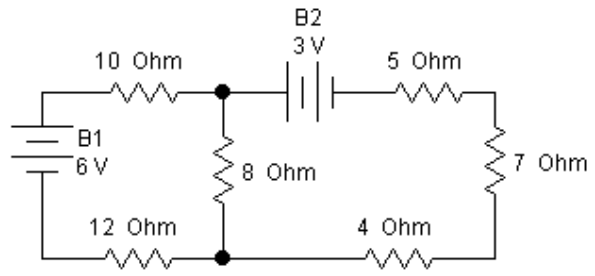


Figure 2

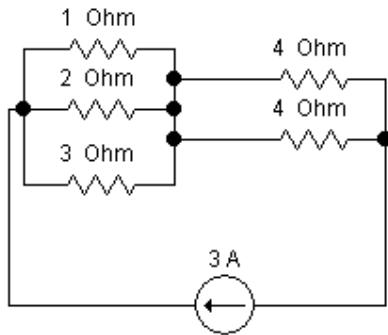


Figure 3

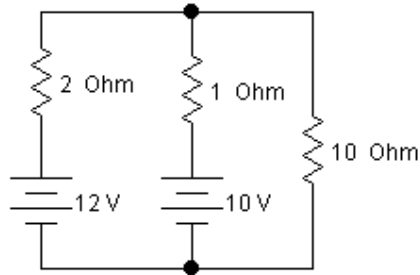


Figure 4

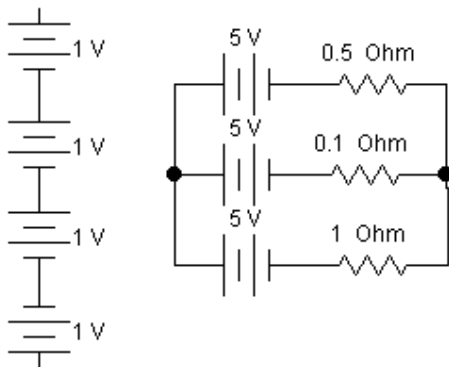


Figure 5

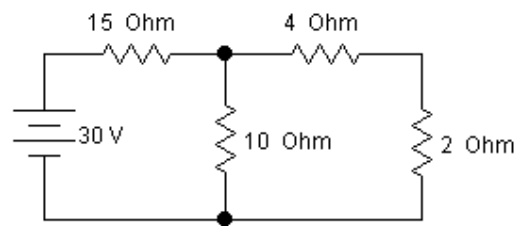


Figure 6

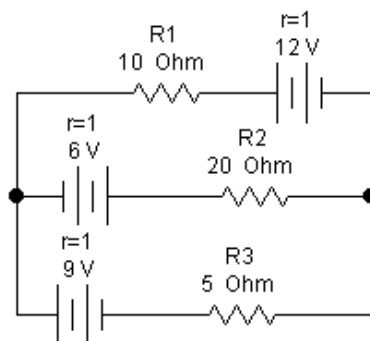


Figure 7

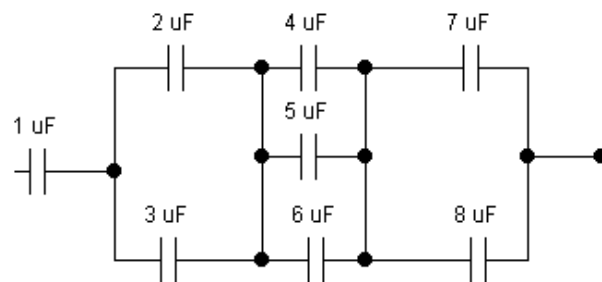


Figure 8