

**GUJARAT TECHNOLOGICAL UNIVERSITY****Diploma Engineering - SEMESTER-II • EXAMINATION – SUMMER 2013****Subject Code: 3322401****Date: 04-06-2013****Subject Name: Basic Electronic Circuits****Time: 10:30 am - 01:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make Suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Use of programmable & Communication aids are strictly prohibited.
5. Use of only simple calculator is permitted in Mathematics.
6. English version is authentic.

- Q.1** Answer any seven out of ten. **14**
1. What is typically the approximate barrier potential for a silicon P-N junction?
  2. When forward biased, a zener acts like what kind of diode?
  3. Give the difference between an LED schematic symbol and that of a regular diode.
  4. Define Light Emitting Diode (LED).
  5. State the direction of current flow in P-N diode.
  6. Give the approximate value of ripple factor of a half-wave rectifier without filter.
  7. State two applications of H- parameter.
  8. Give the types of biasing for PN junction.
  9. Give the symbol and structure of schottky diode.
  10. List any four Applications of transistor.
- Q.2** (a) Draw symbol, construction and characteristics of P-N junction diode. **03**
- OR
- (a) Draw full wave rectifier circuit with input-output voltage waveform. **03**
- (b) Define working principle of photo diode. Draw symbol of photo diode. **03**
- OR
- (b) Define working principle of photo transistor and draw symbol of it. **03**
- (c) Give two points in comparison of schottky diode with conventional diode. **04**
- OR
- (c) Define zener break down. And draw VI characteristics of zener diode **04**
- (d) Give working principle of LDR. Write two applications of LDR. **04**
- OR
- (d) Draw symbol of optocoupler. Why it is needed? Give any two application. **04**
- Q.3** (a) State the most commonly used transistor configuration. And give two reasons for that. **03**
- OR
- (a) Define hybrid parameters. Write the voltage and current equation for hybrid parameters **03**
- (b) Draw voltage divider bias circuit for CE amplifier. **03**
- OR
- (b) Draw fixed bias circuit for CE amplifier. **03**
- (c) Draw symbol, construction of NPN & PNP transistor. **04**
- OR
- (c) Draw CC configuration of a transistor with its output characteristics. **04**
- (d) Give two point in Comparison of CE – CB Configuration. **04**

|     |                                                                                                                                                 |    |
|-----|-------------------------------------------------------------------------------------------------------------------------------------------------|----|
|     | OR                                                                                                                                              |    |
|     | (d) Give two point in Comparison of CE – CC Configuration.                                                                                      | 04 |
| Q.4 | (a) Give two Advantage and disadvantages of fixed bias circuit.                                                                                 | 03 |
|     | OR                                                                                                                                              |    |
|     | (a) Define heat sink. Write materials used for heat sink.                                                                                       | 03 |
|     | (b) State condition for thermal stability. Define thermal runaway.                                                                              | 04 |
|     | OR                                                                                                                                              |    |
|     | (b) For a certain BJT, $\beta=50$ ; $I_{CEO}=3\mu A$ , and $I_C=1.2$ mA. Find $I_B$ and $I_E$ .                                                 | 04 |
|     | (c) Define load line. Give reason to fix the operating point in the middle of the DC load line. Draw CE amplifier input-output characteristics. | 07 |
| Q.5 | (a) Compare L filter and C filter. Give two points for each.                                                                                    | 04 |
|     | (b) Differentiate series and shunt voltage regulator.                                                                                           | 04 |
|     | (c) Give two limitations of using zener diode regulator.                                                                                        | 03 |
|     | (d) Define filter. Write need of filter.                                                                                                        | 03 |

\*\*\*\*\*

|           |                                                                               |    |
|-----------|-------------------------------------------------------------------------------|----|
| પ્રશ્ન. ૧ | દશમાંથી કોઇપણ સાતના જવાબ આપો.                                                 | ૧૪ |
| ૧.        | P-N જંક્શન માટે નો અંદાજિત બેરીયર પોટેન્શીયલ કેટલો હોય છે?                    |    |
| ૨.        | જ્યારે ઝેનર ફોરવર્ડ બાયસ મા હોય ત્યારે તે કેવા પ્રકાર ના ડાયોડ તરીકે કામ કરે? |    |
| ૩.        | LED અને જનરલ ડાયોડ ના સિમ્બોલ વચ્ચે નો તફાવત આપો.                             |    |
| ૪.        | LED ની વ્યાખ્યા આપો.                                                          |    |
| ૫.        | P-N ડાયોડ મા કરંટ કઈ દિશામા ફલો થાય?                                          |    |
| ૬.        | ફિલ્ટર વગરના હાફ-વેવ રેક્ટીફાયર માટે રીપલ ફેક્ટર ની અંદાજિત કિંમત આપો.        |    |
| ૭.        | H- પેરામીટર ની બે ઉપયોગીતા લખો.                                               |    |
| ૮.        | PN જંક્શન મા આવતા બાયસીંગ ના પ્રકાર લખો.                                      |    |
| ૯.        | Schottky ડાયોડ નો સિમ્બોલ અને બંધારણ દોરો.                                    |    |
| ૧૦        | ટ્રાંઝીસ્ટર ની ચાર ઉપયોગીતા જણાવો.                                            |    |
| પ્રશ્ન. ૨ | અ P-N જંક્શન ડાયોડ નો સિમ્બોલ, બંધારણ અને લાક્ષણિકતા દોરો.                    | ૦૩ |
|           | અથવા                                                                          |    |
| અ         | કુલ વેવ રેક્ટીફાયર સરકીટ તેના ઇનપુટ-આઉટપુટ વેવફોર્મ સાથે દોરો.                | ૦૩ |
| બ         | ફોટો ડાયોડ નો કાર્યકારી સિધ્ધાંત વ્યાખ્યાયીત કરો અને તેનો સિમ્બોલ દોરો.       | ૦૩ |
|           | અથવા                                                                          |    |
| બ         | ફોટો ટ્રાંઝીસ્ટર નો કાર્યકારી સિધ્ધાંત વ્યાખ્યાયીત કરો અને તેનો સિમ્બોલ દોરો. | ૦૩ |
| ક         | Schottky ડાયોડ અને જનરલ ડાયોડ વચ્ચે સરખામણી ના બે મુદ્દા આપો.                 | ૦૪ |
|           | અથવા                                                                          |    |
| ક         | ઝેનર બ્રેકડાઉન ની વ્યાખ્યા આપો. અને તેની VI લાક્ષણિકતા દોરો.                  | ૦૪ |

|           |   |                                                                                                                                           |    |
|-----------|---|-------------------------------------------------------------------------------------------------------------------------------------------|----|
|           | ડ | LDR નો કાર્યકારી સિધ્ધાંત વ્યાખ્યાયીત કરો અને તેની બે ઉપયોગીતા લખો.                                                                       | 0૪ |
|           |   | અથવા                                                                                                                                      |    |
|           | ડ | ઓપ્ટો-કપલર નો સિમ્બોલ દોરો. અને તે શા માટે જરૂર છે? તેની બે ઉપયોગીતા લખો.                                                                 | 0૪ |
| પ્રશ્ન. ૩ | અ | ટ્રાંઝીસ્ટર ની મોટેભાગે ઉપયોગ માં આવતી રચના જણાવો. અને તેના બે કારણો આપો.                                                                 | 0૩ |
|           |   | અથવા                                                                                                                                      |    |
|           | અ | હાઈબ્રીડ પેરા મીટર ની વ્યાખ્યા આપો. તથા હાઈબ્રીડ પેરા મીટર માટે ના વોલ્ટેજ અને કરંટ ના સુત્રો લખો.                                        | 0૩ |
|           | બ | CE એમ્પ્લીફાયર માટે વોલ્ટેજ ડીવાયડર બાયસ સર્કીટ દોરો.                                                                                     | 0૩ |
|           |   | અથવા                                                                                                                                      |    |
|           | બ | CE એમ્પ્લીફાયર માટે ફીક્સ બાયસ સર્કીટ દોરો.                                                                                               | 0૩ |
|           | ક | NPN અને PNP ટ્રાંઝીસ્ટર ના સિમ્બોલ અને બંધારણ દોરો.                                                                                       | 0૪ |
|           |   | અથવા                                                                                                                                      |    |
|           | ક | CC એમ્પ્લીફાયર ની રચના તેની આઉટપુટ લાક્ષણીકતા સાથે દોરો.                                                                                  | 0૪ |
|           | ડ | CE – CB રચના ની સરખામણી મા બે મુદ્દા આપો.                                                                                                 | 0૪ |
|           |   | અથવા                                                                                                                                      |    |
|           | ડ | CE – CC રચના ની સરખામણી મા બે મુદ્દા આપો.                                                                                                 | 0૪ |
| પ્રશ્ન. ૪ | અ | ફીક્સ બાયસ સર્કીટ ના બે ફાયદા અને ગેરફાયદા આપો.                                                                                           | 0૩ |
|           |   | અથવા                                                                                                                                      |    |
|           | અ | હીટસિંક ની વ્યાખ્યા આપો. તેના માટે ઉપયોગમાં આવતા મટીરીયલ ના નામ લખો.                                                                      | 0૩ |
|           | બ | થર્મલ સ્ટેબીલિટી માટેની શરત લખો. થર્મલ રનઅવે ની વ્યાખ્યા આપો.                                                                             | 0૪ |
|           |   | અથવા                                                                                                                                      |    |
|           | બ | એક BJT, માટે $\beta=50$ ; $I_{CEO}=3\mu A$ , and $I_C=1.2 mA$ છે. તો $I_B$ અને $I_E$ શોધો.                                                | 0૪ |
|           | ક | લોડ લાઈન ની વ્યાખ્યા આપો. ડીસી. લોડ લાઈન ની વચ્ચે ઓપરેટીંગ પોઈન્ટ રાખવા માટે નુ કારણ આપો. CE એમ્પ્લીફાયર ની ઇનપુટ-આઉટપુટ લાક્ષણીકતા દોરો. | 0૭ |
| પ્રશ્ન. ૫ | અ | L અને C ફિલ્ટર ની સરખામણી કરો. દરેક ના બે મુદ્દા આપો.                                                                                     | 0૪ |
|           | બ | સીરીઝ અને શંટ રેગ્યુલેટર ની સરખામણી કરો.                                                                                                  | 0૪ |
|           | ક | ઝેનર ડાયોડ ના રેગ્યુલેટર ના બે ગેરફાયદા લખો.                                                                                              | 0૩ |
|           | ડ | ફિલ્ટર ની વ્યાખ્યા આપો. અને ફિલ્ટર ની જરૂરિયાત લખો.                                                                                       | 0૩ |

\*\*\*\*\*