

GUJARAT TECHNOLOGICAL UNIVERSITY
Diploma – SEMESTER - I • EXAMINATION – WINTER 2012

Subject code: 3310702**Date: 17/01/2013****Subject Name: Fundamental of Digital Electronics****Time: 10:30 am – 01:00 pm****Total Marks: 70****Instructions:**

1. Make suitable assumptions wherever necessary.
2. Figures to the right indicate full marks.
3. Each question carry equal marks (14 marks)
4. English version is authentic.

- Q.1** Answer any Seven questions only. All questions are of 2 marks each **14**
- (a) Briefly explain reflected code
 - (b) Draw only symbols of following logic gates.
 (i) AND (ii) OR (iii) NOT (iv) NAND
 - (c) Draw K-Map for 3 variables.
 - (d) Draw logic circuit for following expression $F = AB' + A'C$.
 - (e) Convert $(412)_{10}$ decimal number in to binary number.
 - (f) Convert $(2AF)_{16}$ hexa-decimal number in to decimal number.
 - (g) (i) $A+BC =$ _____, (ii) $(A+B)' =$ _____.
 - (h) Write truth table for $f(A,B) = A \oplus B$
 - (i) Perform (i) $11011 + 01011$ (ii) $11010 - 01101$
 - (j) Which combinational circuit can be used to divide data from 1 input line to 4 output line? Also draw block diagram of it.
- Q.2** (a) Briefly explain error detection code. Write down a table of 0 to 7 decimal numbers in to binary form and mentioning odd and even parity for all numbers. **4**
- OR
- (a) If (i) 2's complement of a binary number is 0111, obtain original number. **4**
 (ii) 10's complement of decimal number is 625, obtain original number.
- (b) Apply De-Morgan's theorem to following expressions. **5**
 (i) $[(A+B')(C'+D)]'$ (ii) $[A(B+C)]'$
- OR
- (b) (i) List any four properties of Boolean algebra and prove any one. **5**
 (ii) Reduce expression using Boolean algebra
 $X'Y'Z' + X'YZ' + XY'Z' + XYZ'$
- (c) Obtain simplified SOP expression using K-Map method for $\Sigma(0,1,3,4,5,6,11,14)$ and implement using NAND logic. **5**
- OR
- (c) Obtain simplified POS expression using K-Map method for $\prod(3, 4, 6, 7, 11, 12, 14, 15)$ and implement using NOR logic. **5**
- Q.3** (a) What is the difference between half and full Subtractor? Design half subtractor circuit. **5**

OR

	(a) What is the difference between half adder and full adder? Design half adder circuit.	5
	(b) With proper diagram explain 4-bit binary parallel adder. Also draw pin diagram of IC used as 4-bit parallel adder.	5
	OR	
	(b) With proper diagram explain 4-bit binary parallel subtractor. Also draw pin diagram of IC used as 4-bit parallel subtractor.	5
	(c) Define universal gate. Derive basic logic gates (AND-OR-NOT) using NOR gate.	4
	OR	4
	(c) Define universal gate. Derive basic logic gates (AND-OR-NOT) using NAND gate.	
Q.4	(a) For 0 to 9 decimal numbers write down table of corresponding BCD and Excess-3 code.	3
	OR	
	(a) Briefly explain the steps of combinational logic design with a simple example.	3
	(b) Write short note on don't care conditions. Explain with suitable example.	4
	OR	
	(b) With suitable example explain canonical or standard forms.	4
	(c) Explain magnitude comparator with the help of block diagram and Derive 2 bit magnitude comparator circuit using truth table.	7
Q.5	(a) What is decoder? Derive logic circuit for 2 to 4 decoder.	4
	(b) What is Multiplexer? Derive 4 to 1 Multiplexer circuit.	4
	(c) Prove that	6
	(i) $C'D' + A'B'D' + A'BCD' + ACD' = D'$	
	(ii) $AB'C + B + BD' + ABD' + A'C = B + C$	

પ્રશ્ન-૧	ફક્ત કોઈ પણ સાત પ્રશ્નો નાં જવાબ આપો. બધા પ્રશ્નો ૨ ગુણનાં છે. (૧) ટુંકમાં રીફલેક્ટેડ કોડ સમજાવો (૨) નીચેના ગેટના ફક્ત સીમ્બોલ દોરો (i) AND (ii) OR (iii) NOT (iv) NAND (૩) ત્રણ વેરીએબલ માટેનો K-Map દોરો (૪) આપેલ સમીકરણ $F=AB'+A'C$ માટે લોજિક સર્કીટ દોરો (૫) $(412)_{10}$ દશાંશ સંખ્યાને બાયનરીમાં રૂપાંતર કરો. (૬) $(2AF)_{16}$ Hex સંખ્યાને દશાંશ પધ્ધતી માં રૂપાંતર કરો. (૭) $A+BC = \underline{\hspace{2cm}}$, (ii) $(A+B)' = \underline{\hspace{2cm}}$. (૮) $f(A,B) = A \oplus B$ માટે ટ્રુથટેબલ લખો. (૯) ગણતરી કરો (i) $11011 + 01011$ (ii) $11010 - 01101$ (૧૦) ૧ ઈનપુટ લાઈન ને ૪ આઉટપુટ લાઈનમાં વિભાજન કરવા કઈ કોમ્બીનેશનલ સર્કીટનો ઉપયોગ થાય? તેનો block diagram દોરો.	14
પ્રશ્ન-૨	અ Error Detection કોડ ટુંકમાં સમજાવો. 0 to 7 સુધીની સંખ્યાને બાયનરી માં રૂપાંતર કરો અને તેની સામે Odd અને Even પેરીટી લખો. અથવા અ જો (i) એક બાયનરી સંખ્યાનું 2's કોમ્પલીમેન્ટ 0111, તો મુળ સંખ્યા મેળવો. (ii) એક દશાંશ સંખ્યાનું 10's કોમ્પલીમેન્ટ 625 છે, તો મુળ સંખ્યા મેળવો. બ નીચેના સમીકરણોને ડી-મોર્ગનનો સિધ્ધાંત લાગુ પાડો (i) $[(A+B')(C'+D)]'$ (ii) $[A(B+C)]'$ અથવા બ (i) બુલીયન આલજેબ્રાની કોઈપણ ચાર પ્રોપર્ટી લખો. તેમાંથી કોઈ એક સાબીત કરો. (ii) બુલીયન આલજેબ્રાની મદદથી સાદુરૂપ આપો. $X'Y'Z'+X'YZ'+XY'Z'+XYZ'$ ક K-Map પધ્ધતીથી સાદુરૂપ આપો $\Sigma(0,1,3,4,5,6,11,14)$ અને તેની NAND ગેટના મદદથી લોજિક સર્કીટ દોરો. અથવા ક K-Map પધ્ધતીથી સાદુરૂપ આપો $\Pi(3,4,6,7,11,12,14,15)$ અને તેની NOR ગેટના મદદથી લોજિક સર્કીટ દોરો.	4 4 5 5 5
પ્રશ્ન-૩	અ Half Subtractor અને Full Subtractor વચ્ચે તફાવત સમજાવો. Half Subtractor સર્કીટ ડિઝાઇન કરો. અથવા અ Half Adder અને Full Adder વચ્ચે તફાવત સમજાવો. Half Adder સર્કીટ ડિઝાઇન કરો. બ યોગ્ય આકૃતિની મદદથી 4 Bit Binary Parallel Adder સમજાવો અને 4 Bit Binary Parallel Adder માટે વપરાતી IC 7485 નો પીન ડાયાગ્રામ દોરો. અથવા બ યોગ્ય આકૃતિની મદદથી 4 Bit Binary Parallel Subtractor સમજાવો અને 4 Bit Binary Parallel Subtractor માટે વપરાતી IC 7485 નો પીન ડાયાગ્રામ દોરો. ક Universal gate ની વ્યાખ્યા આપો. NOR gate ની મદદથી બેઝીક લોજિક ગેટ્સ (AND-OR-NOT) મેળવો. અથવા ક Universal gate ની વ્યાખ્યા આપો. NOR gate ની મદદથી બેઝીક લોજિક ગેટ્સ (AND- OR-NOT) મેળવો.	5 5 5 5 4 4

પ્રશ્ન-૪

- અ 0 to 9 સુધીની દશાંશ સંખ્યાઓનું BCD code અને Excess-3 code નું ટેબલ બનાવો. **3**
અથવા
- અ એક સાદા ઊદાહરણથી combinational logic design નાં મુદ્દા સમજાવો. **3**
- બ Don't care conditions વિશે ટુંક નોંધ લખો. યોગ્ય ઊદાહરણથી સમજાવો. **4**
અથવા
- બ યોગ્ય ઊદાહરણી આપી Canonical or Standard forms સમજાવો. **4**
- ક Block diagram ની મદદથી Magnitude comparator સમજાવો અને ટ્રુથટેબલ ની મદદથી 2 bit magnitude comparator સર્કીટ મેળવો. **7**

પ્રશ્ન-૫

- અ Decoder એટલે શું? 2 to 4 decoder સર્કીટ ડીઝાઈન કરો. **4**
- બ Multiplexer એટલે શું? 4 to 1 Multiplexer સર્કીટ ડીઝાઈન કરો. **4**
- ક સાબિત કરો **6**
- (૧) $C'D' + A'B'D' + A'BCD' + ACD' = D'$
- (૨) $AB'C + B + BD' + ABD' + A'C = B+C$
