

GUJARAT TECHNOLOGICAL UNIVERSITY
DIPLOMA ENGG.- SEMESTER-III EXAMINATION – WINTER 2012

Subject code: 331101**Date: 02/01/2013****Subject Name: Electronics Devices and Circuits-II****Time: 2:30 pm – 5:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is Authentic

- | | | |
|-------------|--|-----------|
| Q.1 | (a) What is oscillator ? Explain collpitt oscillator in detail. | 07 |
| | (b) Discuss effect s and advantages of negative feedback. | 07 |
| Q.2 | (a) Give Classification of power amplifier and explain class B push pull amplifier circuit | 07 |
| | (b) Explain different types of Multivibrator | 07 |
| | OR | |
| | (b) Write short note on : Schmitt trigger | 07 |
| Q.3 | (a) Explain RC- phase shift oscillator with help of circuit diagram. | 07 |
| | (b) Explain class A power amplifier with transformer coupled load | 07 |
| | OR | |
| Q.3 | (a) Explain equivalent circuit of crystal and Crystal oscillator . | 07 |
| | (b) Explain class B Complementary symmetry push pull amplifier . | 07 |
| Q.4 | (a) Explain functional block diagram of IC 555. | 06 |
| | (b) Explain OPAMP as summing amplifier | 04 |
| | (c) List various application of OPAMP . | 04 |
| | OR | |
| Q. 4 | (a) List various characteristic of OPAMP and explain OPAMP as Integrator | 06 |
| | (b) Explain OPAMP as non inverting amplifier | 04 |
| | (c) Give compassion between FET and BJT. | 04 |
| | OR | |
| Q.5 | (a) Explain circuit diagram of monostable multivibrator using IC 555 . | 06 |
| | (b) Explain construction, operation and application of enhancement type MOSFET | 08 |
| | OR | |
| Q.5 | (a) Explain block diagram of voltage regulator of IC 723. | 06 |
| | (b) Explain Construction, characteristics and application of IGBT | 08 |

પ્રશ્ન-૧	અ	ઓસીલેટર એટલે શું? કોલપીટ ઓસીલેટર સવિસ્તાર સમજાવો	07
	બ	નેગેટીવ ફીડબેક ની અસરો અને ફાયદા ચર્ચો	07
પ્રશ્ન-૨	અ	પાવર એમ્પ્લીફાયર નુ વર્ગીકરણ આપો અને class B પુશપુલ એમ્પ્લીફાયર સમજાવો.	07
	બ	વિવિધ પ્રકાર ના મલ્ટીવાઇબ્રેટર સમજાવો.	07
	બ	સ્કીમીટ ટ્રીગર વિશે ટુંકનોંધ લખો.	07
પ્રશ્ન-૩	અ	RC ફેજ શિફ્ટ ઓસીલેટર સર્કીટ ડાયાગ્રામ ની મદદ થી સમજાવો.	07
	બ	class A પાવર એમ્પ્લીફાયર ટ્રાંસફોર્મર કપલ્ડ લોડ સાથે સમજાવો.	07
પ્રશ્ન-૩	અ	ક્રીસ્ટલ ની સમકક્ષ સર્કીટ અને ક્રીસ્ટલ ઓસીલેટર સમજાવો.	07
	બ	class B કોમ્પ્લીમેન્ટ્રી સીમેટ્રી પુશપુલ એમ્પ્લીફાયર સમજાવો.	07
પ્રશ્ન-૪	અ	IC 555 નો ફંક્શનલ બ્લોક ડાયાગ્રામ સમજાવો	06
	બ	OPAMP સર્મીંગ એમ્પ્લીફાયર તરીકે સમજાવો	04
	ક	OPAMP ના વિવિધ ઉપયોગોની યાદી આપો	04
પ્રશ્ન-૪	અ	OPAMP ની વિવિધ લાક્ષણિકતા ની યાદી કરો અને OPAMP ઇન્ટીગ્રેટર તરીકે સમજાવો	06
	બ	OPAMP નોન - ઇન્વર્ટીંગ એમ્પ્લીફાયર તરીકે સમજાવો	04
	ક	FET અને BJT ની તુલના આપો..	04
પ્રશ્ન-૫	અ	IC 555 નો ઉપયોગ કરી મોનોસ્ટેબલ મલ્ટીવાઇબ્રેટર નો સર્કીટ ડાયાગ્રામ સમજાવો	06
	બ	એન્હાંસમેન્ટ ટાઇપ MOSFET ની રચના, લાક્ષણિકતા અને ઉપયોગો સમજાવો	08
પ્રશ્ન-૫	અ	IC 723 વોલ્ટેજ રેગ્યુલેટર નો બ્લોક ડાયાગ્રામ સમજાવો	06
	બ	IGBT ની રચના, લાક્ષણિકતા અને ઉપયોગો સમજાવો	08
