

GUJARAT TECHNOLOGICAL UNIVERSITY
DIPLOMA ENGG.- SEMESTER-III EXAMINATION – WINTER 2012

Subject code: 331103**Date: 04/01/2013****Subject Name: Electronic Networks and Lines****Time: 2:30 pm – 5:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is Authentic

- | | | | |
|-------------|-----|---|-----------|
| Q.1 | (a) | Give statement of SUPERPOSITION theorem & Prove it with required equations. | 07 |
| | (b) | Prove THEVENIN theorem using appropriate circuit showing the calculations. | 07 |
| Q.2 | (a) | Explain Kirchhof's law (both). | 07 |
| | (b) | Explain nodal analysis with required equations. | 07 |
| OR | | | |
| | (b) | Explain MUTUAL INDUCTANCE & get the equation for "K". | 07 |
| Q.3 | (a) | Define RESONANCE. Get the resonance frequency equation for a parallel resonance circuit. | 07 |
| | (b) | A series resonance circuit takes a maximum current of 0.2 A at 100 V, 50 Hz., if the voltage across capacitor is 200 V, Calculate for L, R & Q. | 07 |
| OR | | | |
| Q.3 | (a) | Get the equation for characteristics impedance Z_{0T} for a standard 'T' network. | 07 |
| | (b) | Define & get the relation between dB and NEPER. | 07 |
| Q.4 | (a) | Give classification of filters showing frequency response curves For each of them. | 07 |
| | (b) | Design ACTIVE LOW PASS filter & find the cutoff frequency if $R = 10 \text{ ohms}$ & $C = 0.01 \text{ micro farad}$. | 07 |
| OR | | | |
| Q. 4 | (a) | Compare active & passive filters.(any 7 points.) | 07 |
| | (b) | Design m – derived T section Low pass filter if $f_c = 1000 \text{ Hz}$ & very high attenuation at 1065 Hz . Use $R_0 = 500 \text{ ohms}$. | 07 |
| Q.5 | (a) | Explain distortions in a transmission line. | 07 |
| | (b) | Write short note on : SYMMETRICAL T ATTENUATOR. | 07 |
| OR | | | |
| Q.5 | (a) | Explain loading of a telephone cable. | 07 |
| | (b) | Write short note on: PHASE EQUALISER. | 07 |

પ્રશ્ન-૧	અ	સુપરપોઝિશન થિયરમ લખો અને જરૂરી સમીકરણોથી સાબિત કરો.	07
	બ	યોગ્ય સર્કિટ અને જરૂરી ગણતરી વડે થેવેનિન થિયરમ સાબિત કરો.	07
પ્રશ્ન-૨	અ	કિર્યોફના બન્ને નિયમો લખો અને સમજાવો.	07
	બ	જરૂરી સમીકરણોથી નોડલ એનાલિસિસ સમજાવો.	07
પ્રશ્ન-૩	અથવા		
	બ	મ્યુચ્યુઅલ ઇન્ડક્ટન્સ સમજાવો અને “K” નું સમીકરણ મેળવો.	07
પ્રશ્ન-૩	અ	રેઝોનન્સ ની વ્યાખ્યા આપો અને પેરેલલ રેઝોનન્સ માટે રેઝોનન્સ ફ્રિક્વન્સીનું સમીકરણ મેળવો.	07
	બ	એક સિરિઝ રેઝોનન્સ સર્કિટમાં 100 V, 50 Hz., આપવાથી, 0.2 A મહત્તમ પ્રવાહ વહે છે , જો કેપેસિટર વોલ્ટેજ 200 V, હોય તો L , R & Q ની ગણતરી કરો.	07
પ્રશ્ન-૩	અથવા		
	અ	સ્ટાન્ડર્ડ ‘ T ‘ N/W માટે ‘Z _{OT} ’નું સમીકરણ મેળવો.	07
	બ	વ્યાખ્યા આપીને DB અને NEPER વચ્ચેનું સમીકરણ મેળવો.	07
પ્રશ્ન-૪	અ	દરેક પ્રકાર માટે ફ્રિક્વન્સી રિસ્પોન્સની મદદથી ફિલ્ટર નું વર્ગીકરણ સમજાવો.	07
	બ	R= 10 ohms & C = 0.01 micro farad હોય તેવા એક્ટિવ લો પાસ ફિલ્ટરની ડિઝાઇન કરો અને કટ ઓફ ફ્રિક્વન્સી ની ગણતરી કરો.	07
પ્રશ્ન-૪	અથવા		
	અ	એક્ટિવ અને પેસિવ પ્રકારના ફિલ્ટર વચ્ચેનો તફાવત આપો.(ગમે તે સાત મુદ્દા)	07
	બ	f _c =1000 Hz અને ખુબ વધારે એટેન્યુએશન ફ્રિક્વન્સી 1065 Hz તથા. R ₀ = 500 ohms માટે m – derived ટી સેક્શન લો પાસ ફિલ્ટરની ડિઝાઇન કરો.	07
પ્રશ્ન-૫	અ	ટ્રાન્સમીશન લાઇન માટે ડિસ્ટોર્શન સમજાવો.	07
	બ	ટૂંક નોંધ લખો: સિમેટ્રિકલ T એટેન્યુએટર.	07
પ્રશ્ન-૫	અથવા		
	અ	ટેલિફોન ફેબલ માટે લોડિંગ સમજાવો.	07
	બ	ટૂંક નોંધ લખો: ફેઝ ઇક્વલાઇઝર.	07
