

GUJARAT TECHNOLOGICAL UNIVERSITY
Diploma Engineering - SEMESTER – V • EXAMINATION – WINTER 2012

Subject code: 350904**Date: 28/12/2012****Subject Name: Digital Electronics and Digital Instruments****Time: 10.30 am - 01.00 pm****Total Marks: 70****Instructions:**

1. Attempt any five questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is considered to be Authentic.

- Q.1 (a) Answer the following.
- (i) Convert Hexadecimal number $(90BE)_{16}$ to Binary number 02
 - (ii) Subtract $(1101)_2$ from $(0111)_2$ using 2's complement. 02
 - (iii) Convert $(85)_{10}$ in to Excess-3 code. 02
 - (iv) Multiply $(101.10)_2$ and $(1.1)_2$ 02
- (b) Explain Error Correcting Code with example. 06
- Q.2 (a) Explain combined clipper circuit with input and out put wave forms. 07
- (b) Draw and explain 3 input TTL NAND gate circuit. 07
- OR
- (b) List and explain important parameters of digital IC 07
- Q.3 (a) Write De Morgan's theorems and by using that theorem prove that 07
- $$\overline{AB+BC+CA} = \overline{AB} + \overline{BC} + \overline{AC}$$
- (b) 07
- (i) Simplify and implement using NAND gate $Y = (A+B)(\overline{A+B})(\overline{A+B})$
 - (ii) Draw logic circuit for Boolean expression $Y = \overline{(A+B)}. C + \overline{(A+C)}. B$
- OR
- Q.3 (a) Show that Transistor can work as switch. 07
- (b) Draw circuit of edge triggered D flip flop and explain it with truth table. 07
- Q.4 (a) State methods to prevent race around condition and explain JK master slave flip flop with block diagram. 07
- (b) Explain 4 bit serial in serial out shift left register with truth table. 07
- OR
- Q.4 (a) Describe working of 4-bit asynchronous down counter with circuit diagram and sequence table. 07
- (b) Explain octal to binary encoder with circuit diagram and truth table. 07
- Q.5 (a) Explain classification of memory. 07
- (b) Describe construction of LED and find out specification of current limiting resistance used with LED connected to 5V (DC) supply. (Make suitable assumption). 07
- OR
- Q.5 (a) Give advantage and disadvantage of weighted resistor network type D/A converter. 07
- (b) Draw block diagram and explain working of digital frequency meter. 07

પ.૧	અ	નિચેના જવાબ આપો	
	૧	હેક્ઝાડેસીમલ નંબર (90BE) ₁₆ ને બાયનરી નંબરમાં ફેરવો.	૦૨
	૨	2's કોમ્પ્લીમેન્ટની રીતથી (1101) ₂ ને (0111) ₂ માંથી બાદ કરો.	૦૨
	૩	(85) ₁₀ ને Excess-3 કોડમાં ફેરવો.	૦૨
	૪	(101.10) ₂ અને (1.1) ₂ નો ગુણાકાર કરો.	૦૨
	બ	એરર કરેક્ટીંગ કોડ ઉદાહરણ સાથે સમજાવો.	૦૬
પ.૨	અ	કમ્બાઈન ક્લોપર સરકીટ ઈનપુટ અને આઉટપુટ વેવફોર્મ સાથે સમજાવો.	૦૭
	બ	ત્રણ ઈનપુટ TTL NAND ગેટની સરકીટ દોરી સમજાવો.	૦૭
		અથવા	
	બ	ડીજીટલ IC ના અગત્યના પેરામીટર લખી સમજાવો.	૦૭
પ.૩	અ	ડી. મોગ'નના થીયરમ લખો અને તેનો ઉપયોગ કરી સાબિત કરો કે	૦૭
		$\overline{AB+BC+CA} = \overline{AB} + \overline{BC} + \overline{AC}$	
	બ	૧. સાદુરૂપ આપો અને NAND ગેટથી ઈમ્પ્લીમેન્ટ કરો	૦૭
		$Y = (A+B) (\overline{A+B}) (\overline{A+B})$	
		૨. નિચેના બુલીયન એક્સપ્રેસન માટે લોજીક સરકીટ દોરો.	
		$Y = \overline{(A+B)} \cdot C + \overline{(A+C)} \cdot B$	
		અથવા	
પ.૩	અ	ટ્રાંઝિસ્ટર સ્વીચ તરીકે કામ કરી શકે છે તેમ બતાવો.	૦૭
	બ	એજ ટ્રીગડ D ફ્લોપ ફ્લોપની સરકીટ દોરો અને ટ્રુથ ટેબલ સાથે સમજાવો.	૦૭
પ.૪	અ	રેસ એરાઉંડ કંડીશન અટકાવાના ઉપાયો બતાવો અને JK માસ્ટર સ્લેવ ફ્લોપ ફ્લોપ બ્લોકડાયાગ્રામથી સમજાવો.	૦૭
	બ	4 બીટ સીરીયલ ઈન સીરીયલ આઉટ શિફ્ટ લેફ્ટ રજીસ્ટર ટ્રુથ ટેબલ સાથે સમજાવો.	૦૭
		અથવા	
પ.૪	અ	4 બીટ એસીંક્રોનસ ડાઉનકાઉંટરની સરકીટ દોરી ટ્રુથ ટેબલ સાથે વર્ણવો.	૦૭
	બ	ઓક્ટલ ટુ બાયનરી એનકોડર સરકીટ ડાયાગ્રામ અને ટ્રુથ ટેબલ સાથે સમજાવો.	૦૭
પ.૫	અ	મેમરીનું વર્ગીકરણ સમજાવો.	૦૭
	બ	LED ની રચના સમજાવો અને 5V (DC) સપ્લાય સાથે જોડેલ LED સાથે વપરાતા કરંટ લીમીટીંગ અવરોધના સ્પેશીફિકેશન શોધો. (યોગ્ય ધારણા કરો)	૦૭
		અથવા	
પ.૫	અ	વેઈટેડ રજીસ્ટર નેટવર્ક પ્રકારના D/A કન્વર્ટરના ફાયદાઓ તથા ગેરફાયદાઓ આપો.	૦૭
	બ	બ્લોકડાયાગ્રામ દોરી ડીજીટલ ફ્રીક્વેન્સીમીટરનું કાર્ય સમજાવો.	૦૭
