

GUJARAT TECHNOLOGICAL UNIVERSITY**Diploma Engineering - SEMESTER – V • EXAMINATION – WINTER 2012****Subject code: 352403****Date: 27/12/2012****Subject Name: Power Electronics Circuits****Time: 10.30 am - 01.00 pm****Total Marks: 70****Instructions:**

1. Attempt any five questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is considered to be Authentic.

- Q.1** (a) Draw and explain AC to DC half wave uncontrolled converter with necessary waveform for RC load. **07**
(b) Draw and explain single phase AC voltage Controller using RL load with necessary waveform. **07**
- Q.2** (a) Draw and explain electronics Tap changer with necessary waveform. **07**
(b) Draw and explain AC to DC full wave full controlled converter. **07**
- OR**
- (b) Draw and explain AC to DC full wave uncontrolled converter with necessary waveform for RL load. **07**
- Q.3** (a) Explain Single Phase cycloconverter with necessary figure and waveform. **07**
(b) Draw and explain Buck converter with necessary waveform. Also derive equation for the output. **07**
- OR**
- Q.3** (a) Draw various possible schematics for AC chopper Regulator. **07**
(b) Explain resonant pulse commutation of chopper with necessary diagram and waveform. **07**
- Q.4** (a) Draw and Explain CUK converter topology. Derive output equation for the same. **07**
(b) Explain single phase half bridge voltage source inverter with necessary diagrams for RL load. **07**
- OR**
- Q. 4** (a) Explain three phase inverter in 180° conduction mode with necessary waveform. **07**
(b) Explain single phase half bridge voltage source inverter with waveform for RC load. **07**
- Q.5** (a) Draw and explain single phase current source inverter with necessary waveform. **07**
(b) Explain ZCS resonant switch converter with necessary diagram and waveform. **07**
- OR**
- Q.5** (a) Explain ZVS resonant switch converter with necessary diagram and waveform. **07**
(b) Draw schematic diagram of modified McMurray full bridge Inverter. **07**

પ્રશ્ન-૧	અ.	AC થી DC હાફ વેવ અનકંટ્રોલ્ડ કન્વર્ટર જરૂરી વેવફોર્મ સાથે RC લોડ માટે દોરી સમજાવો.	07
	બ.	સિંગલ ફેઝ AC વોલ્ટેજ કંટ્રોલર જરૂરી વેવફોર્મ સાથે RL લોડ માટે દોરી સમજાવો.	07
પ્રશ્ન-૨	અ.	ઇલેક્ટ્રોનિક ટેપ ચેંજર જરૂરી વેવફોર્મ સાથે દોરી સમજાવો.	07
	બ.	AC થી DC કુલ વેવ કુલ કંટ્રોલ્ડ કન્વર્ટર જરૂરી વેવફોર્મ સાથે દોરી સમજાવો.	07
		અથવા	
	બ.	AC થી DC કુલ વેવ અનકંટ્રોલ્ડ કન્વર્ટર જરૂરી વેવફોર્મ સાથે RL લોડ માટે દોરી સમજાવો.	07
પ્રશ્ન-૩	અ.	સિંગલ ફેઝ સાયકલો કન્વર્ટર જરૂરી વેવફોર્મ આકૃતિ સાથે દોરી સમજાવો.	07
	બ.	બક કન્વર્ટર જરૂરી વેવફોર્મ સાથે દોરી સમજાવો. અને આઉટપુટ માટે નુ સુત્ર પણ મેળવો.	07
		અથવા	
પ્રશ્ન-૩	અ.	AC ચોપર રેગ્યુલેટર માટે અલગ અલગ શક્ય ડાયાગ્રામ દોરો.	07
	બ.	ચોપર ના રેસોનન્ટ પ્લસ કોમ્યુટેશન જરૂરી વેવફોર્મ આકૃતિ સાથે દોરી સમજાવો.	07
પ્રશ્ન-૪	અ.	કક કન્વર્ટર ટોપોલોજી દોરી સમજાવો. તથા આઉટપુટ માટે નુ સુત્ર પણ મેળવો.	07
	બ.	સિંગલ ફેઝ હાફ બ્રિજ વોલ્ટેજ સોર્સ ઇન્વર્ટર જરૂરી વેવફોર્મ સાથે RL લોડ માટે દોરી સમજાવો.	07
		અથવા	
પ્રશ્ન-૪	અ.	180° મોડે મા થ્રી ફેઝ ઇન્વર્ટર જરૂરી વેવફોર્મ સાથે દોરી સમજાવો.	07
	બ.	સિંગલ ફેઝ હાફ બ્રિજ વોલ્ટેજ સોર્સ ઇન્વર્ટર જરૂરી વેવફોર્મ સાથે RC લોડ માટે દોરી સમજાવો.	07
પ્રશ્ન-૫	અ.	સિંગલ ફેઝ કરન્ટ સોર્સ ઇન્વર્ટર જરૂરી વેવફોર્મ સાથે દોરી સમજાવો.	07
	બ.	ZCS રેસોનન્ટ સ્વીચ કન્વર્ટર જરૂરી વેવફોર્મ આકૃતિ સાથે દોરી સમજાવો.	07
		અથવા	
પ્રશ્ન-૫	અ.	ZVS રેસોનન્ટ સ્વીચ કન્વર્ટર જરૂરી વેવફોર્મ આકૃતિ સાથે દોરી સમજાવો.	07
	બ.	Modified McMurray કુલ બ્રિજ ઇન્વર્ટર નો ડાયાગ્રામ દોરો.	07
