

GUJARAT TECHNOLOGICAL UNIVERSITY
Diploma Engineering - SEMESTER – V • EXAMINATION – WINTER 2012

Subject code: 352405**Date: 29/12/2012****Subject Name: Power System Protection****Time: 10.30 am - 01.00 pm****Total Marks: 70****Instructions:**

1. Attempt any five questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is considered to be Authentic.

- Q.1 (a) Draw single line diagram of a simple interconnected power system. 07
- (b) For an inrush phenomenon in transformer “derive” $\phi = \phi_r + \left(\frac{V_m}{N\omega}\right) \cos \theta - \left(\frac{V_m}{N\omega}\right) \cos(\omega t + \theta)$ and discuss main factors for inrush phenomenon in brief. 07
- Q.2 (a) Draw equivalent circuit and magnetization characteristics of current transformer (CT). 07
- (b) Draw construction of Buchholz relay and explain its working. 07
- OR**
- (b) List the duties of switchgear and explain anyone in detail. 07
- Q.3 (a) For a three phase Δ -Y transformer, Draw percentage differential relay protection circuit showing phase A-to-ground external fault. 07
- (b) Explain earth leakage protection for single-phase load by supporting circuit diagram. 07
- OR**
- Q.3 (a) For a transmission line explain percentage differential relay along with diagram and operating characteristics. 07
- (b) Draw phasor diagram showing the 30° phase shift between the line voltages of a Y- Δ transformer of three phases transformer along with schematic representation of Y- Δ transformer. 07
- Q.4 (a) Draw transmission line diagram with distance relay protection and explain it in brief. 07
- (b) Draw the structure of reactance relay using the induction cup and explain its working. 07
- OR**
- Q. 4 (a) Explain air break circuit breaker supporting neat sketch. 07
- (b) Write short note on DC circuit breaker. 07
- Q.5 (a) What is current chopping? Discuss in detail. 07
- (b) Draw construction of an induction disc relay and explain its working. 07
- OR**
- Q.5 (a) Write short note on SF6 circuit breaker. 07
- (b) Write short note on instantaneous over current relay. 07

પ્રશ્ન-૧	અ.	સિમ્પલ ઇન્ટરકનેક્ટેડ પાવર સિસ્ટમ માટે એક લાઇન ડાયાગ્રામ દોરો.	07
	બ.	ટ્રાન્સફોર્મર ના ઇનરસ ફિનોમિના માટે $\phi = \phi_r + \left(\frac{V_m}{N\omega}\right) \cos \theta - \left(\frac{V_m}{N\omega}\right) \cos(\omega t + \theta)$ સૂત્ર તાર્વી અને ઇનરસ ફિનોમિના માટે જવાબદાર મુખ્ય પરિબલ વીશે ચર્ચા કરો.	07
પ્રશ્ન-૨	અ.	કરંટ ટ્રાન્સફોર્મર(CT)માટે ઇક્વીવેલેન્ટ સર્કિટ અને મેગ્નેટાઇઝેશન કેરેક્ટરીસ્ટીક દોરો.	07
	બ.	બુકોલ્જ રીલે નૂ કંસટ્રક્શન ડાયાગ્રામ દોરો અને તેનુ વર્ણન કરો.	07
		અથવા	
	બ.	સ્વિચગીયર નિ ડ્યુટી નુ લીસ્ટ બનાવો અને કોઇપણ એક નુ વર્ણન કરો.	07
પ્રશ્ન-૩	અ.	૩-ફેઝ ડેલ્ટા-સ્ટાર ટ્રાંસફોર્મર માટે ફેઝ-એ-થ્રિ-ગ્રાઉંડ (phase A-to-ground) નો એક્સ્ટર્નલ ફોલ્ટ બતાવતી % (પરશંટેજ) ડીફફરનશીયલ પ્રોટેક્શન ની આકૃતિ દોરો.	07
	બ.	૧-ફેઝ લોડ માટે અર્થ લીકેજ પ્રોટેક્શન આકૃતિ સાથે સમજાવો.	07
		અથવા	
પ્રશ્ન-૩	અ.	ટ્રાંસ્મીશન લાઇન માટે % (પરશંટેજ) ડીફફરનશીયલ રીલે ની આકૃતિ અને ઓપરેટીંગ કેરેક્ટરીસ્ટીક સાથે તેનુ વર્ણન કરો.	07
	બ.	૧-ફેઝ લોડ માટે અર્થ લીકેજ પ્રોટેક્શન નિ સર્કિટ સાથે વર્ણન કરો. ૩-ફેઝ (Y-Δ) ટ્રાંસફોર્મર માટે ટ્રાંસફોર્મર ની બન્ને બાજુ ના લાઇન વોલ્ટેજ મા રહેલા 30° ના ફેઝ-શીફ્ટ બતાવતો ફેઝર ડાયાગ્રામ દોરો અને (Y-Δ) ટ્રાંસફોર્મર સ્કિમેટિક ડાયાગ્રામ દોરો.	07
પ્રશ્ન-૪	અ.	ડિસ્ટેન્સ રીલે પ્રોટેક્શન દર્શાવતું ટ્રાંસ્મીશન લાઇન નુ મોડેલ સાથે વર્ણન કરો.	07
	બ.	ઇંડકશન કપ વાળા રીએક્ટેન્સ રીલે નુ બન્ધારણ (સ્ટ્રક્ચર) દોરો અને તેના વર્કીંગ (working) નુ વર્ણન કરો.	07
		અથવા	
પ્રશ્ન-૪	અ.	એર બ્રેક સર્કિટ બ્રેકર નિ આકૃતિ સાથે વર્ણન કરો.	07
	બ.	ડિસિ સર્કિટ બ્રેકર પર ટુંકનોંધ લખો.	07
પ્રશ્ન-૫	અ.	કરંટ ચોપીંગ એટલે શુ? તેના પર ટુક મા ચર્ચા કરો.	07
	બ.	ઇંડકશન ડીસ્ક રીલે નિ કન્સ્ટ્રક્શ સાથે વર્ણન કરો.	07
		અથવા	
પ્રશ્ન-૫	અ.	એસ-એફ-6 (SF6) સર્કિટ બ્રેકર પર ટુંકનોંધ લખો.	07
	બ.	ઇંસ્ટન્ટેનીયસ ઓવર કરંટ રીલે પર ટુંકનોંધ લખો.	07
