

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY

DIPLOMA ENGG.- SEMESTER-VI EXAMINATION - OCTOBER 2012

Subject code: 361702

Date: 27-10-2012

Subject Name: Industrial Electronics And Control

Time: 2:30 pm – 5:00 pm

Total Marks: 70

Instructions:

- 1. Attempt all questions.**
- 2. Make suitable assumptions wherever necessary.**
- 3. Figures to the right indicate full marks.**
- 4. English version is considered to be Authentic**

- | | | | |
|-------------|-----|--|-----------|
| Q.1 | (a) | Draw circuit symbol and p-n-p-n structure of SCR, explain two transistor analogy. | 07 |
| | (b) | Draw cross sectional view of TRIAC, Explain its V-I characteristics. | 07 |
| Q.2 | (a) | Draw unequal voltage distribution across series connected SCRs during dynamic condition and explain it in brief. | 07 |
| | (b) | Draw and explain equalizing circuit for parallel connected SCRs. | 07 |
| | | OR | |
| | (b) | Draw V-I characteristics of UJT, explain with circuit diagram. | 07 |
| Q.3 | (a) | Explain IGBT with structural features and working in brief. | 07 |
| | (b) | Explain SCR snubber circuit. | 07 |
| | | OR | |
| Q.3 | (a) | Explain any one driver circuit of MOSFET. | 07 |
| | (b) | Compare Power MOSFET and BJT. | 07 |
| Q.4 | (a) | Explain operation of 1- ϕ dual converter with circuit diagram and waveforms. | 07 |
| | (b) | Explain operation of 1- ϕ full converter with circuit diagram and waveforms. | 07 |
| | | OR | |
| Q. 4 | (a) | Describe 1- ϕ series inverter with circuit diagram and waveforms | 07 |
| | (b) | Explain mid-point step down cyclo-converter for discontinuous load. | 07 |
| Q.5 | (a) | Describe speed control of D.C. series motor by means of D.C. chopper. | 07 |
| | (b) | Explain A.C. resistance welding scheme with block diagram. | 07 |
| | | OR | |
| Q.5 | (a) | Explain speed control of 1- ϕ induction using DIAC and TRIAC. | 07 |
| | (b) | Explain electrical sequential timer circuit in resistance welding. | 07 |

- Q.1** (a) એસ.સી.આર.ની પરિપથ સંજ્ઞા અને સ્ટ્રક્ચરની આકૃતિ દોરો, તેને બે ટ્રાન્ઝીસ્ટર પરિપથ થી સમજાવો. 07
- (b) ટ્રાયક નો આડછેદ આકૃતિ દોરો, તેની V-I લાક્ષણિકતા દોરી સમજાવો. 07
- Q.2** (a) એસ.સી.આર. ના સીરીઝ જોડાણમાં વોલ્ટેજનું અનઈકવલ વીભાજન આકૃતિ દોરી સમજાવો. 07
- (b) એસ.સી.આર. ના સમાંતર જોડાણમાં પ્રવાહનો ઈકવલાઈઝીંગ પરિપથ આકૃતિ દોરી સમજાવો. 07
- OR**
- (b) UJT ની V-I લાક્ષણિકતા દોરો. તેને પરિપથ થી સમજાવો. 07
- Q.3** (a) IGBT નું કાર્ય અને સ્ટ્રક્ચર ની વિશેષતા સમજાવો. 07
- (b) એસ.સી.આર.નો snubber પરિપથ સમજાવો. 07
- OR**
- Q.3** (a) MOSFET નો કોઈ એક ડ્રાયવર પરિપથ સમજાવો. 07
- (b) પાવર MOSFET અને BJT ની સરખામણી કરો. 07
- Q.4** (a) 1- ϕ ડ્યુલ કનવર્ટર નું કાર્ય સરકીટ પરિપથ અને વેવફોર્મ્સ દોરી સમજાવો. 07
- (b) 1- ϕ ફુલ કનવર્ટર નું કાર્ય સરકીટ પરિપથ અને વેવફોર્મ્સ દોરી સમજાવો. 07
- OR**
- Q. 4** (a) 1- ϕ સીરીઝ ઈનવર્ટર સરકીટ પરિપથ અને વેવફોર્મ્સ દોરી સમજાવો. 07
- (b) મીડ પોઇન્ટ સ્ટેપ ડાઉન સાયકલો કનવર્ટર ડીસકન્ટીન્યુસ લોડ માટે સમજાવો. 07
- Q.5** (a) ડી.સી.ચોપર ની મદદ થી ડી.સી મોટરની સ્પીડ કંટ્રોલની પદ્ધતિ સમજાવો. 07
- (b) એ.સી. રેઝીસ્ટન્સની વેલ્ડીંગની પદ્ધતિ બ્લોક ડાયાગ્રામ ની મદદથી સમજાવો. 07
- OR**
- Q.5** (a) એ.સી. મોટર સ્પીડ કંટ્રોલની પદ્ધતિ DIAC અને TRIAC નો ઉપયોગ કરી સમજાવો. 07
- (b) રેઝીસ્ટન્સ વેલ્ડીંગમાં સીકન્સીયલ ટાઈમર સરકીટ સમજાવો. 07
