

GUJARAT TECHNOLOGICAL UNIVERSITY**Diploma Engineering - SEMESTER-I & II • EXAMINATION – WINTER 2013****Subject Code: 3310702****Date: 24-12-2013****Subject Name: Fundamentals of Digital Electronics****Time: 02:30 pm- 05:00 pm****Total Marks: 70****Instructions:**

1. Attempt any five questions.
2. Make Suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Use of programmable & Communication aids are strictly prohibited.
5. Use of only simple calculator is permitted in Mathematics.
6. English version is authentic.

- Q.1** Answer any seven out of ten. **14**
1. $(B3E)_{16} = (\quad)_{10}$
 2. $(11011.1100)_2 = (\quad)_{16}$
 3. $(423)_{10} = (\quad)_8$
 4. $(121)_8 = (\quad)_{10}$
 5. 2's complement of $(1001)_2 = \underline{\hspace{2cm}}$
 6. $(1001)_2 + (1001)_2 = (\quad)_2$
 7. $A + AB + AC = \underline{\hspace{2cm}}$
 8. Draw Truth Table for EX-OR.
 9. 10's complement of $(625)_{10} = (\quad)_{10}$
 10. Explain "MINTERM".
- Q.2** (a) Draw symbols of NAND, EX-OR and BUBBLED OR gates. **03**
- OR
- (a) Draw the Truth Table for expression $f(A,B) = AB' + A'B + A'B'$ **03**
- (b) Write De-Morgan's theorem and prove any one of them using Truth Table. **03**
- OR
- (b) Prove $(A+C)(A+D)(B+C)(B+D) = AB+CD$ using Boolean algebra laws **03**
- (c) Subtract $(111001)_2$ from $(101011)_2$ using 1's complement **04**
- OR
- (c) $(8E)_{16} + (100)_2 = (\quad)_{10}$ **04**
- (d) Prove that $(A+B)(A'+C) = AC + A'B$ **04**
- OR
- (d) Simplify the Boolean expression $AB + A(B+C) + B(B+C)$ **04**
- Q.3** (a) Draw logic circuit for the expression $(AB+C)' + BC'$ **03**
- OR
- (a) Simplify using K-Map for $f(A,B,C) = \prod(2,3,5,6)$ **03**
- (b) Simplify with the help of K-Map for expression **03**
- $f(A,B,C) = ABC + AB'C + A'BC + A'B'C'$
- OR
- (b) Simplify with the help of K-Map for expression **03**
- $f(X,Y,Z) = \sum m(1,3) + d(0,2,5,7)$
- (c) Realize OR gate using both universal gates **04**
- OR
- (c) Why NAND is known as Universal Gate? Implement EX-OR using NAND. **04**
- (d) Simplify with the help of K-Map for expression **04**
- $f(A,B,C,D) = \sum m(0,2,6,10,11,12,13) + d(3,4,5,14,15)$

	OR	
(d)	Simplify with the help of K-Map for expression $f(P,Q,R,S) = \sum m(1,2,6,7,8,13,14,15) + d(3,5,12)$	04
Q.4	(a) Draw Truth Table & K-Map for Full Subtractor.	03
	OR	
(a)	Draw logic circuit for 3-8 line decoder.	03
(b)	Explain Half Adder in detail with circuit diagram.	04
	OR	
(b)	Give BCD code and Excess-3 code for (i) $(14)_{10}$ (ii) $(5)_{10}$	04
(c)	Explain how to convert BCD code into Excess-3 code using K-Map.	07
Q.5	(a) Explain importance of Multiplexer. Describe 4-1 multiplexer.	07
	(b) Explain 2 bit magnitude comparator with the help of K-Map.	07

ગુજરાતી

પ્રશ્ન. ૧	દશમાંથી કોઇપણ સાતના જવાબ આપો.	૧૪
૧.	$(B3E)_{16} = (\quad)_{10}$	
૨.	$(11011.1100)_2 = (\quad)_{16}$	
૩.	$(423)_{10} = (\quad)_8$	
૪.	$(121)_8 = (\quad)_{10}$	
૫.	$(1001)_2$ નું 2'S complement = _____	
૬.	$(1001)_2 + (1001)_2 = (\quad)_2$	
૭.	$A + AB + AC = \underline{\hspace{2cm}}$	
૮.	EX-OR નું ટ્રુથ ટેબલ બનાવો.	
૯.	$(625)_{10}$ નું 10'S complement = $(\quad)_{10}$	
૧૦	“MINTERM” સમજાવો.	
પ્રશ્ન. ૨	અ NAND, EX-OR અને BUBBLED OR લોજિકલ ગેટની નિશાની દોરો.	03
	OR	
અ	$f(A,B) = AB' + A'B + A'B'$ આ સમીકરણનું ટ્રુથ ટેબલ બનાવો	03
બ	દ-મોર્ગનના પ્રમેય લખો અને કોઈ પણ એક ટ્રુથ ટેબલની મદદથી સાબિત કરો.	03
	OR	
બ	બુલિયન અલ્જીબ્રાના નિયમોથી સાબિત કરો $(A+C)(A+D)(B+C)(B+D) = AB+CD$	03
ક	$(101011)_2$ માંથી $(111001)_2$ ને 1's complement નો ઉપયોગ કરી બાદબાકી કરો.	0૪
	OR	
ક	$(8E)_{16} + (100)_2 = (\quad)_{10}$	0૪
ડ	સાબિત કરો કે $(A+B)(A'+C) = AC + A'B$	0૪

- OR
- 5 $AB + A(B+C) + B(B+C)$ આ સમીકરણને સાદું રૂપ આપો (સીમ્પ્લીફાઈ કરો) 04
- પ્રશ્ન. 3 અ $(AB+C)' + BC'$ આ સમીકરણ માટે લોજિક સર્કીટ દોરો. 03
- OR
- અ $f(A,B,C) = \prod(2,3,5,6)$ ને K-Map નો ઉપયોગ કરી સાદું રૂપ આપો. 03
- બ K-Map નો ઉપયોગ કરી સાદું રૂપ આપો. 03
- $f(A,B,C) = ABC + AB'C + A'BC + A'B'C'$
- OR
- બ K-Map નો ઉપયોગ કરી સાદું રૂપ આપો. $f(X,Y,Z) = \sum m(1,3) + d(0,2,5,7)$ 03
- ક બંને પ્રકારના યુનિવર્સલ ગેટનો ઉપયોગ કરીને OR ગેટ બનાવો. 04
- OR
- ક NAND ગેટ શા માટે યુનિવર્સલ ગેટ તરીકે ઓળખાય છે? EX-OR ગેટ 04
- NAND ગેટ નો ઉપયોગ કરી બનાવો.
- 5 K-Map નો ઉપયોગ કરી સાદું રૂપ આપો. 04
- $f(A,B,C,D) = \sum m(0,2,6,10,11,12,13) + d(3,4,5,14,15)$
- OR
- 5 K-Map નો ઉપયોગ કરી સાદું રૂપ આપો. 04
- $f(P,Q,R,S) = \sum m(1,2,6,7,8,13,14,15) + d(3,5,12)$
- પ્રશ્ન. 4 અ Full Subtractor ના ટ્રુથ ટેબલ અને K-Map દોરો. 03
- OR
- અ 3-8 line decoder માટે લોજિક સર્કીટ દોરો. 03
- બ Half Adder સર્કીટ ડાયાગ્રામ સાથે વિસ્તારથી સમજાવો. 04
- OR
- બ નિમ્નલિખિત માટે BCD કોડ અને Excess-3 કોડ લખો. 04
- (i) $(14)_{10}$
(ii) $(5)_{10}$
- ક BCD કોડને Excess-3 કોડ માં પરિવર્તિત કઈ રીતે કરી શકાય તે K-Map થી 04
- સમજાવો.
- પ્રશ્ન. 5 અ Multiplexer નું મહત્વ સમજાવો. 4-1 multiplexer નું વર્ણન કરો. 04
- બ 2 bit magnitude comparator ને K-Map ની મદદ થી સમજાવો. 04
