

GUJARAT TECHNOLOGICAL UNIVERSITY**Diploma Engineering - SEMESTER-III • EXAMINATION – WINTER 2013****Subject Code: 331103****Date: 28-11-2013****Subject Name: Electronics Network and Lines****Time: 02:30 pm - 05:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is Authentic

- Q.1** (a) Define the following Terms **07**
 (i) Active & Passive Network (ii) Branch, mesh & Node
 (iii) KVL and KCL (iv) Transfer Impedance
- (b) What is the Importance of Thevenin's Theorem & Norton's Theorem in Network analysis & Prove any one. **07**
- Q.2** (a) State & prove Reciprocity Theorem. **07**
 (b) Explain the important characteristics of series resonant circuit with the help of necessary derivation. **07**
- OR**
- (b) A parallel resonant CKT having Inductance of 1mh with quality factor $Q=100$ & Resonant frequency $f_0=100\text{kHz}$ find out value of capacitance C , Resistance R & Bandwidth. If Inductance is changed to 100mh, find out new resonant frequency. **07**
- Q.3** (a) Define the following terms: **07**
 (i) Mutual Inductance (ii) Co-efficient of coupling
 (iii) Band width (iv) Selectivity
- (b) Explain the important characteristics of an Iron core transformer with the help of necessary derivation. **07**
- OR**
- Q.3** (a) Explain the various types of equalizer circuit and explain bridged T-type phase equalizer in brief. **07**
 (b) For the attenuator derive equation Z_{ot} & Z_{on} **07**
- Q.4** (a) State the disadvantages of constant 'K' proto type filter and explain how these disadvantages over come by m-derived filters. **07**
 (b) Design active low pass filter for cut-off freq. 3KHz and load Impedance 1kohm and maximally flat response of filter. Find gain in dB at $f=10f_c$. Draw ckt. of filter. **07**
- OR**
- Q. 4** (a) Explain lattice attenuator & derive the equation for R_1 , R_2 & R_o . **07**
 (b) Design m-derived LPF having cut-off frequency of 1KHz and very high attenuation at 1065Hz, It's load independence is 500ohm. **07**
- Q.5** (a) Derive the general line equations for voltage and current at any point on Infinite line. **07**
 (b) (i) Explain distortion less condition for lines. **07**

(ii) Define neper and DB & give the relation between them.

OR

- Q.5** (a) Define reflection coefficient & standing wave ratio derive the relation between them. **07**
(b) Define Infinite line, wave length & velocity of proposition. **07**

- પ્રશ્ન-૧** અ. નીચેની વ્યાખ્યાઓ સમજાવો. **07**
(૧) એકટીવ અને પેસીવ નેટવર્ક (૨) બ્રાંચ, મેસ અને નોડ
(૩) KVL અને KCL (૪) ટ્રાન્સફર ઈમ્પેડેન્સ
બ. થેવેનીયન અને નોર્ટન પ્રમેયની નેટવર્ક એનાલીસીસમાં અગત્યતા સમજાવો અને ગમે તે એકને સાબિત કરો. **07**

- પ્રશ્ન-૨** અ. રેસીપ્રોસીટી પ્રમેય લખો અને સાબિત કરો. **07**
બ. સીરીઝ પરિપથ માટેની અગત્યની લાક્ષણિકતાઓ સુત્રના મદદથી મેળવો **07**

અથવા

- બ. સમાન્તર જોડાણવાળા પરિ પથમાં ઈન્ડક્ટન્સની વેલ્યુ ૧મીલી હેનરી અને કવોલીટી ફેક્ટર $Q=100$ અને રેજોનેન્ટ આવૃત્તિ $f_0=100\text{kHz}$ તો તેના માટે કેપેસિટન્સ C , અવરોધ R અને બેન્ડવીથ શોધો. જો ઈન્ડક્ટન્સ સંખ્યામાં વધારો 100 મીલી હેનરી થાય તો રેજોનેન્ટ આવૃત્તિ શોધો. **07**

- પ્રશ્ન-૩** અ. નીચેની વ્યાખ્યાઓ જણાવો. **07**
(૧) મ્યુચુઅલ ઈન્ડક્ટન્સ (૨) કોઈફિન્ટ ઓફ કપલીંગ
(૩) બેન્ડવીથ (૪) સિલેક્ટીવીટી
બ. આયન ફોર ટ્રાન્સફોર્મરની ઉપયોગી લાક્ષણિકતાઓ સૂત્રની મદદથી શોધો. **07**

અથવા

- પ્રશ્ન-૩** અ. જુદા જુદા પ્રકારના ઈકવાલાઈઝરની સર્કીટ દોરો. અને બ્રીજ ટીપ્રકારના ફેઝ ઈકવાલાઈઝરને ટૂંકમાં સમજાવો. **07**
બ. એટેન્યુએટર માટે Z_{ot} & Z_{on} નું સૂત્ર શોધો. **07**

- પ્રશ્ન-૪** અ. કોન્સટન્ટ 'K' પ્રોટો ટાઈપ પ્રકારના ફિલ્ટરના ગેરફાયદાઓ જણાવો. અને m-ડીરાઈવડ ફિલ્ટર આ ગેરફાયદાઓને કેવી રીતે દૂર કરે છે તે સમજાવો. **07**
બ. એકટીવ લો પાસ ફિલ્ટર કે જેની કટ ઓફ આવૃત્તિ ૩કીલો હટઝ છે **07**

અને લોડ અવરોધ ૧કીલો ઓહમ છે અને મુખ્યતર ફલેટ રિસપોન્સ અંગે ડિઝાઇન કરો. ગેઈન ડીબીમાં શોધો.
જ્યારે $f=10f_c$ હોય તો તેના માટે સર્કિટ દોરો.

અથવા

પ્રશ્ન-૪

- અ લેટાઈસ એટેન્યુએટર સમજાવો અને તેના માટે R_1 , R_2 અને R_0 ના સૂત્રો તારવો. 07
- બ m- ડીઈરાવડ LPF કે જેની કટ ઓફ આવૃત્તિ ૧KHz છે અને તેની મોટી અવરોધ આવૃત્તિ ૧૦૬૫ હટઝ છે અને લોડ અવરોધ ૫૦૦ ઓહમ છે. તેની રચના કરો. 07

પ્રશ્ન-૫

- અ ટ્રાન્સમિશન લાઈન પર કોઈપણ બિંદુઓ પર વોલ્ટેજ તથા કરન્ટ માટેના સામાન્ય લાઈન સૂત્રો મેળવો. 07
- બ (1) ડિસ્ટોર્શન વગરની લાઈન માટેની શરતો મેળવો. 07
(2) નિપર અને ડીબી જણાવો અને બે વચ્ચેનો સંબંધ જણાવો.

અથવા

પ્રશ્ન-૫

- અ રિફ્લેક્શન કોઈફિસન્ટ અને સ્ટેન્ડીંગ વેવ રેસિઓ શું છે તે જણાવો અને બંનેને જોડતું સમીકરણ શોધો. 07
- બ ટ્રાન્સમિશન લાઈન માટે નીચેની વ્યાખ્યાઓ જણાવો. 07
ઈનફાઈનાઈટ લાઈન, વેવ લેન્થ અને વેલોસિટી ઓફ પ્રોપેગેસીન
