

**GUJARAT TECHNOLOGICAL UNIVERSITY****Diploma Engineering - SEMESTER-III • EXAMINATION – WINTER 2013****Subject Code: 3330301****Date: 28-11-2013****Subject Name: Basic Electronics****Time: 02:30 pm - 05:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is considered to be Authentic.

- Q.1** (a) Describe the working principle of Single Phase Transformer **06**  
(b) Define following terms **08**  
a) Periodic time b) Amplitude c) Angular Velocity d) LDR
- Q.2** (a) Differentiate between intrinsic and extrinsic semiconductor materials. **07**  
(b) Explain working principle and applications of zener diode. **07**  
OR  
(b) Explain working principle of the seven segment display. **07**
- Q.3** (a) Discriminate the working of the optocoupler and opto-isolator. **07**  
(b) Compare the working of CB, CE and CC transistors. **07**  
OR
- Q.3** (a) Differentiate between photo diode and photo transistor. **07**  
(b) Define Leakage current and explain relationship between  $\alpha$  and  $\beta$  . **07**
- Q.4** (a) Explain Transistor as an amplifier. **07**  
(b) Write short note on Regulated power supply. **07**  
OR
- Q. 4** (a) Explain Class B push-pull Amplifier Operation. **07**  
(b) Draw & Explain Block diagram of Switched Mode Power Supply (SMPS). **07**
- Q.5** (a) Explain the need of power amplifier and Class A amplifier. **07**  
(b) Explain Positive and Negative clipper with necessary circuit and waveform. **07**  
OR
- Q.5** (a) Write short note on Uninterrupted Power Supply (UPS). **07**  
(b) Explain Positive and Negative clamper with necessary circuit and waveform. **07**

\*\*\*\*\*

## ગુજરાતી

|           |   |                                                                         |    |
|-----------|---|-------------------------------------------------------------------------|----|
| પ્રશ્ન. ૧ | અ | સીંગલ ફેઝ ટ્રાંસફોર્મર નુ કાર્ય સમજાવો.                                 | ૦૬ |
|           | બ | નીચેની વ્યાખ્યા સમજાવો.                                                 | ૦૮ |
|           |   | અ) પીરીયોડીક ટાઈમ બ) એમ્પલીટ્યુડ ક) એન્ગુલર વેલોસીટી ડ) LDR             |    |
| પ્રશ્ન. ૨ | અ | ઈન્ડ્રેન્સીક અને એક્સટ્રેન્સીક સેમી કન્ડક્ટર વચ્ચેનો તફાવત સમજાવો.      | ૦૭ |
|           | બ | ઝેનર ડાયોડનુ મુખ્ય કાર્ય અને ઉપયોગીતા સમજાવો.                           | ૦૭ |
|           |   | અથવા                                                                    |    |
|           | બ | સેવન સેગમેન્ટ ડિસપ્લેનુ મુખ્ય કાર્ય સમજાવો.                             | ૦૭ |
| પ્રશ્ન. ૩ | અ | ઓપ્ટો કપ્લર અને ઓપ્ટો આઈસોલેટર ના કાર્ય વચ્ચેનો તફાવત સમજાવો.           | ૦૭ |
|           | બ | CB, CE, અને CC નુ કાર્ય સરખાવો.                                         | ૦૭ |
|           |   | અથવા                                                                    |    |
| પ્રશ્ન. ૩ | અ | ફોટો ડાયોડ અને ફોટો ટ્રાન્ઝીસ્ટર વચ્ચેનો તફાવત સમજાવો.                  | ૦૭ |
|           | બ | લીકેજ કરંટ સમજાવો અને $\alpha$ તથા $\beta$ વચ્ચેનો સંબંધ તારવો.         | ૦૭ |
| પ્રશ્ન. ૪ | અ | ટ્રાન્ઝિસ્ટરને એમ્પ્લીફાયર તરીકે સમજાવો.                                | ૦૭ |
|           | બ | રેગ્યુલેટેડ પાવર સપ્લાય વિષે ટુંક નોંધ લખો.                             | ૦૭ |
|           |   | અથવા                                                                    |    |
| પ્રશ્ન. ૪ | અ | ક્લાસ B પુશ-પુલ એમ્પ્લીફાયરનુ કાર્ય સમજાવો.                             | ૦૭ |
|           | બ | સ્વિચિંગ સ્થિતિ પાવર સપ્લાય (SMPS) નો બ્લોક ડાયાગ્રામ દોરો અને સમજાવો.  | ૦૭ |
| પ્રશ્ન. ૫ | અ | પાવર એમ્પ્લીફાયર અને ક્લાસ A એમ્પ્લીફાયરની જરૂરિયાત સમજાવો.             | ૦૭ |
|           | બ | પોઝિટિવ અને નેગેટીવ ક્લીપર જરૂરી સર્કિટ અને વેવફોર્મ્સની સાથે સમજાવો.   | ૦૭ |
|           |   | અથવા                                                                    |    |
| પ્રશ્ન. ૫ | અ | અવિરત પાવર સપ્લાય (UPS) પર ટુંક નોંધ લખો.                               | ૦૭ |
|           | બ | પોઝિટિવ અને નેગેટીવ ક્લેમ્પર જરૂરી સર્કિટ અને વેવફોર્મ્સની સાથે સમજાવો. | ૦૭ |

\*\*\*\*\*