

GUJARAT TECHNOLOGICAL UNIVERSITY**Diploma Engineering - SEMESTER-III • EXAMINATION – WINTER 2013****Subject Code: 3331102****Date: 28-11-2013****Subject Name: Analog Electronics****Time: 02:30 pm - 05:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is considered to be Authentic.

- Q.1** (a) Explain the concept of positive feedback and negative feedback & list out advantages & disadvantages of negative feedback. **07**
(b) Explain construction, working & characteristics of UJT. **07**
- Q.2** (a) Explain Drain & Transfer characteristics of JFET. **07**
(b) Explain Crystal oscillator. **07**
- OR
- (b) Explain Wein Bridge oscillator. **07**
- Q.3** (a) Derive an equation for overall gain of negative feedback amplifier. **07**
(b) Explain working of different types of power amplifier class A, class B, Class AB, Class C, (without derivation) **07**
- OR
- Q.3** (a) Derive an equation for efficiency of class B push-pull power amplifier. **07**
(b) Explain working of class B push-pull power amplifier. **07**
- Q.4** (a) Define JFET parameters r_d , g_m , & μ & find relation in between them. **07**
(b) Explain working of Enhancement type MOSFET. **07**
- OR
- Q.4** (a) Define the terms related to Power Amplifier :- i) Efficiency ii) Distortion iii) Power dissipation capability **07**
(b) Explain basic block diagram of OP-AMP. **07**
- Q.5** (a) Explain OP-AMP as an Inverting Amplifier (Closed loop) with derivation of voltage gain. **07**
(b) Explain working of astable multivibrator by using IC555. **07**
- OR
- Q.5** (a) Explain OP-AMP as a Summing Amplifier. **07**
(b) Explain OP-AMP as Comparator **07**

- પ્રશ્ન. ૧ અ પોઝીટીવ ફીડબેક અને નેગેટીવ ફીડબેક નું કન્સેપ્ટ સમજાવો અને નેગેટીવ ફીડબેક ના ફાયદાઓ અને ગૈર ફાયદાઓ ની યાદી લખો . ૦૭
- બ UJT ની રચના, વર્કિંગ ઓપરેશન અને લાક્ષણિકતા સમજાવો. ૦૭
- પ્રશ્ન. ૨ અ JFET ના ડ્રેન(Drain) અને ટ્રાન્સફર (Transfer) કેરેક્ટરીસ્ટીક (લાક્ષણિકતા) સમજાવો.. ૦૭
- બ ક્રીસ્ટલ ઓસીલેટર (Crystal oscillator) સમજાવો. ૦૭
- અથવા
- બ વેન બ્રીજ ઓસીલેટર (Wein Bridge oscillator) સમજાવો. ૦૭
- પ્રશ્ન. ૩ અ નેગેટીવ ફીડબેક એમ્પ્લીફાયર માટે overall gain નું equation(સમીકરણ) derive કરો ૦૭
- બ અલગ અલગ પ્રકારના પાવર એમ્પ્લીફાયર class A, class B, Class AB, Class C નું કાર્ય સમજાવો. (without derivation) ૦૭
- અથવા
- પ્રશ્ન. ૩ અ class B પુશ-પૂલ એમ્પ્લીફાયર ની (efficiency) કાર્યક્ષમતા નું. સમીકરણ (equation) derive કરો. ૦૭
- બ Class B પુશ-પૂલ પાવર એમ્પ્લીફાયર નું વર્કિંગ ઓપરેશન. સમજાવો. ૦૭
- પ્રશ્ન. ૪ અ JFET પેરેમિટર r_d , g_m , & μ ની વ્યાખ્યા લખો અને એમના વચ્ચેનું સંબંધ (relation) સાબિત કરો . ૦૭
- બ એન્હાસમેન્ટ પ્રકારના (Enhancement type) MOSFET નું કાર્ય (working operation) સમજાવો ૦૭
- અથવા
- પ્રશ્ન. ૪ અ પાવર એમ્પ્લીફાયર ના રિલેટેડ વ્યાખ્યા લખો :-i) ઇફીસીએન્સી (કાર્યક્ષમતા)(Efficiency) ii ડીસ્ટોર્શન (Distortion) iii) પાવર ડિસીપેશન કેપેબીલીટી (power dissipation capability) ૦૭
- બ OP-AMP નું બેસીક બ્લોક ડાયગ્રામ સમજાવો. ૦૭
- પ્રશ્ન. ૫ અ OP-AMP ને Inverting Amplifier (Closed loop) કલોઝડ લુપ ઈન્વર્ટીંગ એમ્પ્લીફાયર તરીકે સમજાવો. સાથે એના વોલ્ટેજ ગેન નું ડેરીવેશન લખો. ૦૭
- બ અસ્ટેબલ મલ્ટીફાયબ્રેટર નું વર્કિંગ ઓપરેશન IC555 નું ઉપયોગ કરીને સમજાવો. ૦૭
- OR
- પ્રશ્ન. ૫ અ OP-AMP નું અપ્લીકેશન સમીંગ એમ્પ્લીફાયર ને Summing Amplifier સમજાવો. ૦૭
- બ OP-AMP નું અપ્લીકેશન કમ્પેરેટર(Comparator)ને સમજાવો. ૦૭
