

GUJARAT TECHNOLOGICAL UNIVERSITY
DIPLOMA ENGINEERING - SEMESTER-V • EXAMINATION – WINTER 2013

Subject Code: 350904**Date: 05-12-2013****Subject Name: Digital Electronics and Digital Instruments****Time: 02:30 pm - 05:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is considered to be Authentic.

- Q.1** Answer any of Seven of the following: **14**
- (i) Convert $(652.43)_2$ to Decimal number.
 - (ii) Convert $(111.101)_8$ to binary number.
 - (iii) Convert $(35AC.90F)_{16}$ to Octal number.
 - (iv) Convert $(111011.11)_2$ to hexadecimal number.
 - (v) Add $(11011011)_2$ to $(01011101)_2$
 - (vi) Multiply $(1101.11)_2$ by $(1.01)_2$
 - (vii) Subtract $(10110)_2$ from $(1101101)_2$
 - (viii) Divide $(10011)_2$ by $(100)_2$
 - (ix) Perform the binary subtraction using 2's complement: $(01101)_2 - (00101)_2$
 - (x) Perform the binary subtraction using 1's complement: $(1011)_2 - (0111)_2$
- Q.2** (a) Give and explain different characteristics of digital logic families. **07**
- (b) Prove that NAND gate is Universal gate with truth tables. **07**
- OR**
- (b) Draw and explain working of (i) N-channel MOSFET as NOR and (ii) CMOS as Inverter. **07**
- Q.3** (a) Explain BCD Adder circuit with the help of logic diagram and truth table. **07**
- (b) Prove following using Boolean algebra. **07**
- (i) $\overline{A}B + A\overline{B} + \overline{A}\overline{B} + AB = 1$
- (ii) $\overline{A}BC + A\overline{B}C + ABC + \overline{A}BC = BC + \overline{A}C$
- OR**
- Q.3** (a) Draw the logic diagram for the following Boolean Expression. **07**
- (i) $y = \overline{A}\overline{B}C D + A\overline{B}CD + ABCD$
- (ii) $y = \overline{A}B\overline{C}D + A\overline{B}CD + ABC\overline{D} + ABCD$
- (b) State and explain De Morgan's theorems with the help of Truth Table. **07**
- Q.4** (a) Describe the working of J-K flip flop with wave form & Truth Table and Explain how the Race condition is eliminated? **07**
- (b) Describe the working of Modulo – 5 ripple counter with wave form & Truth Table. **07**
- OR**
- Q.4** (a) Draw and explain Universal Shift Registers with Truth Table. **07**
- (b) Compare the static RAM and Dynamic RAM. **07**
- Q.5** (a) State and explain the specification of D/A converters. **07**
- (b) Draw the block diagram of digital frequency meter and explain its working. **07**
- OR**
- Q.5** (a) Draw and explain the R-2R ladder D/A converter. **07**
- (b) Explain working and construction of LCD. **07**

પ્રશ્ન-૧	નીચેનામાંથી કોઈના સાતના જવાબ આપો.	૧૪
	(i) $(652.43)_2$ ને ડેસીમલ નંબરમાં ફેરવો.	
	(ii) $(111.101)_8$ ને બાયનરી નંબરમાં ફેરવો.	
	(iii) $(35AC.90F)_{16}$ ને ઓક્ટેલ નંબરમાં ફેરવો.	
	(iv) $(111011.11)_2$ ને હેક્ઝાડેસીમલ નંબરમાં ફેરવો.	
	(v) $(11011011)_2$ અને $(01011101)_2$ નો સરવાળો કરો.	
	(vi) $(1101.11)_2$ ને $(1.01)_2$ થી ગુણાકાર કરો.	
	(vii) $(10110)_2$ ને $(1101101)_2$ માંથી બાદ કરો.	
	(viii) $(10011)_2$ ને $(100)_2$ વડે ભાગો.	
	(ix) 2's કોમ્પ્લીમેન્ટનો ઉપયોગ કરીની બાદબાકી કરો.: $(01101)_2 - (00101)_2$	
	(x) 1's કોમ્પ્લીમેન્ટનો ઉપયોગ કરીની બાદબાકી કરો.: $(1011)_2 - (0111)_2$	
પ્રશ્ન-૨	અ ડીજીટલ લોજીક ફેમીલીના ગુણધર્મો જણાવો અને સમજાવો.	૦૭
	બ સાબીત કરો ટ્રુથ ટેબલ સાથે કે NAND ગેટ એ સાર્વત્રીક ગેટ છે.	૦૭
	અથવા	
	બ ડાયાગ્રામની મદદથી સમજાવો. (1) NOR ગેટ N-ચેનલ MOSFET થી અને (2) ઇન્વર્ટર એ CMOS થી.	૦૭
પ્રશ્ન-૩	અ લોજીક ડાયાગ્રામ અને ટ્રુથ ટેબલ ની મદદથી BCD એડરની સરકીટ સમજાવો.	૦૭
	બ નીચેના બુલીયન એક્સપ્રેશન સાબિત કરો.	૦૭
	(i) $\overline{AB} + A\overline{B} + \overline{A}\overline{B} + AB = 1$	
	(ii) $\overline{ABC} + \overline{A}\overline{B}\overline{C} + ABC + A\overline{B}\overline{C} = BC + A\overline{C}$	
	અથવા	
પ્રશ્ન-૩	અ નીચેના બુલીયન એક્સપ્રેશનના સુત્રો માટે લોજીક ડાયાગ્રામ દોરો.	૦૭
	(i) $y = \overline{A}\overline{B}\overline{C}\overline{D} + A\overline{B}\overline{C}\overline{D} + ABCD$	
	(ii) $y = \overline{A}\overline{B}\overline{C}\overline{D} + A\overline{B}\overline{C}\overline{D} + A\overline{B}\overline{C}\overline{D} + ABCD$	
	બ ડી મોર્ગનના પ્રમયો લખો અને ટ્રુથ ટેબલની મદદથી સમજાવો.	૦૭
પ્રશ્ન-૪	અ J-K ફ્લોપ ફ્લોપને દોરી વેવ ફોર્મ અને ટ્રુથ ટેબલની મદદથી કાર્યપદ્ધતિ સમજાવો અને સમજાવો રેસ કન્ડીશનને કેવી રીતે નાબુદ કરી શકાય?	૦૭
	બ Modulo - 5 રીપલ કાઉન્ટરની કાર્યપદ્ધતિ વેવ ફોર્મ અને ટ્રુથ ટેબલની મદદથી સમજાવો.	૦૭
	અથવા	
પ્રશ્ન-૪	અ યુનિવર્સલ શીફ્ટ રજીસ્ટરને દોરીને ટ્રુથ ટેબલની મદદથી સમજાવો.	૦૭
	બ સ્ટેટીક રેમ અને ડાયનેમીક રેમ વચ્ચે સરખામણી કરો.	૦૭
પ્રશ્ન-૫	અ ડીજીટલ થી એનાલોગ કન્વર્ટરના સ્પેસીફિકેશન જણાવો અને સમજાવો.	૦૭
	બ ડીજીટલ ફીકવન્સી મીટરનો બ્લોક ડાયાગ્રામ દોરી તેની કાર્યપદ્ધતિ સમજાવો.	૦૭
	અથવા	
પ્રશ્ન-૫	અ R-2R લેડર ડીજીટલ થી એનાલોગ કન્વર્ટર દોરીને સમજાવો.	૦૭
	બ LCD ની રચના અને કાર્યપદ્ધતિ સમજાવો.	૦૭
