

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY**Diploma Engineering C to D Bridge Course Examination – WINTER 2013****Subject Code: C300014****Date: 26-12-2013****Subject Name: Basic of Electrical and Electronics****Time: 02:30 pm - 04:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Each Question is of 1 Mark.
4. English version is considered to be Authentic.
5. Use of Simple Calculator is permissible. (Scientific / Higher Version not allowed)

No.	Question Text and Option			
1.	How many terminals are there in diode?			
	A.	Two	B.	Three
	C.	Four	D.	Five
2.	Which material is used to make PN junction Diode?			
	A.	conducting	B.	semiconducting
	C.	insulating	D.	None of above
3.	How many terminals are there in transistor?			
	A.	Two	B.	Three
	C.	Four	D.	Five
4.	What is the function of a Resistor?			
	A.	To increase the current	B.	To oppose the current
	C.	To generate the current	D.	None of above
5.	What is the function of capacitor?			
	A.	Charging & discharging	B.	Generating & decreasing
	C.	Generating & increasing	D.	None of above
6.	The charge density of emitter is always _____ collector in transistor.			
	A.	Higher than	B.	Lower than
	C.	Halved than	D.	Same as
7.	If two inductors L1 and L2 are connected in series, then total Inductor L=_____.			
	A.	$L=L1 - L2$	B.	$L=L1 \times L2$
	C.	$L=L1 \div L2$	D.	$L=L1 + L2$
8.	If two capacitors C1 and C2 are connected in parallel, then total capacitor C=_____.			
	A.	$C=C1 - C2$	B.	$C=C1 \times C2$
	C.	$C=C1 \div C2$	D.	$C=C1 + C2$
9.	If two inductors L1 and L2 are connected in parallel, then total Inductor L=_____.			
	A.	$L=(1/L1)+(1/L2)$	B.	$L=(L1 \times L2)/(L1 + L2)$
	C.	$L=(L1 \div L2)/(L1 \times L2)$	D.	$L=(L1 - L2)/(L1 \times L2)$
10.	If two capacitors C1 and C2 are connected in series, then total capacitor C=_____.			
	A.	$C=(C1 - C2)/(C1 \times C2)$	B.	$C=(C1 + C2)/(C1 \times C2)$
	C.	$C=(C1 \div C2)/(C1 \times C2)$	D.	$C=(C1) + (C2)$
11.	If two resistors R1 and R2 are connected in series, then total resistor R=_____.			
	A.	$R=(R1 + R2)$	B.	$R=(R1 \times R2)$
	C.	$R=(R1 - R2)$	D.	$R=(R1 \div R2)$
12.	If two resistors R1 and R2 are connected in parallel, then total resistor R=_____.			
	A.	$R=(1/R1)+(1/R2)$	B.	$R=(R1 \times R2)/(R1 + R2)$
	C.	$R=(R1 - R2)/(R1 + R2)$	D.	$R=(R1 \div R2)/(R1 + R2)$
13.	The charged capacitor can acts as a _____.			
	A.	Voltage source	B.	Inverter
	C.	Rectifier	D.	None of above

14.	The charged inductor can acts as a _____.			
	A.	Rectifier	B.	Current source
	C.	Inverter	D.	Resistor
15.	What type of impurity can be added to make P type semiconductor?			
	A.	Acceptor and Donor	B.	Acceptor
	C.	Donor	D.	None of above
16.	What type of impurity can be added to make N type semiconductor?			
	A.	Acceptor and Donor	B.	Acceptor
	C.	Donor	D.	None of above
17.	What types of transistors are available?			
	A.	P-P-N & P-N-P	B.	N-N-P & N-P-P
	C.	N-P-N & P-N-P	D.	P-P-P & N-N-N
18.	What type of DC voltage connection makes diode forward biased?			
	A.	Positive-Positive	B.	Positive-Positive & Negative-Negative
	C.	Negative-Negative	D.	None of above
19.	If two resistors of same value are connected in series then equivalent resistor is _____.			
	A.	Double	B.	Half
	C.	Triple	D.	Not Possible
20.	If two resistors of same value are connected in parallel then equivalent resistor is _____.			
	A.	Double	B.	Half
	C.	Triple	D.	Not Possible
21.	Ideally a diode can acts as a _____.			
	A.	Wire	B.	Switch
	C.	Voltage source	D.	Current source
22.	What is the function of a rectifier?			
	A.	DC to DC	B.	DC to AC
	C.	AC to DC	D.	All of above
23.	What is the function of an Inverter?			
	A.	DC to DC	B.	DC to AC
	C.	AC to DC	D.	All of above
24.	How many diodes are used in Half wave rectifier?			
	A.	Two	B.	One
	C.	All of above	D.	Four
25.	How many diodes are used in Full wave rectifier?			
	A.	Two	B.	One
	C.	All of above	D.	Four
26.	How many diodes are used in Bridge Rectifier?			
	A.	Two	B.	One
	C.	All of above	D.	Four
27.	What is the function of Transformer?			
	A.	AC to AC	B.	AC to DC
	C.	DC to AC	D.	All of above
28.	_____ is also known as rotating transformer.			
	A.	AC Motor	B.	Rectifier
	C.	DC Motor	D.	Inverter
29.	The main components in AC Motor's are _____.			
	A.	Stator & Rotor	B.	Inductor & diode
	C.	Stator & Transistor	D.	Stator & tube
30.	The main components in DC Motor's are _____.			
	A.	Armature winding & diode	B.	Armature winding & Field Winding
	C.	Transistor & Field Winding	D.	Transistor & Diode
31.	In transformer, if secondary voltage increases then secondary current _____.			
	A.	Increases	B.	Remain same
	C.	Decreases	D.	Half

32.	In which region the transistor can work as an amplifier?			
	A.	Active	B.	Saturation
	C.	Cut off	D.	All of above
33.	The resistance of forward biased diode is always higher then reverse biased diode.			
	A.	True	B.	False
	C.	Not always	D.	Cannot say
34.	In which region the transistor can work as an ON switch?			
	A.	Active	B.	Saturation
	C.	Cut off	D.	All of above
35.	In which region the transistor can work as an OFF switch?			
	A.	Active	B.	Saturation
	C.	Cut off	D.	All of above
36.	The Ohm's law is given by _____.			
	A.	$V = IR$	B.	$R = VI$
	C.	$P = IR$	D.	$I = VR$
37.	An emf induced in a coil due to change in current in a neighbouring coil is known as _____.			
	A.	Self induced emf	B.	Dynamically induced emf
	C.	Mutually induced emf	D.	None of above
38.	For an AC system in which frequency is 100Hz, periodic time is _____ milliseconds.			
	A.	20	B.	10
	C.	5	D.	50
39.	For an AC system an inductive reactance is given by _____.			
	A.	$X_c = 1/2\pi fC$	B.	$X_L = 2\pi fL$
	C.	$R_c = 2\pi fC$	D.	None of above
40.	For an AC system a capacitive reactance is given by _____.			
	A.	$X_c = 1/2\pi fC$	B.	$X_L = 2\pi fL$
	C.	$R_c = 2\pi fC$	D.	None of above
41.	The transformer works on the principle of _____.			
	A.	Self induction	B.	Multiple induction
	C.	Mutual induction	D.	Electric formation
42.	The transformers are rated in _____.			
	A.	KVA	B.	KI
	C.	KV	D.	Ampere
43.	A transformer steps up the voltage by a factor of 10. The ratio of secondary voltage to primary voltage is _____.			
	A.	1	B.	10
	C.	0.1	D.	100
44.	The direction of rotation of a DC motor can be reversed by _____.			
	A.	Changing the supply polarity	B.	Reversing the armature connection
	C.	Reversing the field connection	D.	None of above
45.	The direction of rotation of an AC motor can be reversed by _____.			
	A.	Changing the supply polarity	B.	Reversing the armature connection
	C.	Reversing the field connection	D.	None of above
46.	The unit of resistance is _____.			
	A.	Faraday	B.	ohm
	C.	henry	D.	mho
47.	The unit of current is _____.			
	A.	ohm	B.	meter
	C.	mho	D.	ampere
48.	The unit of an Inductor is _____.			
	A.	ohm	B.	ampere
	C.	henry	D.	mho

49.	The resistance of conducting material _____.			
	A.	Varies with temperature	B.	Varies with moisture
	C.	Varies with frequency	D.	Varies with sound
50.	The unit of Flux is _____.			
	A.	ampere	B.	weber
	C.	meter	D.	henry
51.	Frequency f can also be measured in _____.			
	A.	Meter per second	B.	Cycle per second
	C.	Cycle per meter	D.	Ampere per meter
52.	T and f are related by _____.			
	A.	$T = 1/f$	B.	$T = f$
	C.	$f = T/2$	D.	None of above
53.	Transistor is commonly used to amplify _____.			
	A.	voltage	B.	current
	C.	power	D.	All of above
54.	Which type of capacitor commonly has negative and positive polarity?			
	A.	Ceramic	B.	electrolytic
	C.	Carbon film	D.	Metal film
55.	What is relation between input and output ripple frequency for bridge rectifier?			
	A.	$f_{\text{output}} = f_{\text{input}}$	B.	$f_{\text{output}} = 2f_{\text{input}}$
	C.	$f_{\text{output}} = 3f_{\text{input}}$	D.	$f_{\text{output}} = 4f_{\text{input}}$
56.	What is an average dc voltage available at the output of Half wave rectifier?			
	A.	V_m/π	B.	$2V_m/\pi$
	C.	V_m	D.	$2V_m$
57.	The centre tape transformer is used in _____.			
	A.	Half wave rectifier	B.	Full wave rectifier
	C.	Bridge rectifier	D.	All of above
58.	In transformer, the output power is _____ input power.			
	A.	Same as	B.	Less than
	C.	Greater than	D.	None of above
59.	The capacitor always charges and discharges _____.			
	A.	sinusoidally	B.	abruptly
	C.	exponentially	D.	All of above
60.	The capacitive reactance of capacitor varies with _____.			
	A.	voltage	B.	frequency
	C.	current	D.	power
61.	If $R_1=5\Omega$, $R_2=5\Omega$ connected in parallel, what is equivalent resistance R?			
	A.	1Ω	B.	10Ω
	C.	2.5Ω	D.	25Ω
62.	If $R_1=5\Omega$, $R_2=5\Omega$ connected in series, what is equivalent resistance R?			
	A.	1Ω	B.	10Ω
	C.	2.5Ω	D.	25Ω
63.	If $C_1=10\mu\text{F}$, $C_2=10\mu\text{F}$ connected in series, what is equivalent capacitance C?			
	A.	$20\mu\text{F}$	B.	$100\mu\text{F}$
	C.	$5\mu\text{F}$	D.	$10\mu\text{F}$
64.	If $C_1=10\mu\text{F}$, $C_2=10\mu\text{F}$ connected in parallel, what is equivalent capacitance C?			
	A.	$20\mu\text{F}$	B.	$100\mu\text{F}$
	C.	$5\mu\text{F}$	D.	$10\mu\text{F}$
65.	What is PIV of diode used in half wave rectifier?			
	A.	$2V_m$	B.	$2V_m/\pi$
	C.	V_m	D.	V_m/π

66.	What is PIV of diode used in Bridge rectifier?			
	A.	2Vm	B.	2Vm/ π
	C.	Vm	D.	Vm/ π
67.	Applications of diode are			
	A.	Clamper	B.	clipper
	C.	switch	D.	All of above
68.	Which diode is also called variable capacitor diode?			
	A.	LED	B.	Photodiode
	C.	Tunnel diode	D.	Varactor diode
69.	If L1=10H, L2=10H connected in parallel, what is equivalent inductance L?			
	A.	5H	B.	20H
	C.	100H	D.	1H
70.	If L1=10H, L2=10H connected in series, what is equivalent inductance L?			
	A.	5H	B.	20H
	C.	100H	D.	1H

ગુજરાતી

નં.	પ્રશ્ન તેમજ વિકલ્પ			
૧.	ડાયોડમાં કેટલા ટર્મિનલ હોય છે?			
	A.	બે	B.	ત્રણ
	C.	ચાર	D.	પાંચ
૨.	પીએન જંકશન ડાયોડમાં કયુ મટિરીયલ વપરાય છે?			
	A.	કંન્ડક્ટિંગ	B.	સેમિકંન્ડક્ટિંગ
	C.	ઇન્સ્યુલેટિંગ	D.	એક પણ નહિં
૩.	ટ્રાન્ઝિસ્ટરમાં કેટલા ટર્મિનલ હોય છે?			
	A.	બે	B.	ત્રણ
	C.	ચાર	D.	પાંચ
૪.	રેઝિસ્ટરનુ કામ શું છે?			
	A.	કરંટ વધારવો	B.	કરંટ રોકવો
	C.	કરંટ બનાવવો	D.	એક પણ નહિં
૫.	કેપેસિટરનું કામ શું છે?			
	A.	ચાર્જિંગ અને ડિસચાર્જિંગ	B.	બનાવવુ અને ઘટાડવુ
	C.	બનાવવુ અને વધારવુ	D.	એક પણ નહિં
૬.	ટ્રાન્ઝિસ્ટરમાં એમિટરની ચાર્જડેન્સિટી કલેક્ટર કરતા _____ હોય છે.			
	A.	વધારે	B.	ઓછી
	C.	અડધી	D.	સરખી

૭.	જો બે ઇન્ડક્ટર L1 અને L2 સીરીઝમાં જોડેલા હોય તો ટોટલ ઇન્ડક્ટર L= _____.			
	A.	$L=L1 - L2$	B.	$L=L1 \times L2$
	C.	$L=L1 \div L2$	D.	$L=L1 + L2$
૮.	જો બે કેપેસિટર C1 અને C2 પેરેલલમાં જોડેલા હોય તો ટોટલ કેપેસિટર C= _____.			
	A.	$C=C1 - C2$	B.	$C=C1 \times C2$
	C.	$C=C1 \div C2$	D.	$C=C1 + C2$
૯.	જો બે ઇન્ડક્ટર L1 અને L2 પેરેલલમાં જોડેલા હોય તો ટોટલ ઇન્ડક્ટર L= _____. If two inductors L1 and L2 are connected in parallel, then total Inductor L= _____.			
	A.	$L=(1/L1)+(1/L2)$	B.	$L=(L1 \times L2)/(L1 + L2)$
	C.	$L=(L1 \div L2)/(L1 \times L2)$	D.	$L=(L1 - L2)/(L1 \times L2)$
૧૦.	જો બે કેપેસિટર C1 અને C2 સીરીઝમાં જોડેલા હોય તો ટોટલ કેપેસિટર C= _____.			
	A.	$C=(C1 - C2)/(C1 \times C2)$	B.	$C=(C1 + C2)/(C1 \times C2)$
	C.	$C=(C1 \div C2)/(C1 \times C2)$	D.	$C=(C1) + (C2)$
૧૧.	જો બે રેઝિસ્ટર R1 અને R2 સીરીઝમાં જોડેલા હોય તો ટોટલ રેઝિસ્ટર R= _____.			
	A.	$R=(R1 + R2)$	B.	$R=(R1 \times R2)$
	C.	$R=(R1 - R2)$	D.	$R=(R1 \div R2)$
૧૨.	જો બે રેઝિસ્ટર R1 અને R2 પેરેલલમાં જોડેલા હોય તો ટોટલ રેઝિસ્ટર R= _____.			
	A.	$R=(1/R1) + (1/R2)$	B.	$R=(R1 \times R2)/(R1 + R2)$
	C.	$R=(R1 - R2)/(R1 + R2)$	D.	$R=(R1 \div R2)/(R1 + R2)$
૧૩.	ચાર્જ કેપેસિટર _____ તરીકે કામ કરી શકે છે.			
	A.	વોલ્ટેજ સોર્સ	B.	ઇન્વર્ટર
	C.	રેક્ટીફાયર	D.	એક પણ નહિં
૧૪.	ચાર્જ ઇન્ડક્ટર _____ તરીકે કામ કરી શકે છે.			
	A.	રેક્ટીફાયર	B.	કરંટ સોર્સ
	C.	ઇન્વર્ટર	D.	રેઝિસ્ટર
૧૫.	પી ટાઇપ સેમિકન્ડક્ટર બનાવવા કઈ ઇમ્પ્યોરિટી ઉમેરાય છે?			
	A.	એક્સેપ્ટર અને ડોનર	B.	એક્સેપ્ટર
	C.	ડોનર	D.	એક પણ નહિં
૧૬.	એન ટાઇપ સેમિકન્ડક્ટર બનાવવા કઈ ઇમ્પ્યોરિટી ઉમેરાય છે?			
	A.	એક્સેપ્ટર અને ડોનર	B.	એક્સેપ્ટર
	C.	ડોનર	D.	એક પણ નહિં
૧૭.	કયા ટાઇપના ટ્રાન્ઝિસ્ટર મળતા હોય છે?			
	A.	P-P-N & P-N-P	B.	N-N-P & N-P-P
	C.	N-P-N & P-N-P	D.	P-P-P & N-N-N

૧૮.	ડીસી વોલ્ટેજ સાથે કેવી રીતે જોડવાથી ડાયોડ ફોરવર્ડ બાયસ થાય છે?			
	A.	પોઝીટીવ - પોઝીટીવ	B.	પોઝીટીવ - પોઝીટીવ અને નેગેટીવ - નેગેટીવ
	C.	નેગેટીવ - નેગેટીવ	D.	એક પણ નહિં
૧૯.	જો બે સરખા વેલ્યુના રેઝીસ્ટર સીરીઝમાં જોડીયેતો બનતો રેઝીસ્ટર _____ હોય છે .			
	A.	બમણો	B.	અડધો
	C.	ત્રણ ગણો	D.	શક્ય નથી
૨૦.	જો બે સરખા વેલ્યુના રેઝીસ્ટર પેરેલલમાં જોડીયેતો બનતો રેઝીસ્ટર _____ હોય છે .			
	A.	બમણો	B.	અડધો
	C.	ત્રણ ગણો	D.	શક્ય નથી
૨૧.	ડાયોડ _____ તરીકે કામ કરે છે.			
	A.	વાયર	B.	સ્વીચ
	C.	વોલ્ટેજ સોર્સ	D.	કરંટ સોર્સ
૨૨.	રેક્ટીફાયરનું કામ શું છે?			
	A.	DC નું DC	B.	DC નું AC
	C.	AC નું DC	D.	આપેલા બધા જ
૨૩.	ઈન્વર્ટરનું કામ શું છે?			
	A.	DC નું DC	B.	DC નું AC
	C.	AC નું DC	D.	આપેલા બધા જ
૨૪.	હાફ વેવ રેક્ટીફાયરમાં કેટલા ડાયોડ વપરાય છે?			
	A.	બે	B.	એક
	C.	આપેલા બધા જ	D.	ચાર
૨૫.	ફુલવેવરેક્ટીફાયરમાં કેટલા ડાયોડ વપરાય છે?			
	A.	બે	B.	એક
	C.	આપેલા બધા જ	D.	ચાર
૨૬.	બ્રિજ રેક્ટીફાયરમાં કેટલા ડાયોડ વપરાય છે?			
	A.	બે	B.	એક
	C.	આપેલા બધા જ	D.	ચાર
૨૭.	ટ્રાન્સફોર્મરનું કામ શું છે?			
	A.	AC નું AC	B.	AC નું DC
	C.	DC નું AC	D.	આપેલા બધા જ

	_____ ને રોટેટીંગ ટ્રાન્સફોર્મર કહેવાય છે.			
૨૮.	A.	એસી મોટર	B.	રેક્ટીફાયર
	C.	ડીસી મોટર	D.	ઈન્વર્ટર
	એસી મોટરના મુખ્ય ભાગ _____ છે.			
૨૯.	A.	સ્ટેટર અને રોટર	B.	ઈન્ડક્ટર અને ડાયોડ
	C.	સ્ટેટર અને ટ્રાન્ઝીસ્ટર	D.	સ્ટેટર અને ટ્યુબ
	ડીસી મોટરના મુખ્ય ભાગ _____ છે.			
૩૦.	A.	આર્મેચર અને ડાયોડ	B.	આર્મેચર અને ફિલ્ડવાઈન્ડિંગ
	C.	ટ્રાન્ઝીસ્ટર અને ફિલ્ડવાઈન્ડિંગ	D.	ટ્રાન્ઝીસ્ટર અને ડાયોડ
	ટ્રાન્સફોર્મરમાં સેકન્ડરી વોલ્ટેજ વધારીએ તો સેકન્ડરી કરંટ _____.			
૩૧.	A.	વધે	B.	સરખો રહે
	C.	ઘટે	D.	અડધો થાય
	ટ્રાન્ઝીસ્ટર કયા રીજીયનમાં એમ્પ્લીફાયર તરીકે કામ કરે છે?			
૩૨.	A.	એક્ટીવ	B.	સેટ્યુરેશન
	C.	કટ ઓફ	D.	આપેલા બધા જ
	ફોર્વર્ડ બાયસ ડાયોડ નો રેઝીસ્ટન્સ રીવર્સ બાયસ ડાયોડ કરતા વધારે હોય છે.			
૩૩.	A.	ખરું	B.	ખોટું
	C.	હમેશા નહિં	D.	કહી ના શકાય
	કયા રીજીયનમાં ટ્રાન્ઝીસ્ટર ઓન સ્વીચ તરીકે કામ કરે છે?			
૩૪.	A.	એક્ટીવ	B.	સેટ્યુરેશન
	C.	કટ ઓફ	D.	આપેલા બધા જ
	કયા રીજીયનમાં ટ્રાન્ઝીસ્ટર ઓફ સ્વીચ તરીકે કામ કરે છે?			
૩૫.	A.	એક્ટીવ	B.	સેટ્યુરેશન
	C.	કટ ઓફ	D.	આપેલા બધા જ
	_____ ઓહમ નો નિયમ છે.			
૩૬.	A.	$V = IR$	B.	$R = VI$
	C.	$P = IR$	D.	$I = VR$
	કોઈલમાં વહેતા કરંટમાં બદલાવને કારણે બાજુની કોઈલમાં ઈએમફ ઉદભવે તેને _____ કહેવાય છે.			
૩૭.	A.	સેલ્ફ ઈન્ડ્યુસ્ડ ઈએમફ	B.	ડાયનામીકલી ઈન્ડ્યુસ્ડ ઈએમફ
	C.	મ્યુટ્યુઅલી ઈન્ડ્યુસ્ડ ઈએમફ	D.	એક પણ નહિં
	એસી સીસ્ટમમાં 100Hz ફ્રીક્વન્સિ છે તો તેનો ટાઈમ _____ મીલી સેકન્ડ છે.			
૩૮.	A.	20	B.	10
	C.	5	D.	50

૩૯.	એસી સીસ્ટમમાં ઈન્ડક્ટીવ રીયક્ટન્સ એટલે _____ .			
	A.	$X_c = 1/2\pi fC$	B.	$X_L = 2\pi fL$
	C.	$R_c = 2\pi fC$	D.	એક પણ નહિં
૪૦.	એસી સીસ્ટમમાં કેપેસિટીવ રીયક્ટન્સ એટલે _____ .			
	A.	$X_c = 1/2\pi fC$	B.	$X_L = 2\pi fL$
	C.	$R_c = 2\pi fC$	D.	એક પણ નહિં
૪૧.	ટ્રાન્સફોર્મર _____ નિયમ મુજબ કામ કરે છે.			
	A.	સેલ્ફ ઈન્ડક્શન	B.	મલ્ટીપલ ઈન્ડક્શન
	C.	મ્યુટ્યુઅલ ઈન્ડક્શન	D.	ઇલેક્ટ્રિક ફોર્મેશન
૪૨.	ટ્રાન્સફોર્મરનું રેટીંગ _____ માં થાય છે.			
	A.	KVA	B.	KI
	C.	KV	D.	Ampere
૪૩.	જો ટ્રાન્સફોર્મર આઉટપુટ વોલ્ટેજને 10 ના ગુણકમાં વધારે તો સેકન્ડરી વોલ્ટેજ અને પ્રાયમરી વોલ્ટેજનો ગુણોત્તર _____ હોય છે.			
	A.	1	B.	10
	C.	0.1	D.	100
૪૪.	ડીસી મોટરમાં _____ બદલવાથી વિરુદ્ધ દિશામાં ફેરવી શકાય છે.			
	A.	સપ્લાય પોલારિટી	B.	આર્મેચરના જોડાણ
	C.	ફિલ્ડના જોડાણ	D.	એક પણ નહિં
૪૫.	એસી મોટરમાં _____ બદલવાથી વિરુદ્ધ દિશામાં ફેરવી શકાય છે.			
	A.	સપ્લાય પોલારિટી	B.	આર્મેચરના જોડાણ
	C.	ફિલ્ડના જોડાણ	D.	એક પણ નહિં
૪૬.	રેઝીસ્ટન્સનો એકમ _____ છે.			
	A.	ફેરાડે	B.	ઓહમ
	C.	હેન્રી	D.	મ્હો
૪૭.	કરંટનો એકમ _____ છે.			
	A.	ઓહમ	B.	મીટર
	C.	મ્હો	D.	એમ્પિયર
૪૮.	ઈન્ડક્ટરનો એકમ _____ છે.			
	A.	ઓહમ	B.	એમ્પિયર
	C.	હેન્રી	D.	મ્હો
૪૯.	કન્ડક્ટીંગ મટીરીયલનો રેઝીસ્ટન્સ _____ બદલાય છે.			
	A.	તાપમાન બદલાવાથી	B.	મોઈસ્યર બદલાવાથી
	C.	ફીક્વન્સી બદલાવાથી	D.	અવાજ બદલાવાથી

૫૦.	ફલક્ષનો એકમ શું છે?			
	A.	એમ્પીયર	B.	વેબર
	C.	મીટર	D.	હેન્રી
૫૧.	ફ્રીક્વન્સી એફ _____ માં પણ મપાય છે.			
	A.	મીટર/સેકન્ડ	B.	સાયકલ/સેકન્ડ
	C.	સાયકલ/મીટર	D.	એમ્પીયર/મીટર
૫૨.	T અને f _____ રીતે સંકળાયેલા છે.			
	A.	$T = 1/f$	B.	$T = f$
	C.	$f = T/2$	D.	એક પણ નહિં
૫૩.	ટ્રાન્ઝિસ્ટર _____ એમ્પ્લિફાય કરવા વપરાય છે.			
	A.	વોલ્ટેજ	B.	કરંટ
	C.	પાવર	D.	આપેલા બધા જ
૫૪.	કયા ટાઈપના કેપેસિટરમાં નેગેટીવ અને પોઝિટીવ પોલારીટી હોય છે?			
	A.	સેરામીક	B.	ઈલેક્ટ્રોલાયટીક
	C.	કાર્બનફિલ્મ	D.	મેટલફિલ્મ
૫૫.	બ્રિજ રેક્ટીફાયરમાં ઈનપુટ અને આઉટપુટ રીપલ ફ્રીક્વન્સીનો સબંધ કયો છે?			
	A.	$f_{\text{output}} = f_{\text{input}}$	B.	$f_{\text{output}} = 2f_{\text{input}}$
	C.	$f_{\text{output}} = 3f_{\text{input}}$	D.	$f_{\text{output}} = 4f_{\text{input}}$
૫૬.	હાફ વેવ રેક્ટીફાયરના આઉટપુટમાં એવરેજ ડીસી વોલ્ટેજ કેટલા મળે છે?			
	A.	V_m/π	B.	$2V_m/\pi$
	C.	V_m	D.	$2V_m$
૫૭.	સેન્ટર ટેપ ટ્રાન્સફોર્મર _____ માં વપરાય છે.			
	A.	હાફવેવ રેક્ટીફાયર	B.	ફુલવેવ રેક્ટીફાયર
	C.	બ્રિજ રેક્ટીફાયર	D.	આપેલા બધા જ
૫૮.	ટ્રાન્સફોર્મરમાં આઉટપુટ પાવર ઈનપુટ પાવર _____ હોય છે.			
	A.	સરખા	B.	કરતા ઓછા
	C.	કરતા વધારે	D.	એક પણ નહિં
૫૯.	કેપેસિટર હમેશા યાર્જ અને ડીસ્ચાર્જ _____ પ્રમાણે થાય છે.			
	A.	સાયનોસોઈડલી	B.	અબ્રપ્ટલી
	C.	એક્ષપોનેન્સીયલી	D.	બધી જ રીતે
૬૦.	કેપેસિટરનો કેપેસિટીવ રીયક્ટન્સ _____ બદલાવાથી બદલાય છે.			
	A.	વોલ્ટેજ	B.	ફ્રીક્વન્સી
	C.	કરંટ	D.	પાવર

૬૧.	જો $R_1=5\Omega$, $R_2=5\Omega$ પેરેલલમાં જોડવામાં આવેતો ટોટલ રેઝીસ્ટન્સ R શોધો.			
	A.	1Ω	B.	10Ω
	C.	2.5Ω	D.	25Ω
૬૨.	જો $R_1=5\Omega$, $R_2=5\Omega$ સીરીઝમાં જોડવામાં આવેતો ટોટલ રેઝીસ્ટન્સ R શોધો.			
	A.	1Ω	B.	10Ω
	C.	2.5Ω	D.	25Ω
૬૩.	જો $C_1=10\mu F$, $C_2=10\mu F$ સીરીઝમાં જોડવામાં આવેતો ટોટલ કેપેસિટન્સ C શોધો.			
	A.	$20\mu F$	B.	$100\mu F$
	C.	$5\mu F$	D.	$10\mu F$
૬૪.	જો $C_1=10\mu F$, $C_2=10\mu F$ પેરેલલમાં જોડવામાં આવેતો ટોટલ કેપેસિટન્સ C શોધો.			
	A.	$20\mu F$	B.	$100\mu F$
	C.	$5\mu F$	D.	$10\mu F$
૬૫.	હાફવેવ રેક્ટીફાયરમાં ડાયોડનો PIV શોધો.			
	A.	$2V_m$	B.	$2V_m/\pi$
	C.	V_m	D.	V_m/π
૬૬.	બ્રિજ રેક્ટીફાયરમાં ડાયોડનો PIV શોધો			
	A.	$2V_m$	B.	$2V_m/\pi$
	C.	V_m	D.	V_m/π
૬૭.	ડાયોડની ઉપયોગીતા _____ છે .			
	A.	ક્લેમ્પર	B.	ક્લીપર
	C.	સ્વીચ	D.	આપેલી બધી જ
૬૮.	કયા ડાયોડને વેરીએબલ કેપેસિટર ડાયોડ કહેવાય છે?			
	A.	એલઈડી	B.	ફોટો ડાયોડ
	C.	ટનલ ડાયોડ	D.	વેરેક્ટર ડાયોડ
૬૯.	જો $L_1=10H$, $L_2=10H$ પેરેલલમાં જોડવામાં આવેતો ટોટલ ઈન્ડક્ટન્સ શોધો .			
	A.	$5H$	B.	$20H$
	C.	$100H$	D.	$1H$
૭૦.	જો $L_1=10H$, $L_2=10H$ સીરીઝમાં જોડવામાં આવેતો ટોટલ ઈન્ડક્ટન્સ શોધો .			
	A.	$5H$	B.	$20H$
	C.	$100H$	D.	$1H$
