

GUJARAT TECHNOLOGICAL UNIVERSITY
DIPLOMA ENGINEERING - SEMESTER-III • EXAMINATION – WINTER • 2014

Subject Code: 331101**Date: 27-11-2014****Subject Name: Electronics Devices and Circuits - II****Time: 10:30 am - 01:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is considered to be Authentic.

- Q.1** (a) Explain advantages of Negative Feedback. **07**
(b) Give classification of Oscillator. Explain Hartley Oscillator. **07**
- Q.2** (a) Obtain the expression of efficiency of class B Push-pull amplifier and from that obtain the value of maximum efficiency. **07**
(b) Write short-note on Bistable Multivibrator. **07**
- OR
- (b) Give difference between Voltage Amplifier and Power Amplifier. **07**
- Q.3** (a) Explain the Integrating Circuit with the input and output waveforms. **07**
(b) Draw the circuit of Common Source Amplifier using JFET and explain its working. **07**
- OR
- Q.3** (a) Write short-note on MOSFET. **07**
(b) Give difference between class A transformer coupled and push-pull Amplifier. **07**
- Q.4** (a) Draw and explain the functional block diagram of IC 555. **07**
(b) Explain Inverting Amplifier and Non-inverting Amplifier using Op-amp. **07**
- OR
- Q. 4** (a) Give requirements for oscillations and Explain Wein bridge Oscillator. **07**
(b) Explain class A power amplifier with Transformer coupled load. **07**
- Q.5** (a) Give applications of Op-amp. Explain Differentiator Circuit using IC 741. **07**
(b) Discuss Astable Multivibrator using Transistor. **07**
- OR
- Q.5** (a) Write short-note on : **07**
1) JFET 2) Summing Amplifier
(b) Draw and explain circuit diagram of Current Series and Voltage Shunt type of feedback amplifier. **07**

ગુજરાતી

- પ્રશ્ન. ૧ અ નેગેટીવ ફીડ બેક નાં ફાયદા સમજાવો. ૦૭
બ ઓસિલેટર નું વર્ગીકરણ આપો. Hartley Oscillator સમજાવો. ૦૭

- પ્રશ્ન. ૨ અ ક્લાસ બી પુશ-પુલ એમ્પ્લિફાયરની કાર્યક્ષમતાનું સુત્ર તારવો અને તેનો ઉપયોગ કરી મહત્તમ કાર્યક્ષમતાની કિંમત શોધો. ૦૭
બ ટ્રંક નોંધ લખો: Bistable Multivibrator ૦૭

અથવા

- બ વોલ્ટેજ એમ્પ્લિફાયર અને પાવર એમ્પ્લિફાયર વચ્ચેનો તફાવત આપો. ૦૭
પ્રશ્ન. ૩ અ Integrating Circuit તેના ઇનપુટ અને આઉટપુટ વેવફોર્મ સાથે સમજાવો. ૦૭
બ કોમન સોર્સ એમ્પ્લિફાયરની સર્કિટ JFET ની મદદથી દોરો અને તેનું કાર્ય સમજાવો. ૦૭

અથવા

- પ્રશ્ન. ૩ અ ટ્રંક નોંધ લખો : MOSFET ૦૭
બ ક્લાસ એ ટ્રાંસફોર્મર કપલ્ડ અને પુશ-પુલ એમ્પ્લિફાયર વચ્ચેનો તફાવત આપો. ૦૭
પ્રશ્ન. ૪ અ IC555 ની ખંડીય આકૃતિ દોરી સમજાવો. ૦૭
બ Inverting Amplifier અને Non-Inverting Amplifier Op-amp ની મદદથી સમજાવો. ૦૭

અથવા

- પ્રશ્ન. ૪ અ Oscillations ની જરૂરીયાતો આપો અને Wein Bridge Oscillator સમજાવો. ૦૭
બ ક્લાસ એ પાવર એમ્પ્લિફાયરને ટ્રાંસફોર્મર કપલ્ડ લોડની મદદથી સમજાવો. ૦૭
પ્રશ્ન. ૫ અ Op-ampના ઉપયોગો આપો. Differentiator પરિપથને IC741ની મદદથી સમજાવો. ૦૭
બ ટ્રાંઝિસ્ટર સાથેના Astable Multivibrator ની ચર્ચા કરો. ૦૭

અથવા

- પ્રશ્ન. ૫ અ ટ્રંક નોંધ લખો: ૦૭
૧. JFET ૨. Summing Amplifier
બ કરંટ સીરીઝ અને વોલ્ટેજ શંટ પ્રકાર નાં ફીડ-બેક એમ્પ્લિફાયર ને આકૃતિ દોરી સમજાવો. ૦૭
