

GUJARAT TECHNOLOGICAL UNIVERSITY**Diploma Engineering - SEMESTER-III • EXAMINATION – WINTER • 2014****Subject Code: 331103****Date: 11-12-2014****Subject Name: Electronics Network and Lines****Time: 10:30 am - 01:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is considered to be Authentic.

- Q.1** (a) State & Prove Maximum Power Transfer Theorem **07**
(b) Define the followings: **07**
Branch, Mesh, Node, Linear Network, Bilateral Element, Q-Factor, Resonance
- Q.2** (a) State and prove Thevenin's theorem. **07**
(b) Derive equations to convert π -type network into T-type network. **07**
OR
(b) Explain Kirchhoff's current & voltage laws with examples. **07**
- Q.3** (a) Explain MUTUAL INDUCTANCE & get the equation for "K". **07**
(b) A series RLC circuit has $R = 30 \Omega$, $L = 0.5 \text{ H}$ and $C = 5\mu\text{F}$. Calculate (i) Q-factor, (ii) Band Width (iii) upper cut-off and lower cut-off frequencies. **07**
OR
- Q.3** (a) For series R-L-C circuit get the equation for resonance frequency. Also show that it is an example of voltage amplifier circuit. **07**
(b) A coil with $R = 10 \Omega$, $L = 0.2 \text{ H}$ is connected in parallel with a capacitor $C = 20 \mu\text{F}$. Find (i) resonance frequency (ii) Q of coil (iii) band width. **07**
- Q.4** (a) Explain Symmetrical Lattice Attenuator With Required Equations. **07**
(b) Design a symmetrical π network if $R_0 = 600 \text{ ohms}$ and $D = 40 \text{ dB}$. **07**
OR
- Q.4** (a) Define Neper & Db. Get The Relation Between Them. **07**
(b) Design a symmetrical T attenuator if $R_0 = 600 \text{ ohms}$ and $D = 40 \text{ dB}$. **07**
- Q.5** (a) Give comparison of active filters and passive filters. **07**
(b) Explain the loading of telephone cable. **07**
OR
- Q.5** (a) Give classification of filters using definitions and characteristics graphs for each. **07**
(b) What is duality? Explain using a series R-L-C circuit & required equations. **07**

ગુજરાતી

- પ્રશ્ન. ૧ અ મેક્સીમમ પાવર ટ્રાંસફર થીયરમ લખો અને સાબીત કરો. ૦૭
બ વ્યાખ્યાયીત કરો: બ્રાંચ, મેશ, નોડ, લીનીયર નેટવર્ક, બાઈલેટરલ એલીમેન્ટ, ક્યુ-ફેક્ટર, રેઝોનન્સ ૦૭

- પ્રશ્ન. ૨ અ થેવેનીન્સ થીયરમ લખો અને સાબીત કરો. ૦૭
બ પાઈ-ટાઇપ નેટવર્કમાંથી ટી-ટાઇપ નેટવર્કના કન્વર્ઝનના સૂત્રો મેળવો. ૦૭

અથવા

- બ કીર્યોફના કરંટ અને વોલ્ટેજના નિયમો ઉદાહરણ સાથે સમજાવો. ૦૭
પ્રશ્ન. ૩ અ મ્યુચુઅલ ઇન્ડક્સ સમજાવો અને “K” નું સમીકરણ મેળવો. ૦૭
બ સીરીઝ RLC સર્કીટમાં $R = 30 \Omega$, $L = 0.5 \text{ H}$ અને $C = 5 \mu\text{F}$ છે. તેમાં (1) Q-ફેક્ટર (2) બેન્ડવીથ (3) અપરકટ ઓફ અને લોવરકટ ઓફ ફ્રીક્વન્સી શોધો. ૦૭

અથવા

- પ્રશ્ન. ૩ અ સીરીઝ RLC સર્કીટ માટે રેઝોનન્સ ફ્રીક્વન્સીનું સમીકરણ મેળવો. તે એક વોલ્ટેજ એમ્પ્લીફાયરનું ઉદાહરણ છે તેમ દર્શાવો. ૦૭
બ પેરેલલ સર્કીટમાં લગાવેલ કોઇલમાં $R = 10 \Omega$, $L = 0.2 \text{ H}$ છે. કેપેસિટરનો કેપેસિટન્સ $20 \mu\text{F}$ છે. તેમાં (1) રેઝોનન્સ ફ્રીક્વન્સી (2) કોઇલનો Q-ફેક્ટર (3) બેન્ડવીથ શોધો. ૦૭

- પ્રશ્ન. ૪ અ સીમેટ્રીકલ લેટાઇસ એટેન્યુટર જરૂરી સમીકરણો સાથે સમજાવો. ૦૭
બ જો $R_0 = 600 \text{ ohms}$ અને $D = 40 \text{ dB}$ હોય તો સીમેટ્રીકલ π નેટવર્ક દોરો. ૦૭

અથવા

- પ્રશ્ન. ૪ અ વ્યાખ્યા આપીને DB અને NEPER વચ્ચેનું સમીકરણ મેળવો. ૦૭
બ જો $R_0 = 600 \text{ ohms}$ અને $D = 40 \text{ dB}$ હોય તો સીમેટ્રીકલ T એટેન્યુટર દોરો. ૦૭

- પ્રશ્ન. ૫ અ એક્ટીવ અને પેસીવ ફીલ્ટરની સરખામણી કરો. ૦૭
બ ટેલીફોન કેબલનું લોડીંગ સમજાવો. ૦૭

અથવા

- પ્રશ્ન. ૫ અ વ્યાખ્યા આપો અને કેરેક્ટરીસ્ટીકના આલેખ વાપરીને ફીલ્ટરનું વર્ગીકરણ કરો. ૦૭
બ ડ્યુઆલીટી એટલે શું? જરૂરી સમીકરણોની મદદથી સીરીઝ R-L-C સર્કીટને તેની ડ્યુઅલ સર્કીટમાં ફેરવો. ૦૭
