

GUJARAT TECHNOLOGICAL UNIVERSITY**DIPLOMA ENGINEERING - SEMESTER-III • EXAMINATION – WINTER • 2014****Subject Code: 3332403****Date: 01-12-2014****Subject Name: Advance Electronic Devices and Circuit****Time: 10:30 am - 01:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make Suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Use of programmable and Communication aids are strictly prohibited.
5. Use of only simple calculator is permitted in Mathematics.
6. English version is authentic.

- Q.1** Answer any seven out of ten. **14**
1. Define: feedback
 2. Write advantages of negative voltage feedback.
 3. Define: power amplifier.
 4. Draw output characteristics of common emitter circuit with load line.
 5. Define: Time constant.
 6. Define: duty Cycle.
 7. Define: photo electric Effect.
 8. Draw a symbol of - 1) photo Diode 2) photo transistor.
 9. Draw symbol of - 1) N-channel JFET 2) P-Channel E-MOSFET.
 10. FET has a $V_p = 6V$ and $I_{dss} = 100 \text{ mA}$. Find out 1) R_{ds} 2) Gate cut-off Voltage.
- Q.2** (a) Classify Oscillator. **03**
- OR
- (a) Explain operation of LC Tank circuit with Circuit diagram. **03**
- (b) Draw and discuss basic RC phase shift network for RC phase shift oscillator. **03**
- OR
- (b) Draw and discuss Basic circuit of wien bridge oscillator. **03**
- (c) Explain Transistorized Hartly oscillator with circuit diagram **04**
- OR
- (c) Explain Transistorized Colpitts oscillator with circuit diagram **04**
- (d) Explain RC coupling for two stage amplifier with circuit diagram. **04**
- OR
- (d) Explain Transformer coupling for two stage amplifier with circuit diagram. **04**
- Q.3** (a) Write advantages and applications of multi stage amplifier. **03**
- OR
- (a) Compare coupling methods for multistage amplifier with any three points. **03**
- (b) Draw Drain curve (I_d Verses V_{ds}) for N-channel JFET with different Gate-Source voltage. **03**
- OR
- (b) Draw Drain curve (I_d Verses V_{ds}) for N-channel E-MOSFET with different Gate-Source voltage. **03**
- (c) Explain working of Opto-coupler with circuit diagram. **04**
- OR
- (c) Explain working of Solar cell with circuit diagram. **04**
- (d) Explain working of IC 555 As a Monostable mode operation. **04**
- OR

	(d) Explain working of IC 555 As a Astable mode operation.	04
Q.4	(a) Compare Class A, Class B and Class AB Power amplifier with any three points.	03
	OR	
	(a) Explain Waveforms representing working of class A power amplifier operation.	03
	(b) Describe RC Differentiator using circuit diagram.	04
	OR	
	(b) Describe RC Integrator using circuit diagram.	04
	(c) Explain Push Pull Class B amplifier circuit diagram and various waveforms.	07
Q.5	(a) Explain direct coupling for two stage amplifier with circuit diagram.	04
	(b) Draw construction of 1) Depletion mode MOSFET. 2) Enhancement mode MOSFET.	04
	(c) Define: Schmitt trigger. Draw Schmitt trigger circuit.	03
	(d) Write any one application of 1)Photo transistor 2)Solar cell 3) Opto coupler	03

ગુજરાતી

પ્રશ્ન. ૧	દશમાંથી કોઇપણ સાતના જવાબ આપો.	૧૪
	૧. વ્યાખ્યાયીત કરો: ફીડબેક.	
	૨. નેગેટિવ વોલ્ટેજ ફીડબેક ના ફાયદા જણાવો.	
	૩. વ્યાખ્યાયીત કરો: પાવર એમ્પ્લિફાયર.	
	૪. લોડ લાઈન સાથે કોમન એમીટર સર્કિટ ની આઉટપુટ લાક્ષણિકતા દોરો.	
	૫. વ્યાખ્યાયીત કરો: ટાઈમ કોન્સ્ટન્ટ.	
	૬. વ્યાખ્યાયીત કરો: ડ્યુટી સાઈકલ.	
	૭. વ્યાખ્યાયીત કરો: ફોટો ઇલેક્ટ્રિક ઈફેક્ટ.	
	૮. સંજ્ઞા દોરો: 1) ફોટો ડાયોડ 2) ફોટો ટ્રાંસિસ્ટર	
	૯. સંજ્ઞા દોરો: 1)N- ચેનલ JFET 2) P-ચેનલ E-MOSFET.	
	૧૦ FET ને $V_p = 6V$ અને $I_{dss} = 100\text{ mA}$ છે તો 1) R_{ds} 2) ગેટ કટ ઓફ વોલ્ટેજ શોધો.	
પ્રશ્ન. ૨	અ ઓસ્સિલેટર ને વર્ગીકૃત કરો.	૦૩
	અથવા	
	અ LC ટેંક સર્કિટ ડાયાગ્રામ સાથે સમજાવો.	૦૩
	બ RC ફેઝ સીફ્ટ ઓસ્સિલેટર માટેની બેઝીક સર્કિટ દોરી સમજાવો.	૦૩
	અથવા	
	બ વેઈન બ્રિજ ઓસ્સિલેટર માટેની બેઝીક સર્કિટ દોરી સમજાવો.	૦૩
	ક ટ્રાંસિસ્ટર વાળુ હાર્ટલી ઓસ્સિલેટર દોરી સમજાવો.	૦૪
	અથવા	
	ક ટ્રાંસિસ્ટર વાળુ કોલ્પીટ ઓસ્સિલેટર દોરી સમજાવો.	૦૪
	ડ બે સ્ટેજ એમ્પ્લિફાયર માટે RC કપ્લિંગ સર્કિટ ડાયાગ્રામ સાથે સમજાવો.	૦૪

	અથવા		
	ડ બે સ્ટેજ એમ્પ્લિફાયર માટે ટ્રાંસ્ફોર્મર કપ્લીંગ સર્કિટ ડાયાગ્રામ સાથે સમજાવો.	0૪	
પ્રશ્ન. ૩	અ મલ્ટી સ્ટેજ એમ્પ્લિફાયર ના ફાયદા અને ઉપયોગીતા લખો.	0૩	
	અથવા		
	અ કોઈપણ ત્રણ મુદ્દા સાથે મલ્ટી સ્ટેજ એમ્પ્લિફાયર ની જોડાવાની રીત સરખાવો.	0૩	
	બ જુદા-જુદા ગેટ સોર્સ વોલ્ટેજ માટે N-ચેનલ JFET માટે ડ્રેઈન કર્વ દોરો.	0૩	
	અથવા		
	બ જુદા-જુદા ગેટ સોર્સ વોલ્ટેજ માટે N-ચેનલ E-MOSFET માટે ડ્રેઈન કર્વ દોરો.	0૩	
	ક સર્કિટ ડાયાગ્રામ સાથે ઓપ્ટો કપ્લર નુ કાર્ય સમજાવો.	0૪	
	અથવા		
	ક સર્કિટ ડાયાગ્રામ સાથે સોલર સેલ નુ કાર્ય સમજાવો.	0૪	
	ડ મોનો સ્ટેબલ કાર્ય માટે IC 555 નુ કાર્ય સમજાવો.	0૪	
	અથવા		
	ડ એસ્ટેબલ કાર્ય માટે IC 555 નુ કાર્ય સમજાવો.	0૪	
પ્રશ્ન. ૪	અ Class A, Class B અને Class AB પાવર એમ્પ્લીફાયરને કોઈપણ ત્રણ મુદ્દા સાથે સરખાવો.	0૩	
	અથવા		
	અ Class A પાવર એમ્પ્લિફાયર નુ કાર્ય દર્શાવતા વેવફોર્મ સમજાવો.	0૩	
	બ સર્કિટ ડાયાગ્રામ સાથે RC Differentiator વર્ણવો.	0૪	
	અથવા		
	બ સર્કિટ ડાયાગ્રામ સાથે RC Integrator વર્ણવો.	0૪	
	ક પુસપુલ ક્લાસ – B એમ્પ્લિફાયર ને સર્કિટ ડાયાગ્રામ અને જુદા જુદા વેવફોર્મ સાથે સમજાવો.	0૭	
પ્રશ્ન. ૫	અ બે સ્ટેજ એમ્પ્લિફાયર માટે ડાયરેક્ટ કપ્લીંગ સર્કિટ ડાયાગ્રામ સાથે સમજાવો.	04	
	બ માળખું દોરો. 1) ડેપ્લેશન મોડ MOSFET 2) એન્હાંસમેંટ મોડ MOSFET	04	
	ક સ્કિમટ ટ્રીગર વ્યાખ્યાયીત કરી ને તેની સર્કિટ દોરો.	0૩	
	ડ નીચેના ની કોઈ એક ઉપયોગીતા લખો. 1) ફોટો ટ્રાંસીસ્ટર 2)સોલર સેલ. 3) ઓપ્ટો કપ્લર	0૩	
