

GUJARAT TECHNOLOGICAL UNIVERSITY**Diploma Engineering - SEMESTER-IV • EXAMINATION – WINTER • 2014****Subject Code: 3340904****Date: 04-12-2014****Subject Name: Digital Electronics and Digital Instruments****Time: 02:30 pm - 05:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is considered to be Authentic.

- Q.1** (a) Attempt the following questions. **07**
- i) Obtain Excess-3 code for $(625)_{10}$.
 - ii) Convert $(BEC45)_{16}$ in to binary number.
 - iii) Convert $(0.875)_{10}$ in to binary number.
 - iv) Obtain the result for $(1.01)_2 * (10.1)_2$.
 - v) Obtain the 2's compliment for (1101) .
 - vi) Obtain BCD code for $(725)_{10}$.
 - vii) State the full form of ASCII.
- (b) Attempt the following questions.
- i) Compare LED with LCD. **03**
 - ii) Explain error correcting code. **04**
- Q.2** (a) Show that how NAND gate is universal gate. **07**
- (b) Explain working of transistor as a switch. **07**
- OR
- (b) Explain diode transistor logic with its merits and demerits. **07**
- Q.3** (a) Explain race around condition in JK flip flop and show how it is eliminated in master slave JK flip flop. **07**
- (b) Explain IC-7490 decade counter. **07**
- OR
- Q.3** (a) Explain random access memory with its classification. **07**
- (b) Explain 4-bit shift left register using J-K flip flop. **07**
- Q.4** (a) Draw circuit arrangement for decimal to BCD encoder and explain with truth table. **07**
- (b) Draw the logic diagram for the given Boolean expressions: **07**
- (i) $Y = \overline{A}\overline{D} + \overline{B}\overline{C}D + B\overline{C}D$ (ii) $Y = ABC + \overline{A}\overline{B}\overline{C}$
- OR
- Q. 4** (a) Draw logic diagram for half adder and full adder and explain with truth table. **07**
- (b) Applying laws of Boolean algebra prove that – **07**
- (i) $A + \overline{A}B + \overline{A}\overline{B} = A + B$ (ii) $AB + \overline{A}\overline{B} + \overline{A}B + \overline{A}\overline{B} + B = 1$
- Q.5** (a) Explain parallel comparator analog to digital converter. **07**
- (b) Draw the block diagram of digital frequency meter and explain working. **07**
- OR
- Q.5** (a) Explain seven segment LED display. **07**
- (b) Explain ramp type analogue to digital converter digital voltmeter. **07**

ગુજરાતી

પ્રશ્ન. ૧	અ	પ્રશ્નો ના જવાબ લખો.	૦૭
		i) $(625)_{10}$ માટે એક્સેસ-૩ કોડ મેળવો.	
		ii) $(BEC45)_{16}$ ને બાયનરી નંબર મા ફેરવો.	
		iii) $(0.875)_{10}$ ને બાયનરી નંબર મા ફેરવો.	
		iv) $(1.01)_2 * (10.1)_2$ નું પરિણામ મેળવો.	
		v) (1101) નું 2's કોમ્પ્લીમેન્ટ મેળવો.	
		vi) $(725)_{10}$ માટે BCD કોડ મેળવો.	
		vii) ASCII નું આખું નામ લખો.	
	બ	પ્રશ્નો ના જવાબ લખો.	૦૩
		i) LED અને LCD ની સરખામણી કરો. ii) એરર કરેક્ટીંગ કોડ સમજાવો.	૦૪
પ્રશ્ન. ૨	અ	NAND ગેટ એ યુનિવર્સલ ગેટ છે તે સાબિત કરો.	૦૭
	બ	ટ્રાન્ઝીસ્ટરનું સ્વીચ તરીકે કાર્ય સમજાવો.	૦૭
		અથવા	
	બ	ડાયોડ - ટ્રાન્ઝીસ્ટર લોજીક તેના ફાયદા અને ગેર ફાયદા સહિત સમજાવો.	૦૭
પ્રશ્ન. ૩	અ	જે કે ફ્લોપ- ફ્લોપ માં રેસ અરાઉન્ડ કંડિશન સમજાવો અને માસ્ટર સ્લેવ જે કે ફ્લોપ- ફ્લોપ માં તે કેવી રીતે દૂર થાય છે તે સમજાવો.	૦૭
	બ	IC-7490 ને ડીકેડ કાઉન્ટર તરીકે સમજાવો.	૦૭
		અથવા	
પ્રશ્ન. ૩	અ	રેન્ડમ એક્સેસ મેમરી તેના વર્ગીકરણ સહિત સમજાવો.	૦૭
	બ	જે કે ફ્લોપ- ફ્લોપ ની મદદ થી ૪-બીટ શીફ્ટ લેફ્ટ રજીસ્ટર સમજાવો.	૦૭
પ્રશ્ન. ૪	અ	ડેસીમલ થી બીસીડી એનકોડર ની સર્કીટ દોરો અને ટ્રુથ ટેબલ ની મદદ થી સમજાવો.	૦૭
	બ	આપેલ બૂલીયન સમીકરણ માટે લોજીક ડાયાગ્રામ દોરો -	૦૭
		(i) $Y = \overline{A}D + \overline{B}CD + BCD$ (ii) $Y = ABC + \overline{A}\overline{B}\overline{C}$	
		અથવા	
પ્રશ્ન. ૪	અ	હાફ એડર અને ફૂલ એડર નોલોજીક ડાયાગ્રામ દોરો અને તેના ટ્રુથ ટેબલ સાથે સમજાવો.	૦૭
	બ	બૂલીયન એલ્જીબ્રા ના નિયમો થી સાબિત કરો -	૦૭
		(i) $A + \overline{A}B + A\overline{B} = A + B$ (ii) $AB + \overline{A}B + A\overline{B} + \overline{A}\overline{B} + B = 1$	
પ્રશ્ન. ૫	અ	પેરેલલ કંપેરેટર એનાલોગ ટુ ડીજીટલ કન્વર્ટર સમજાવો.	૦૭
	બ	ડીજીટલ ફ્રીક્વેન્સી મીટર નો બ્લોક ડાયાગ્રામ દોરો અને તેનું કાર્ય સમજાવો.	૦૭
		અથવા	
પ્રશ્ન. ૫	અ	સેવન સેગમેન્ટ એલ.ઇ.ડી. ડીસ્પ્લે સમજાવો.	૦૭
	બ	રેમ્પ ટાઇપ એનાલોગ ટુ ડીજીટલ કન્વર્ટર ડીજીટલ વોલ્ટમીટર સમજાવો.	૦૭
