

GUJARAT TECHNOLOGICAL UNIVERSITY
DIPLOMA ENGINEERING - SEMESTER-V • EXAMINATION – WINTER • 2014

Subject Code: 350902**Date: 28-11-2014****Subject Name: Industrial Electronics****Time: 10:30 am - 01:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is considered to be Authentic.

- Q.1** (a) Write the advantages of poly phase rectifier over single phase rectifier and list applications of poly phase rectifier. **07**
- (b) Explain the working of six phase half wave rectifier with the help of circuit diagram and waveforms. Write the expressions for E_{dc} and ripple factor. **07**
- Q.2** (a) Draw and explain the circuit for the speed control of 1- Φ A.C. motor using two SCRs connected back to back and one UJT. **07**
- (b) Explain the construction and working principle of following device. **07**
(1) DAIC (2) TRIAC
- OR**
- (b) Explain the speed control of D.C. motor using SCR and UJT with neat circuit diagram. **07**
- Q.3** (a) Draw the circuit diagram of parallel inverter and explain its working. **07**
- (b) Explain construction, working and Turn on, Turn off process of MCT. **07**
- OR**
- Q.3** (a) State the different methods used to turn off SCR. Explain class B commutation with circuit diagram. **07**
- (b) Explain the speed control of slip ring induction motor by using chopper circuit. **07**
- Q.4** (a) Explain working principle of chopper. Draw and explain the circuit of class B chopper. **07**
- (b) Write basic properties of X-rays. Explain medical and industrial applications of X-rays. **07**
- OR**
- Q.4** (a) Explain the advantages and disadvantages of induction heating and state the applications of induction heating. **07**
- (b) Explain the block diagram of resistance welding. **07**
- Q.5** (a) Explain the sequential timer circuit using IC 555 for welding sequence with the aid of circuit diagram. **07**
- (b) Write short notes on (1) photo voltaic cell (2) Twilight switch circuit. **07**
- OR**
- Q.5** (a) Explain flame failure circuit using LDR and SCR. **07**
- (b) Explain construction and working of constant voltage transformer. **07**

પ્રશ્ન-૧	અ	પોલીફેઇઝ રેક્ટીફાયર ના સીંગલ ફેઇઝ રેક્ટીફાયર ઉપર થતા ફાયદા લખો અને પોલીફેઇઝ રેક્ટીફાયર ના ઉપયોગો જણાવો.	૦૭
	બ	સરકીટ ડાયાગ્રામ અને વેવફોર્મ ની મદદ થી છ ફેઝ હાફ વેવ રેક્ટીફાયર નું કાર્ય સમજાવો.તથા E_{dc} અને રીપલ ફેક્ટર ના સુત્રો લખો.	૦૭
પ્રશ્ન-૨	અ	બે SCR બેક ટુ બેક જોડ્યા હોય તેવી અને UJT નો ઉપયોગ કરીને 1- Φ A. C. મોટરના સ્પીડ કંટ્રોલની સરકીટ દોરી સમજાવો.	૦૭
	બ	નીચેની ડીવાઈસ ની રચના અને કાર્યસિધ્ધાંત સમજાવો.(1) ડાયક (2)ટ્રાયક	૦૭
		અથવા	
	બ	SCR અને UJT નો ઉપયોગ કરીને D. C. મોટરના સ્પીડ કંટ્રોલની સરકીટ દોરી સમજાવો.	૦૭
પ્રશ્ન-૩	અ	પેરેલલ ઈંવર્ટર નો સરકીટ ડાયાગ્રામ દોરી તેનું કાર્ય સમજાવો.	૦૭
	બ	MCT ની રચના, કાર્ય, ટર્ન ઓન અને ટર્ન ઓફ પ્રોસેસ સમજાવો.	૦૭
		અથવા	
પ્રશ્ન-૩	અ	SCR ને ટર્ન ઓફ કરવા માટેની જુદીજુદી રીતો લખો અને સરકીટ ડાયાગ્રામ દોરી ક્લાસ બી કોમ્યુટેશન સમજાવો.	૦૭
	બ	ચોપર સરકીટ નો ઉપયોગ કરી ને સ્લીપ રીંગ ઈંડક્શન મોટર નો સ્પીડ કંટ્રોલ સમજાવો.	૦૭
પ્રશ્ન-૪	અ	ચોપર નો કાર્યસિધ્ધાંત સમજાવો અને ક્લાસ બી ચોપર ની સરકીટ દોરી સમજાવો.	૦૭
	બ	ક્ષ-કિરણો ના મુળભૂત ગુણધર્મો લખો અને તેના મેડિકલ તેમજ ઈંડસ્ટ્રીયલ ઉપયોગો સમજાવો.	૦૭
		અથવા	
પ્રશ્ન-૪	અ	ઈંડક્શન હીટીંગ ના ફાયદા તથા ગેરફાયદા સમજાવો અને તેના ઉપયોગો લખો.	૦૭
	બ	રેજુસ્ટંસ વેલ્ડીંગ નો બ્લોક ડાયાગ્રામ સમજાવો.	૦૭
પ્રશ્ન-૫	અ	વેલ્ડીંગ સીકવંસ માટે ની, IC 555 નો ઉપયોગ કરેલી, સીકવંસીયલ ટાઈમર સરકીટ દોરી અને સમજાવો.	૦૭
	બ	ટ્રંક નોન્ડ લખો. (1) ફોટો વોલ્ટાઈક સેલ (2) ટવીલાઈટ સ્વીચ સરકીટ	૦૭
		અથવા	
પ્રશ્ન-૫	અ	LDR અને SCR નો ઉપયોગ કરી ને ફ્લેમ ફેઈલ્યોર સરકીટ સમજાવો.	૦૭
	બ	કોંસ્ટંટ વોલ્ટેજ ટ્રાંસફોર્મર ની રચના અને કાર્ય સમજાવો.	૦૭
