

**GUJARAT TECHNOLOGICAL UNIVERSITY**  
**DIPLOMA ENGINEERING – SEMESTER – V • EXAMINATION – WINTER • 2014**

**Subject Code: 350904****Date: 04-12-2014****Subject Name: Digital Electronics and Digital Instrument****Time: 10:30 am - 01:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is considered to be Authentic.

- Q.1** (a) Explain Error Correcting Code with example. **07**  
 (b) Draw circuit of positive edge triggered JK flip-flop and explain it with truth table. **07**
- Q.2** (a) i) Subtract using 2's complement form:  $(01010101)_2 - (11101110)_2$  **07**  
 ii) Convert  $(11011)_{GRAY} = ( )_2$   
 (b) Explain a Diode Negative Clipper circuit and draw its input and output waveforms **07**
- OR
- (b) Explain the working of a digital energy meter, with the help of a block diagram. **07**
- Q.3** (a) Prove that NAND gate is Universal gate with truth tables **07**  
 (b) Prove that :  $AB + A\bar{C} + A\bar{B}C(AB + C) = 1$  **07**
- OR
- Q.3** (a) Explain TTL NAND gate with totem pole output **07**  
 (b) Explain working of 4 bit parallel binary adder/subtractor circuit **07**
- Q.4** (a) Explain Staircase type of A/D converter **07**  
 (b) Draw the block diagram of digital frequency meter and explain its working **07**
- OR
- Q. 4** (a) Draw and explain the R-2R ladder D/A converter. **07**  
 (b) Draw block diagram of Digital voltmeter using dual slope A/D converter and explain its working. **07**
- Q.5** (a) What are the different types of Shift Registers? Explain them in brief. **07**  
 (b) Give comparison between static RAM & dynamic RAM. **07**
- OR
- Q.5** (a) Explain with the help of a block diagram BCD to decimal decoder also give its truth table **07**  
 (b) Explain the types of LCD. **07**

પ્રશ્ન. ૧ અ ઉદાહરણ સાથે ભૂલ સુધારવી (Error Correcting) કોડ સમજાવો ૦૭  
 બ પોઝીટીવ એજ ટ્રિગલ જે કે ફ્લિપ-ફ્લોપ ની સર્કિટ દોરો અને ટ્રુથ ટેબલ સાથે સમજાવો ૦૭

પ્રશ્ન. ૨ અ i) 2'sના કોમ્પ્લીમેન્ટ રીત થી  $(11101110)_2$  ને  $(01010101)_2$  માંથી બાદ કરો ૦૭  
 ii)  $(11011)_{GRAY}$  ને બાયનરી નબંર માં ફેરવો.  
 બ ડાયોડ Negative ક્લીપર સરકીટ ઈનપુટ અને આઉટપુટ વેવફોર્મ સાથે સમજાવો. ૦૭

અથવા

બ બ્લોકડાયાગ્રામ દોરી ડીજીટલ ફ્રીક્વન્સીમીટર નું કાર્ય સમજાવો. ૦૭  
 પ્રશ્ન. ૩ અ સાબીત કરો ટ્રુથ ટેબલ સાથે કે NAND ગેટ એ Universal ગેટ છે. ૦૭  
 બ સાબીત કરો  $AB + A\bar{C} + A\bar{B}C(AB + C) = 1$  ૦૭

અથવા

પ્રશ્ન. ૩ અ ટોટેમ પોલ આઉટપુટ સાથે TTL NAND ગેટ સમજાવો . ૦૭  
 બ 4 બીટ સમાંતર બાઈનરી adder / subtractor સર્કિટ નું કામ સમજાવો ૦૭  
 પ્રશ્ન. ૪ અ એ / ડી કન્વર્ટર ના દાદરા પ્રકાર સમજાવો ૦૭  
 બ ડિજિટલ ફ્રીક્વન્સી મીટર બ્લોક ડાયાગ્રામ દોરો અને તેના કામ સમજાવો ૦૭

અથવા

પ્રશ્ન. ૪ અ દોરો અને આર 2R લેડર ડી / એ કન્વર્ટર સમજાવો ૦૭  
 બ ડ્યુઅલ slope A/D કન્વર્ટર મદદથી Digital voltmeter ના બ્લોક ડાયાગ્રામ દોરો અને તેના કામ સમજાવો. ૦૭  
 પ્રશ્ન. ૫ અ શીફ્ટ રજિસ્ટર્સ વિવિધ પ્રકારની શું છે? તેમને સંક્ષિપ્ત માં સમજાવો. ૦૭  
 બ સ્ટેટિક RAM અને ડાયનેમિક RAM વચ્ચે સરખામણી આપો. ૦૭

અથવા

પ્રશ્ન. ૫ અ BCD થી decimal decoder માટે નું બ્લોક ડાયાગ્રામ truth table સાથે સમજાવો ૦૭  
 બ એલસીડી ના પ્રકારો સમજાવો. ૦૭

\*\*\*\*\*

