

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY

Diploma Engineering - SEMESTER-II (CtoD) • EXAMINATION – WINTER • 2014

Subject Code: C320903**Date: 29-12-2014****Subject Name: D. C. CIRCUIT****Time: 10:30 am - 12:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumption wherever necessary.
3. Each question is of 1 mark.
4. Use of SIMPLE CALCULATOR is permissible. (Scientific/Higher Version not allowed)
5. English version is authentic.

No.	Question Text and Option			
1.	The unit Joule/Second is _____			
	A.	Watt	B.	Ohm
	C.	Volt	D.	Ampere
2.	1000 MΩ = _____ mΩ			
	A.	10 ³	B.	10 ⁶
	C.	10 ⁹	D.	10 ¹²
3.	The electric current is defined as _____			
	A.	Sec/coulomb	B.	Coulomb*sec
	C.	Coulomb/sec	D.	Coulomb ² /sec
4.	Which of the following materials does not follow Ohm's law?			
	A.	Nickle	B.	Silicon
	C.	Copper	D.	Aluminium
5.	Which of the following equation is true for electric power?			
	A.	$W=V^2/R$	B.	$W=V^2 \cdot R$
	C.	$W=R^2/V$	D.	$W=R^2 \cdot V$
6.	Value of α_0 for copper is _____ Ω/ Ω°C			
	A.	1/123.4	B.	1/23.45
	C.	1/234.5	D.	1/2345
7.	Unit of Resistivity is _____			
	A.	Ohm-meter	B.	Ohm/meter
	C.	Meter/ohm	D.	Ohm/mm
8.	The value of Joule's constant J is _____ joule/calorie			
	A.	4186	B.	41.86
	C.	4.186	D.	418.6
9.	To produce 1 kilo calorie heat _____ joule electrical work has to be done.			
	A.	4186	B.	41.86
	C.	4.186	D.	418.6
10.	1 kWh = _____ kilo calorie			
	A.	4186	B.	4.186
	C.	41.86	D.	860
11.	The basic unit of electric charge is _____			
	A.	Farad	B.	Coulomb
	C.	Ampere-hour	D.	Watt-hour
12.	Which of the following statement is True?			
	A.	Unit of emf is watt & potential difference is volt	B.	Unit of emf is volt & potential difference is volt

	C.	Unit of emf is volt & potential difference is watt	D.	Unit of emf is watt; potential difference is watt
13.	Which of the following statement is True? Unit of conductance is			
	A.	Ohm and symbol is G	B.	Ohm and symbol is R
	C.	Siemens and symbol is R	D.	Siemens and symbol is G
14.	For how many hours a 25 W lamp should be used so that 1 unit energy is consumed?			
	A.	40	B.	4
	C.	400	D.	4000
15.	Which of the following statement is True? The resistance of the conductor is			
	A.	Inversely proportional to length of conductor	B.	Inversely proportional to cross sectional area of conductor
	C.	Directly proportional to cross sectional area of conductor	D.	None of above
16.	When the diameter of conductor is doubled & length is increased four times, its resistance			
	A.	Will not change	B.	Will become four times
	C.	Will become half	D.	Will become double
17.	Rate of doing work is _____			
	A.	joule	B.	Potential
	C.	energy	D.	Power
18.	Three resistors of 20 Ω , 30 Ω & 50 Ω are connected in parallel. The equivalent resistance will be _____ Ω			
	A.	12	B.	18.75
	C.	9.67	D.	0.103
19.	Find the active element from following			
	A.	Capacitor	B.	Inductor
	C.	Resistor	D.	Current source
20.	Find the passive element from following			
	A.	Voltage source	B.	Battery
	C.	Resistor	D.	Current source
21.	Which one of the following statement is NOT true about network?			
	A.	Every mesh is loop	B.	Every loop is not mesh
	C.	Element connected between two node is called branch	D.	A network can not have both the voltage source and the current source
22.	When two equal values of resistors are connected in parallel, the equivalent resistance will be			
	A.	Greater than individual resistance	B.	Equal to value of each resistance
	C.	Less than individual resistance	D.	None of above
23.	Condition for maximum transfer of power from source to load is			
	A.	$R_L = \infty$	B.	$R_S > R_L$
	C.	$R_S < R_L$	D.	$R_S = R_L$
24.	Three resistors of 30 Ω are connected in delta. Each resistance of equivalent star connection will be _____ Ω .			
	A.	10 Ω	B.	30 Ω
	C.	90 Ω	D.	900 Ω
25.	Three resistors of 30 Ω are connected in star. Each resistance of equivalent delta connection will be _____ Ω .			
	A.	10 Ω	B.	30 Ω
	C.	90 Ω	D.	900 Ω
26.	A network in which the voltage current relations are same in either direction is called _____			
	A.	Unilateral network	B.	Symmetrical network
	C.	Linear network	D.	Bilateral network

27.	A network in which the voltage current relations are NOT same in either direction is called _____			
	A.	Unilateral network	B.	Symmetrical network
	C.	Linear network	D.	Bilateral network
28.	A network in which electrical properties are NOT changed when the input and output terminals are interchanged is called _____			
	A.	Unilateral network	B.	Symmetrical network
	C.	Linear network	D.	Bilateral network
29.	Equivalent current source of 30 V, 5Ω voltage source is _____			
	A.	30 A, 5Ω	B.	15 A, 10Ω
	C.	6 A, 5Ω	D.	15 A, 5Ω
30.	Equivalent voltage source of 10 A, 2Ω current source is _____			
	A.	10 V, 2Ω	B.	20 V, 2Ω
	C.	5 V, 1Ω	D.	5 V, 2Ω
31.	Capacitance is given by _____			
	A.	$C=Q*V$	B.	$C=Q+V$
	C.	$C=Q/V$	D.	$C=V/Q$
32.	Value of Permittivity ϵ_0 is _____ f/m			
	A.	8.854×10^{-11}	B.	8.854×10^{-12}
	C.	8.854×10^{-10}	D.	8.854×10^{-9}
33.	Which is the dual of Thevenin's theorem			
	A.	Superposition Theorem	B.	Maximum Power Transfer Theorem
	C.	Kirchhoff's Laws	D.	Norton's Theorem
34.	In Electrostatics electric flux is denoted by _____			
	A.	P	B.	Φ
	C.	Σ	D.	Ψ
35.	Coulomb/m ² is the unit of _____			
	A.	Electric field intensity	B.	Electric flux density
	C.	Electric charge	D.	Electric flux
36.	1 pF = _____			
	A.	10^{-12} F	B.	10^{-9} F
	C.	10^{-6} F	D.	10^{-3} F
37.	Energy stored by capacitor is given by _____ formula			
	A.	$\frac{1}{2} * Q/C$	B.	$\frac{1}{2} * Q/C^2$
	C.	$\frac{1}{2} * CV$	D.	$\frac{1}{2} * Q^2/C$
38.	Farad =			
	A.	Volt/coulomb ²	B.	Volt * coulomb
	C.	Coulomb/volt	D.	Volt/coulomb
39.	R-C Time constant is denoted by _____			
	A.	α	B.	β
	C.	θ	D.	λ
40.	The capacitance of a capacitor is NOT influenced by _____			
	A.	Plate area	B.	Plate thickness
	C.	Plate separation	D.	Nature of the dielectric
41.	A capacitor that stores a charge of 0.5 Coulomb at 10 volts has a capacitance of _____ farad.			
	A.	0.05	B.	20
	C.	10	D.	5

42.	The time constant of an R-C circuit is defined as the time during which capacitor charging current becomes _____ percent of its _____ value.			
	A.	63, final	B.	37, final
	C.	37, initial	D.	63, initial
43.	A capacitor consists of two _____			
	A.	Silver-coated insulators	B.	Ceramic plates and one mica disc
	C.	Conductors separated by an insulators	D.	Insulation separated by a dielectric
44.	When two capacitors of 8 μF connected in series the total capacitance will be _____			
	A.	16 μF	B.	8 μF
	C.	4 μF	D.	2 μF
45.	Dielectric constant $K =$ _____			
	A.	$4\pi * 10^{-7}$	B.	$1/4\pi\epsilon_0\epsilon_r$
	C.	$4\pi\epsilon_0\epsilon_r$	D.	$1/4\pi\epsilon_0\epsilon_r d^2$
46.	Charge of an electron is _____ Coulomb			
	A.	$1.602 * 10^{-18}$	B.	$1.602 * 10^{-19}$
	C.	$1.602 * 10^{-20}$	D.	$1.602 * 10^{-21}$
47.	Mass of an electron is _____ kg			
	A.	$9.108 * 10^{-31}$	B.	$9.108 * 10^{-32}$
	C.	$9.108 * 10^{-33}$	D.	$9.108 * 10^{-34}$
48.	When two capacitors of 8 μF connected in parallel the total capacitance will be			
	A.	16 μF	B.	8 μF
	C.	4 μF	D.	2 μF
49.	When three capacitors of 20 μF , 25 μF and 30 μF are connected in series, the equivalent capacitance will be _____			
	A.	25 μF	B.	75 μF
	C.	0.1233 μF	D.	8.11 μF
50.	Two capacitors of 50 μF each are connected in series and 200 Volt are applied. Then energy stored in each capacitor will be _____ joule.			
	A.	2	B.	1
	C.	0.5	D.	0.25
51.	Unit of magnetic flux is _____			
	A.	Tesla	B.	Ampere-turn
	C.	Weber	D.	Coulomb
52.	The magnetising force (H) and magnetic flux density (B) are given by _____ relation			
	A.	$B = H/\mu_0 \mu_r$	B.	$B = \mu H$
	C.	$B = \mu_0 H/\mu_r$	D.	$B = \mu_r H/\mu_0$
53.	Dynamically induced emf is given by _____			
	A.	$BIL\sin\theta$	B.	$BLV\cos\theta$
	C.	$BLV\sin\theta$	D.	NdI/dt
54.	Which is the true formula from the following?			
	A.	$\mu=\mu_0 \mu_r$	B.	$\mu=\mu_0 \mu_r/2$
	C.	$\mu=\sqrt{\mu_0 \mu_r}$	D.	$\mu=(\mu_0+\mu_r)/2$
55.	Direction of dynamically induced emf can be found by using _____			
	A.	Cork screw rule	B.	Fleming's right hand rule
	C.	Fleming's left hand rule	D.	Right hand rule
56.	Value of self induced emf is _____			
	A.	Directly proportional to the square of number of turns of coil	B.	Directly proportional to number of turns of coil
	C.	Inversely proportional to the	D.	Inversely proportional to number of

		square of number of turns of coil		turns of coil
57.	Area of hysteresis loop			
	A.	Shows only eddy current loss	B.	Is less when hysteresis loss is more
	C.	Shows only hysteresis loss	D.	Shows both hysteresis and eddy current loss
58.	According to Faraday's Law of Electromagnetic induction, an e.m.f. is induced in a conductor whenever it			
	A.	Lies in a magnetic field	B.	Moves parallel to the direction of magnetic field
	C.	Cuts magnetic flux	D.	Lies perpendicular to magnetic flux
59.	The magnitude of the induced e.m.f. in a conductor depends on _____			
	A.	Amount of flux-linkages	B.	Amount of flux cut
	C.	Flux density of magnetic field	D.	Rate of change of flux-linkages
60.	Coefficient of coupling is given by _____			
	A.	$k=M/\sqrt{L_1+L_2}$	B.	$k=M/\sqrt{L_1-L_2}$
	C.	$k=M/\sqrt{L_1L_2}$	D.	$k=\sqrt{L_1L_2}/M$
61.	Higher the self inductance of a coil			
	A.	Greater the flux produced by it	B.	Lesser its weber-turns
	C.	Lower the e.m.f. induced in it.	D.	Longer the delay in establishing steady current through it
62.	Mutual inductance between two magnetically coupled coils depends on _____			
	A.	The number of their turns	B.	Cross-sectional area of their common core
	C.	Permeability of the core	D.	All of the above
63.	Permanent magnets are normally made of _____			
	A.	Cast iron	B.	Alnico alloys
	C.	Wrought iron	D.	Aluminium
64.	Those magnetic materials are best suited for making armature and transformer cores which have _____ permeability and _____ hysteresis loss.			
	A.	High, low	B.	High, high
	C.	Low, high	D.	Low, low
65.	In a magnetic material, hysteresis loss takes place primarily due to _____			
	A.	Its high retentivity	B.	Molecular friction
	C.	Rapid reversals of its magnetisation	D.	Flux density lagging behind magnetising force
66.	Energy stored in a magnetic field is given by _____			
	A.	$\frac{1}{2} \cdot LI$	B.	$\frac{1}{2} \cdot L^2 I$
	C.	$\frac{1}{2} \cdot LI^2$	D.	$\frac{1}{2} \cdot L^2 I^2$
67.	Which of the following formula used for self induction of a coil?			
	A.	$N\phi^2/I$	B.	$N^2\phi/I$
	C.	NI^2/ϕ	D.	$N\phi/I$
68.	The lifting power of an electromagnetic depends on _____			
	A.	Magnetic flux density	B.	Its pole area
	C.	Both (A) and (B)	D.	Its shape
69.	Inductance of a coil having 100 turns is 500 mH. To produce 2 mWb flux, the current required to be passed is _____ A			
	A.	40	B.	4
	C.	0.4	D.	0.04
70.	Inductance in series given by which of the following formula?			
	A.	$L = L_1 - L_2 - M$	B.	$L = L_2 - L_1 - M$

C.	$L = L_1 + L_2 \pm 2M$	D.	All of the above
----	------------------------	----	------------------

ગુજરાતી

નં.	પ્રશ્ન તેમજ વિકલ્પ		
1.	એકમ જુલ/સેકન્ડ એટલે _____		
	A.	વોટ	B. ઓહ્મ
	C.	વોલ્ટ	D. એમ્પિયર
2.	$1000 \text{ M}\Omega = \text{_____ m}\Omega$		
	A.	10^3	B. 10^6
	C.	10^9	D. 10^{12}
3.	વિદ્યુતપ્રવાહ _____ રીતે વ્યાખ્યાયિત થાય છે.		
	A.	સેકન્ડ/કુલંબ	B. કુલંબ*સેકન્ડ
	C.	કુલંબ/સેકન્ડ	D. કુલંબ ² /સેકન્ડ
4.	નીચેનામાંથી કયું મટીરીયલ ઓહ્મના નિયમને અનુસરતું નથી?		
	A.	નિકલ	B. સિલિકોન
	C.	કોપર	D. એલ્યુમિનિયમ
5.	નીચેના પૈકી કયું સૂત્ર ઇલેક્ટ્રિક પાવર માટે સાચું છે?		
	A.	$W = V^2/R$	B. $W = V^2 * R$
	C.	$W = R^2/V$	D. $W = R^2 * V$
6.	કોપર માટે α_0 ની કિંમત _____ $\Omega/\Omega/^\circ\text{C}$ છે.		
	A.	1/123.4	B. 1/23.45
	C.	1/234.5	D. 1/2345
7.	વિશિષ્ટ અવરોધનો એકમ _____ છે.		
	A.	ઓહ્મ-મીટર	B. ઓહ્મ/મીટર
	C.	મીટર/ઓહ્મ	D. ઓહ્મ/મિમી
8.	જુલના અચળાંકની કિંમત _____ જુલ/કેલરી છે.		
	A.	4186	B. 41.86
	C.	4.186	D. 418.6
9.	1 કિલો કેલરી ઉષ્મા ઉત્પન્ન કરવા માટે _____ જુલ ઇલેક્ટ્રિક કાર્ય કરવું જોઈએ.		
	A.	4186	B. 41.86
	C.	4.186	D. 418.6
10.	1 કિલો વોટ અવર = _____ કિલો કેલરી		
	A.	4186	B. 4.186
	C.	41.86	D. 860
11.	ઇલેક્ટ્રિક ચાર્જનો મૂળ એકમ _____ છે		

	A.	ફેરડ	B.	કુલંબ
	C.	એમ્પિયર-અવર	D.	વોટ-અવર
12.	નીચેનામાંથી કયું વિધાન સાચું છે?			
	A.	વીજ ચાલક બળનો એકમ વોટ છે અને પોટેન્શીયલ તફાવતનો એકમ વોલ્ટ છે	B.	વીજ ચાલક બળનો એકમ વોલ્ટ છે અને પોટેન્શીયલ તફાવતનો એકમ વોલ્ટ છે
	C.	વીજ ચાલક બળનો એકમ વોલ્ટ છે અને પોટેન્શીયલ તફાવતનો એકમ વોટ છે	D.	વીજ ચાલક બળનો એકમ વોટ છે અને પોટેન્શીયલ તફાવતનો એકમ વોટ છે
13.	નીચેના પૈકી કયું વિધાન સાચું છે? વાહકત્વનો એકમ			
	A.	ઓહ્મ અને સંજ્ઞા G છે	B.	ઓહ્મ અને સંજ્ઞા R છે
	C.	સિમેંસ અને સંજ્ઞા R છે	D.	સિમેંસ અને સંજ્ઞા G છે
14.	25 Wનો લેમ્પ કેટલા કલાક વાપરીએ તો 1 યુનીટ શક્તિ વપરાય?			
	A.	40	B.	4
	C.	400	D.	4000
15.	નીચેના પૈકી કયું વિધાન સાચું છે? વાહકનો અવરોધ			
	A.	વાહકની લંબાઈના વ્યસ્ત પ્રમાણમાં હોય છે	B.	વાહકના આડછેદના ક્ષેત્રફળના વ્યસ્ત પ્રમાણમાં હોય છે
	C.	વાહકના આડછેદના ક્ષેત્રફળના સમ પ્રમાણમાં હોય છે	D.	ઉપરના બધામાંથી કોઈ નહિ
16.	જ્યારે વાહકનો વ્યાસ બમણો અને લંબાઈ ચાર ગણી વધારવામાં આવે તો તેનો અવરોધ			
	A.	બદલાશે નહિ	B.	ચાર ગણો વધી જશે
	C.	અડધો થઈ જશે	D.	બમણો થઈ જશે
17.	કાર્ય કરવાનો દર _____ છે			
	A.	જુલ	B.	પોટેન્શીયલ
	C.	શક્તિ	D.	પાવર
18.	ત્રણ અવરોધ 20 Ω , 30 Ω અને 50 Ω સમાંતરમાં જોડેલા છે. સમતુલ્ય અવરોધ _____ થશે			
	A.	12	B.	18.75
	C.	9.67	D.	0.103
19.	નીચેનામાંથી એક્ટિવ એલિમેંટ શોધો.			
	A.	કેપેસિટર	B.	ઇન્ડક્ટર
	C.	અવરોધ	D.	કરંટ સોર્સ
20.	નીચેનામાંથી પેસિવ એલિમેંટ શોધો.			
	A.	વોલ્ટેજ સોર્સ	B.	બેટરી
	C.	અવરોધ	D.	કરંટ સોર્સ
21.	નીચેના પૈકી કયું વિધાન નેટવર્ક વિષે સાચું નથી?			

	A.	દરેક મેશ એ લૂપ છે	B.	દરેક લૂપ એ મેશ નથી
	C.	બે નોડ વચ્ચેના એલિમેન્ટને બ્રાંચ કહેવાય છે	D.	નેટવર્કને બંને વોલ્ટેજ સોર્સ તેમજ કરંટ સોર્સ ના હોઈ શકે
22.	જ્યારે બે સરખી કિંમતના અવરોધોને સમાંતરમાં જોડવામાં આવે છે, ત્યારે સમતુલ્ય અવરોધ			
	A.	દરેક અવરોધની કિંમત કરતા વધુ થશે	B.	દરેક અવરોધની કિંમત જેટલો થશે
	C.	દરેક અવરોધની કિંમત કરતા ઓછો થશે	D.	ઉપરના બધામાંથી કોઈ નહિ
23.	સોર્સથી લોડ તરફ મહત્તમ પાવર ટ્રાંસફર થવા માટેની શરત			
	A.	$R_L = \infty$	B.	$R_S > R_L$
	C.	$R_S < R_L$	D.	$R_S = R_L$
24.	ત્રણ 30Ω ના અવરોધ ડેલ્ટામાં જોડેલા છે. તો તેના સમતુલ્ય સ્ટાર જોડાણનો પ્રત્યેક પ્રતિરોધ _____ Ω થાય.			
	A.	10Ω	B.	30Ω
	C.	90Ω	D.	900Ω
25.	ત્રણ 30Ω ના અવરોધ સ્ટારમાં જોડેલા છે. તો તેના સમતુલ્ય ડેલ્ટા જોડાણનો પ્રત્યેક પ્રતિરોધ _____ Ω થાય.			
	A.	10Ω	B.	30Ω
	C.	90Ω	D.	900Ω
26.	જે નેટવર્કમાં વોલ્ટેજ વીજપ્રવાહનો સંબંધ કોઈપણ દિશામાં સરખો હોય તેને _____ કહે છે.			
	A.	યુનિલેટરલ નેટવર્ક	B.	સિમેટ્રિકલ નેટવર્ક
	C.	લિનિયર નેટવર્ક	D.	બાયલેટરલ નેટવર્ક
27.	જે નેટવર્કમાં વોલ્ટેજ વીજપ્રવાહનો સંબંધ કોઈપણ દિશામાં સરખો ના હોય તેને _____ કહે છે.			
	A.	યુનિલેટરલ નેટવર્ક	B.	સિમેટ્રિકલ નેટવર્ક
	C.	લિનિયર નેટવર્ક	D.	બાયલેટરલ નેટવર્ક
28.	જે નેટવર્કમાં ઇનપુટ તથા આઉટપુટ છેડાઓ અદલ-બદલ કરતા તેના ઇલેક્ટ્રિકલ ગુણધર્મોમાં ફેરફાર થતો નથી તેને _____ કહે છે.			
	A.	યુનિલેટરલ નેટવર્ક	B.	સિમેટ્રિકલ નેટવર્ક
	C.	લિનિયર નેટવર્ક	D.	બાયલેટરલ નેટવર્ક

29.	30 V, 5Ω વોલ્ટેજ સોર્સનો સમતુલ્ય કરંટ સોર્સ _____ છે.			
	A.	30 A, 5Ω	B.	15 A, 10 Ω
	C.	6 A, 5Ω	D.	15 A, 5Ω
30.	10 A, 2Ω કરંટ સોર્સનો સમતુલ્ય વોલ્ટેજ સોર્સ _____ છે.			
	A.	10 V, 2Ω	B.	20 V, 2Ω
	C.	5 V, 1Ω	D.	5 V, 2Ω
31.	કેપેસિટંસ _____ દ્વારા દર્શાવવામાં આવે છે.			
	A.	$C=Q \cdot V$	B.	$C=Q+V$
	C.	$C=Q/V$	D.	$C=V/Q$
32.	પરમીટીવીટી ϵ_0 ની કિંમત _____ f/m છે.			
	A.	8.854×10^{-11}	B.	8.854×10^{-12}
	C.	8.854×10^{-10}	D.	8.854×10^{-9}
33.	થેવેનીન થીયરમનો ડ્યુઅલ થીયરમ કયો છે?			
	A.	સુપરપોઝીશન થીયરમ	B.	મહત્તમ પાવર ટ્રાંસફર થીયરમ
	C.	કિર્ચોફના નિયમો	D.	નોર્ટનનો થીયરમ
34.	ઇલેક્ટ્રોસ્ટેટિક્સમાં ઇલેક્ટ્રિક ફ્લક્સ _____ થી દર્શાવવામાં આવે છે.			
	A.	P	B.	Φ
	C.	Σ	D.	Ψ
35.	કુલંબ/મી ² એ _____ નો એકમ છે.			
	A.	ઇલેક્ટ્રિક ફીલ્ડ ઇન્ટેન્સિટી	B.	ઇલેક્ટ્રિક ફ્લક્સ ઘનતા
	C.	ઇલેક્ટ્રિક ચાર્જ	D.	ઇલેક્ટ્રિક ફ્લક્સ
36.	1 pF = _____			
	A.	10^{-12} F	B.	10^{-9} F
	C.	10^{-6} F	D.	10^{-3} F
37.	કેપેસિટર દ્વારા શક્તિ સંગ્રહનું સૂત્ર _____ થી આપવામાં આવે છે.			
	A.	$\frac{1}{2} \cdot Q/C$	B.	$\frac{1}{2} \cdot Q/C^2$
	C.	$\frac{1}{2} \cdot CV$	D.	$\frac{1}{2} \cdot Q^2/C$
38.	ફેરડે = _____			
	A.	વોલ્ટ/કુલંબ ²	B.	વોલ્ટ*કુલંબ
	C.	કુલંબ/વોલ્ટ	D.	વોલ્ટ/કુલંબ
39.	R-C સમય અચળાંક _____ થી દર્શાવાય છે.			
	A.	α	B.	β
	C.	θ	D.	λ

40.	કેપેસિટરનો કેપેસિટંસ _____ થી પ્રભાવિત થતો નથી.			
	A.	પ્લેટનું ક્ષેત્રફળ	B.	પ્લેટની જાડાઈ
	C.	પ્લેટ વચ્ચેનું અંતર	D.	ડાય-ઇલેક્ટ્રિકનો પ્રકાર
41.	એક કેપેસિટર જે 0.5 કુલંબ ચાર્જનો સંગ્રહ 10 વોલ્ટ પર કરે છે તેનો કેપેસિટંસ _____ ફેરડ થશે			
	A.	0.05	B.	20
	C.	10	D.	5
42.	R-C પરિપથનો સમય અચળાંક એવી રીતે વ્યાખ્યાયિત કરવામાં આવે છે કે જે સમય દરમિયાન કેપેસિટર ચાર્જિંગ વીજપ્રવાહ _____ ટકા તેની _____ કિંમતના થાય.			
	A.	63, અંતિમ	B.	37, અંતિમ
	C.	37, શરૂઆતની	D.	63, શરૂઆતની
43.	કેપેસિટર એ બે _____ ધરાવે છે.			
	A.	ચાંદીના આવરણવાળા અવાહકો	B.	સીરામીક પ્લેટ્સ અને એક અબરખની ડીસ્ક
	C.	વાહકો જે અવાહકોથી અલગ કરેલા	D.	ડાય-ઇલેક્ટ્રિકથી અલગ કરેલા અવાહક
44.	જો 8 μF ના બે કેપેસિટરને શ્રેણીમાં જોડવામાં આવે તો કુલ કેપેસિટંસ _____ થશે.			
	A.	16 μF	B.	8 μF
	C.	4 μF	D.	2 μF
45.	ડાય-ઇલેક્ટ્રિક કોસ્ટન્ટ $K =$ _____			
	A.	$4\pi * 10^{-7}$	B.	$1/4\pi\epsilon_0\epsilon_r$
	C.	$4\pi\epsilon_0\epsilon_r$	D.	$1/4\pi\epsilon_0\epsilon_r d^2$
46.	એક ઇલેક્ટ્રોનનો ચાર્જ _____ કુલંબ છે.			
	A.	$1.602 * 10^{-18}$	B.	$1.602 * 10^{-19}$
	C.	$1.602 * 10^{-20}$	D.	$1.602 * 10^{-21}$
47.	એક ઇલેક્ટ્રોનનું દળ _____ કિગ્રા છે.			
	A.	$9.108 * 10^{-31}$	B.	$9.108 * 10^{-32}$
	C.	$9.108 * 10^{-33}$	D.	$9.108 * 10^{-34}$
48.	જ્યારે 8 μF ના બે કેપેસિટરને સમાંતરમાં જોડવામાં આવે તો કુલ કેપેસિટંસ _____ થશે.			
	A.	16 μF	B.	8 μF
	C.	4 μF	D.	2 μF
49.	જ્યારે ત્રણ કેપેસિટર 20 μF , 25 μF અને 30 μF ને શ્રેણીમાં જોડવામાં આવે તો સમતુલ્ય કેપેસિટંસ _____ થશે.			
	A.	25 μF	B.	75 μF

	C.	0.1233 μF	D.	8.11 μF
50.	50 μF ના દરેક કેપેસિટરને શ્રેણીમાં જોડી અને 200 વોલ્ટ આપવામાં આવે છે. તો દરેક કેપેસિટરમાં _____ જુલ શક્તિ સંચય થશે.			
	A.	2	B.	1
	C.	0.5	D.	0.25
51.	ચુંબકીય ફલક્ષનો એકમ _____ છે.			
	A.	ટેસ્લા	B.	એમ્પિયર-ટર્ન
	C.	વેબર	D.	કુલંબ
52.	મેગ્નેટાઇઝિંગ ફોર્સ (H) અને ચુંબકીય ફલક્ષ ઘનતા (B) _____ સંબંધથી અપાય છે.			
	A.	$B = H/\mu_0 \mu_r$	B.	$B = \mu H$
	C.	$B = \mu_0 H/\mu_r$	D.	$B = \mu_r H/\mu_0$
53.	ડાયનેમિકલી ઇન્ડ્યુસ્ડ ઇએમએફ _____ દ્વારા આપવામાં આવે છે.			
	A.	$BL\sin\theta$	B.	$BLV\cos\theta$
	C.	$BLV\sin\theta$	D.	NdI/dt
54.	નીચેનામાંથી સાચું સૂત્ર કયું છે?			
	A.	$\mu = \mu_0 \mu_r$	B.	$\mu = \mu_0 \mu_r/2$
	C.	$\mu = \sqrt{\mu_0 \mu_r}$	D.	$\mu = (\mu_0 + \mu_r)/2$
55.	ડાયનેમિકલી ઇન્ડ્યુસ્ડ ઇએમએફની દિશા _____ દ્વારા શોધવામાં આવે છે.			
	A.	કોર્ક સ્ક્રુ નિયમ	B.	ફ્લેમિંગના જમણા હાથનો નિયમ
	C.	ફ્લેમિંગના ડાબા હાથનો નિયમ	D.	જમણા હાથનો નિયમ
56.	સ્વ પ્રેરિત ઇએમએફની કિંમત			
	A.	ધૂંચળાના આંટાની સંખ્યાના વર્ગના સમપ્રમાણમાં	B.	ધૂંચળાના આંટાની સંખ્યાના સમપ્રમાણમાં
	C.	ધૂંચળાના આંટાની સંખ્યાના વર્ગના વ્યસ્ત પ્રમાણમાં	D.	ધૂંચળાના આંટાની સંખ્યાના વ્યસ્ત પ્રમાણમાં
57.	હિસ્ટેરેસિસ લુપનું ક્ષેત્રફળ			
	A.	માત્ર એડી કરંટ લોસ દર્શાવે છે	B.	જેમ ઓછું તેમ હિસ્ટેરેસિસ લોસ વધારે
	C.	માત્ર હિસ્ટેરેસિસ લોસ દર્શાવે છે	D.	બંને હિસ્ટેરેસિસ લોસ તથા એડી કરંટ લોસ દર્શાવે છે
58.	ફેરેડેના ઇલેક્ટ્રોમેગ્નેટિક ઇન્ડક્શનના નિયમ મુજબ, વાહકમાં ઇએમએફ ત્યારે પ્રેરિત થાય છે જ્યારે તે			
	A.	ચુંબકીય ક્ષેત્રમાં રહે છે	B.	ચુંબકીય ક્ષેત્રની દિશાને સમાંતર ગતિ કરે છે
	C.	ચુંબકીય ફલક્ષ કાપે છે	D.	ચુંબકીય ફલક્ષના લંબ રહે છે
59.	વાહકમાં પ્રેરિત થતા ઇએમએફની કિંમત _____ પર આધાર રાખે છે			
	A.	ફલક્ષ લીકેજની કિંમત	B.	કપાતી ફલક્ષની કિંમત

	C.	ચુંબકીય ક્ષેત્રની ફલક્ષ ઘનતા	D.	ફલક્ષ લીકેજના ફેરફારના દર
60.	કોએફિસીએન્ટ ઓફ કપલીંગ _____ દ્વારા અપાય છે			
	A.	$k=M/\sqrt{L_1+L_2}$	B.	$k=M/\sqrt{L_1-L_2}$
	C.	$k=M/\sqrt{L_1L_2}$	D.	$k=\sqrt{L_1L_2}/M$
61.	જેમ ધૂંચળાનું સેલ્ફ ઇન્ડક્ટન્સ વધારે તેમ			
	A.	તેના દ્વારા ઉત્પન્ન થતી ફલક્ષ વધારે	B.	તેના વેબર-આંટા ઓછા
	C.	તેમાં પ્રેરિત થતું ઈએમએફ ઓછું	D.	તેમાં સ્થિર વીજ પ્રવાહ પ્રસ્થાપિત કરવા માટેનો વિલંબ વધુ
62.	ચુંબકીય રીતે જોડાયેલી બે કોઇલનો મ્યુચ્યુઅલ ઇન્ડક્ટન્સ _____ પર આધાર રાખે છે			
	A.	તેઓના આંટાની સંખ્યા	B.	તેઓના સહિયારા કોરના આડછેદના ક્ષેત્રફળ
	C.	કોરની પરમીયાબિલીટી	D.	ઉપરના બધા જ
63.	કાયમી ચુંબક સામાન્ય રીતે _____ થી બનેલા હોય છે			
	A.	કાસ્ટ આયર્ન	B.	એલ્નિકો એલ્લોય
	C.	રોટ આયર્ન	D.	એલ્યુમિનિયમ
64.	જે ચુંબકીય મટીરીયલ્સ આર્મેચર તથા પરિવર્તકની કોર બનાવવા માટે સૌથી અનુકૂળ હોય છે તેઓના પરમીયાબિલીટી _____ અને હિસ્ટેરીસીસ લોસ _____ હોય છે.			
	A.	વધુ, ઓછા	B.	વધુ, વધુ
	C.	ઓછા, વધુ	D.	ઓછા, ઓછા
65.	ચુંબકીય મટીરીયલમાં પ્રાથમિક રીતે હિસ્ટેરીસીસ લોસ _____ ને લીધે થતો હોય છે			
	A.	તેની ઉચ્ચ રીટેટીવીટી	B.	આણ્વિક ઘર્ષણ
	C.	તેના મેગ્નેટાઇઝેશનનું ઝડપી ઉલટફેર	D.	ફલક્ષ ઘનતા મેગ્નેટાઇઝિંગ ફોર્સની પાછળ હોય છે
66.	ચુંબકીય ક્ષેત્રમાં સંચિત થયેલી શક્તિ _____ થી દર્શાવાય છે.			
	A.	$\frac{1}{2} * LI$	B.	$\frac{1}{2} * L^2 I$
	C.	$\frac{1}{2} * LI^2$	D.	$\frac{1}{2} * L^2 I^2$
67.	ધૂંચળાના સ્વ પ્રેરણ માટે નીચેનામાંથી કયું સૂત્ર વપરાય છે?			
	A.	$N\phi^2/I$	B.	$N^2\phi/I$
	C.	NI^2/ϕ	D.	$N\phi/I$
68.	ચુંબકની ઊંચકવાની શક્તિ _____ પર આધાર રાખે છે.			
	A.	ચુંબકીય ફલક્ષ ઘનતા	B.	તેના પોલનું ક્ષેત્રફળ
	C.	(A) તથા (B) બંને	D.	તેનો આકાર
69.	જે ધૂંચળાને 100 આંટા છે તેનો ઇન્ડક્ટન્સ 500 mH છે. 2 mWb ફલક્ષ ઉત્પન્ન કરવા માટે _____ A વીજપ્રવાહ પસાર કરવો પડે.			
	A.	40	B.	4

	C.	0.4	D.	0.04
70.	શ્રેણીમાં ઇંડક્ટેસ નીચેના કયા સૂત્રથી આપવામાં આવે છે?			
	A.	$L = L_1 - L_2 - M$	B.	$L = L_2 - L_1 - M$
	C.	$L = L_1 + L_2 \pm 2M$	D.	ઉપરના બધા જ
