

GUJARAT TECHNOLOGICAL UNIVERSITY**Diploma Semester -III Remedial Examination April - 2010****Subject code:330903****Subject Name: ELECTRICAL MACHINE-I****Date: 23 /04 /2010****Time: 03.00 pm – 05.30 pm****Instructions:****Total Marks :70**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version Authentic

- | | | |
|-------------|---|-----------|
| Q.1 | (a) Explain construction of D.C.machine with neat sketch and explain function of each part. | 07 |
| | (b) Derive EMF equation of transformer and give specifications of transformer. | 07 |
| Q.2 | (a) Explain cooling methods for three phase transformer. | 07 |
| | (b) State necessity of starter.Explain 3- point starter for D.C.shunt motor with sketch. | 07 |
| OR | | |
| Q.3 | (b) Explain methods of electromechanical energy conversion | 07 |
| | (a) State speed control methods for D.C. shunt motor and explain field control method. | 05 |
| | (b) A 250V, 10kw D.C. shunt generator runs at 50% load.The shunt field resi. is 250 Ω and armature resistance is 0.5 Ω . Calculate armature current and induced emf. | 05 |
| | (c) Explain magnetization characteristic of D.C. machine. | 04 |
| OR | | |
| Q.3 | (a) Derive EMF equation of D.C. generator. | 05 |
| | (b) Explain various losses in D.C. machine. | 05 |
| | (c) Write short note on brake test. | 04 |
| Q.4 | (a) Draw ON LOAD vector diagram of 1-phase transformer for lagging power factor | 05 |
| | (b) Explain O.C. and S.C. test of 1-phase transformer. | 05 |
| | (c) Write short note on auto transformer. | 04 |
| OR | | |
| Q. 4 | (a) List various accessories of 3-phase power transformer and explain function of breather. | 05 |
| | (b) A 440/220V , 2 KVA , 50 Hz 1-phase transformer has maximum flux of 5 mwb. Calculate (1) Full load primary current (2) Full load secondary current. (3) No.of primary turns (4) No. of secondary turns (5) Volt/ turn ratio. | 05 |
| | (c) State condition for parallel operation of 1-phase transformer. | 04 |
| Q.5 | (a) Explain commutation process in D.C.generator. | 05 |
| | (b) Draw and explain internal and external characteristics of D.C.shunt generator. | 05 |
| | (c) Draw different cross sectional view of transformer core. | 04 |
| OR | | |
| Q.5 | (a) Draw and explain T-Ia, T-N , and N-Ia characteristic of D.C. series motor. | 05 |
| | (b) Write short note on all day efficiency of transformer. | 05 |
| | (c) Compare core type and shell type 1-phase transformer | 04 |

પ્રશ્ન-૧	અ	સ્વચ્છ આકૃતિ દોરી ડી.સી. મશીનની રચના સમજાવો અને દરેક ભાગનું કાર્ય સમજાવો.	07
	બ	ટ્રાન્સફોર્મરના ઇ. એમ.એફ. નું સમીકરણ સાબિત કરો અને ટ્રાન્સફોર્મરના સ્પેસિફિકેશન લખો.	07
પ્રશ્ન-૨	અ	થ્રી ફેઝ ટ્રાન્સફોર્મરની ફૂલીંગ પદ્ધતિઓ સમજાવો.	07
	બ	સ્ટાર્ટરની જરૂરિયાત જણાવો. ડી.સી.શન્ટ મોટર માટે ૩-પોઇન્ટ સ્ટાર્ટર આકૃતિની મદદથી સમજાવો.	07
		અથવા	
	બ	ઇલેક્ટ્રોમેકેનિકલ એનર્જી કન્વર્ઝનની પદ્ધતિઓ સમજાવો.	07
પ્રશ્ન-૩	અ	ડી.સી. શન્ટ મોટર માટે સ્પીડ કંટ્રોલની પદ્ધતિઓ જણાવો અને ફિલ્ડ કન્ટ્રોલ પદ્ધતિ સમજાવો	05
	બ	એક 250V , 10 kw ડી.સી. શન્ટ જનરેટર 50 % લોડ ઉપર કાર્ય કરે છે.શન્ટ ફિલ્ડ રેસીસ્ટન્સ 250 Ω અને આર્મેચર રેસીસ્ટન્સ 0.5 Ω છે.તો આર્મેચર કરન્ટ અને ઇન્ડ્યુસ્ડ ઇ.એમ.એફ. ની કિંમત ગણો.	05
	ક	ડી.સી.મશીનની મેગ્નેટાઇઝેશન કેરેક્ટરીસ્ટીક સમજાવો.	04
		અથવા	
પ્રશ્ન-૩	અ	ડી.સી. જનરેટરનું ઇ.એમ.એફ.નું સમીકરણ તારવો.	05
	બ	ડી.સી.મશીનના જુદા જુદા પ્રકારના લોસીસ સમજાવો.	05
	ક	બ્રેક ટેસ્ટ ઉપર ટૂંક નોંધ લખો.	04
પ્રશ્ન-૪	અ	સીંગલ ફેઝ ટ્રાન્સફોર્મરનો લેગીંગ પાવર ફેક્ટર માટે ઓન લોડ માટે વેક્ટર ડાયાગ્રામ દોરો.	05
	બ	સીંગલ ફેઝ ટ્રાન્સફોર્મરની ઓપન સર્કીટ અને શોર્ટ સર્કીટ ટેસ્ટ સમજાવો.	05
	ક	ઓટો ટ્રાન્સફોર્મર ઉપર ટૂંક નોંધ લખો.	04
		અથવા	
પ્રશ્ન-૪	અ	થ્રી ફેઝ ટ્રાન્સફોર્મરની સહાયક સામગ્રીની યાદી બનાવો અને બ્રીધરનું કાર્ય સમજાવો	05
	બ	એક 440/220 V, 2 KVA, 50 Hz સીંગલ ફેઝ ટ્રાન્સફોર્મરનું મહત્તમ ફલક્ષ 5 mw છે. તો ગણો.(૧) કુલ લોડ પ્રાથમરી કરન્ટ (૨) કુલ લોડ સેકન્ડરી કરન્ટ (૩) પ્રાથમરી ટર્નસની સંખ્યા(૪) સેકન્ડરી ટર્નસની સંખ્યા (૫) વોલ્ટ/ટર્ન રેશીયો.	05
	ક	સીંગલ ફેઝ ટ્રાન્સફોર્મરના પેરેલલ ઓપરેશનની શરતો જણાવો.	04
પ્રશ્ન-૫	અ	ડી.સી. જનરેટરમા કોમ્યુટેશન પ્રક્રિયા સમજાવો.	05
	બ	ડી.સી. શન્ટ જનરેટરની એક્ષર્નલ અને ઇન્ટર્નલ કેરેક્ટરીસ્ટીક દોરો અને સમજાવો.	05
	ક	ટ્રાન્સફોર્મરના કોરના જુદા જુદા કોસ સેક્શનલ વ્યૂ (દેખાવ) દોરો.	04
		અથવા	
પ્રશ્ન-૫	અ	ડી.સી. સીરીઝ મોટર માટે T-Ia , T-N, અને N-Ia કેરેક્ટરીસ્ટીક દોરો અને સમજાવો.	05
	બ	ટ્રાન્સફોર્મરની ઓલ ડે એફિસીયન્સી ઉપર ટૂંક નોંધ લખો.	05
	ક	સીંગલ ફેઝ ટ્રાન્સફોર્મર માટે કોર ટાઇપ અને શેલ ટાઇપ ની સરખામણી કરો.	04
