

GUJARAT TECHNOLOGICAL UNIVERSITY**Diploma Engineering - SEMESTER-III • EXAMINATION – SUMMER • 2014****Subject Code: 3331601****Date: 11-06-2014****Subject Name: Digital Memory System****Time: 10:30 am - 01:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is considered to be Authentic.

- Q.1** (a) Explain basic gates with symbol, operation and truth table. **07**
(b) What is Universal Gate? Explain in detail. **07**
- Q.2** (a) What is sequential circuit? Explain D and T Flip-Flop. **07**
(b) Explain S-R Flip-Flop in detail. **07**
- OR
- (b) Explain J-K Flip-Flop in detail. **07**
- Q.3** (a) Explain D-type Edge triggered Flip-Flop. **07**
(b) Differentiate combinational and sequential circuit. **07**
- OR
- Q.3** (a) Explain Master Slave J-K Flip-Flop. **07**
(b) Explain asynchronous sequential circuit with example. **07**
- Q.4** (a) Explain 4-bit binary up-down counter with necessary diagram. **07**
(b) Explain ROM. **07**
- OR
- Q.4** (a) Explain 4-bit BCD Ripple counter with necessary diagram. **07**
(b) What is RAM? Explain different types of RAM. **07**
- Q.5** (a) Explain 8086 processor architecture. **07**
(b) Develop the excitation table of J-K Flip-Flop. **07**
- OR
- Q.5** (a) Explain Flynn's classification. **07**
(b) Develop the excitation table of R-S Flip-Flop. **07**

ગુજરાતી

- પ્રશ્ન. ૧ અ મૂળભૂત ગેટ પ્રતીક, પ્રક્રિયા અને truth table સાથે સમજાવો. ૦૭
બ Universal ગેટ એટલે શું? વિગતવાર સમજાવો. ૦૭
- પ્રશ્ન. ૨ અ Sequential circuit એટલે શું? D અને T Flip-Flop સમજાવો. ૦૭
બ S-R Flip-Flop વિગતવાર સમજાવો. ૦૭
- અથવા
- બ J-K Flip-Flop વિગતવાર સમજાવો. ૦૭
- પ્રશ્ન. ૩ અ D-પ્રકારનો Edge triggered Flip-Flop સમજાવો. ૦૭
બ Combinational અને Sequential circuit વચ્ચેનો તફાવત સમજાવો. ૦૭
- અથવા
- પ્રશ્ન. ૩ અ Master Slave J-K Flip-Flop સમજાવો. ૦૭
બ Asynchronous sequential circuit ઉદાહરણ સાથે સમજાવો. ૦૭
- પ્રશ્ન. ૪ અ 4-bit binary up-down counter જરૂરી આકૃતિ સાથે સમજાવો. ૦૭
બ ROM સમજાવો. ૦૭
- અથવા
- પ્રશ્ન. ૪ અ 4-bit BCD Ripple counter જરૂરી આકૃતિ સાથે સમજાવો. ૦૭
બ RAM એટલે શું? વિવિધ પ્રકારની RAM વિશે સમજાવો. ૦૭
- પ્રશ્ન. ૫ અ 8086 processor architecture સમજાવો. ૦૭
બ J-K Flip-Flop નું excitation table વિકસાવો. ૦૭
- અથવા
- પ્રશ્ન. ૫ અ Flynn's નું વર્ગીકરણ સમજાવો. ૦૭
બ R-S Flip-Flop નું excitation table વિકસાવો. ૦૭
