

GUJARAT TECHNOLOGICAL UNIVERSITY**Diploma Engineering - SEMESTER-III • EXAMINATION – SUMMER • 2014****Subject Code: 3332002****Date: 19-06-2014****Subject Name: Digital Circuits****Time: 10:30 am - 01:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Each question carry equal marks (14 marks)

- Q.1** (a) (i) Convert Hexa-decimal no $(7A6)_{16}$ in to Binary and Octal **07**
(ii) Convert $(101010)_2 = (\dots\dots\dots)_{10} = (\dots\dots\dots)_{16}$
(iii) Obtain Gray code of $(1110010)_2$
- (b) State and Prove De Morgan's Theorem. **07**
- Q.2** (a) Why NOR gate is called Universal gate? Build AND, OR, NOT AND EX-NOR gate using NOR gate. **07**
- (b) Explain Positive logic and Negative logic system **07**
- OR
- (b) Why NAND gate is called Universal gate? Build AND, OR, NOT AND EX-NOR gate using NOR gate. **07**
- Q.3** (a) Write a short note on J-K flip flop. **07**
- (b) Write a short note on decoder. **07**
- OR
- Q.3** (a) Draw Karnaugh-Map for following **07**
(i) $F(A,B,C) = \sum_m (0, 1, 2, 4, 5, 6, 7)$
(ii) $F(A,B,C) = \sum_m (0, 1, 2, 5, 6)$
- (b) Simplify following logic equation using Boolean –Algebra. **07**
(i) $F = A'BC + AB'C + ABC' + ABC$
(ii) $F = A'BC + ABC + BC'$
- Q.4** (a) Write a short note on 2 - bit magnitude comparator. **07**
- (b) Write a short note on R-S flip-flop. **07**
- OR
- Q.4** (a) (i) Perform binary addition $(11011)_2 + (01011)_2$ **07**
(ii) Perform binary division : $10110 \div 10$
- (b) Write a short note on shift register. **07**
- Q.5** (a) Compare Combinational logic circuit and Sequential logic circuit. **07**
- (b) Write a short note on D flip –flop **07**
- OR
- Q.5** (a) Draw and Explain Binary UP/DOWN counter with necessary diagram. **07**
- (b) Write a short note on 4-bit binary counter. **07**

ગુજરાતી

- પ્રશ્ન. ૧ અ (i) હેક્સડેસીમલ $(7A6)_{16}$ ને બાયનરી તથા ઓક્ટલ માં ફેરવો. ૦૭
- (ii) $(101010)_2 = (\dots\dots\dots)_{10} = (\dots\dots\dots)_{16}$ રૂપાંતર કરો.
- (iii) $(1110010)_2$ બાયનરી નું ગ્રે કોડ માં રૂપાંતર કરો.
- બ દ-મોર્ગન નાં પ્રમેય લખો અને સાબિત કરો. ૦૭

- પ્રશ્ન. ૨ અ નોર ગેટ ને શા માટે યુનીવર્સલ ગેટ કહેવામાં આવે છે? નોર ગેટ માં થી એન્ડ, ૦૭
- ઓર, નોટ અને એક્સ-નોર ગેટ બનાવો.
- બ પોજેટીવ અને નેગેટીવ લોજિક સમજાવો. ૦૭

અથવા

- બ નેન્ડ ગેટ ને શા માટે યુનીવર્સલ ગેટ કહેવામાં આવે છે? નેન્ડ ગેટ માં થી એન્ડ, ૦૭
- ઓર, નોટ અને એક્સ-નોર ગેટ બનાવો.

- પ્રશ્ન. ૩ અ J-K ફ્લીપ ફ્લોપ ઉપર ટ્રેક્નોંધ લખો. ૦૭
- બ ડિકોડર ઉપર ટ્રેક્નોંધ લખો. ૦૭

અથવા

- પ્રશ્ન. ૩ અ નીચેના માટે કારનોટ મેપ દોરો. ૦૭
- (i) $F(A,B,C) = \sum_m (0, 1, 2, 4,5, 6,7)$
- (ii) $F(A,B,C) = \sum_m (0,1,2,5,6)$
- બ બુલીયન એલજીબ્રા ની મદદ થી નીચેના સમીકરણો નું સાદુરૂપ આપો. ૦૭
- (i) $F = A'BC + AB'C + ABC' + ABC$
- (ii) $F = A'BC + ABC + BC'$

- પ્રશ્ન. ૪ અ 2 – મેગનિટ્યુડ કમ્પેરેટર ઉપર ટ્રેક્નોંધ લખો. ૦૭
- બ R-S ફ્લીપ ફ્લોપ ઉપર ટ્રેક્નોંધ લખો. ૦૭

અથવા

- પ્રશ્ન. ૪ અ (i) બાયનરી સરવાળો કરો. $(11011)_2 + (01011)_2$ ૦૭
- (ii) બાયનરી ભાગાકાર કરો : $10110 \div 10$
- બ શીફ્ટ રજીસ્ટર ઉપર ટ્રેક્નોંધ લખો. ૦૭

- પ્રશ્ન. ૫ અ કોમ્પીનેશનલ લોજીક અને સીક્વન્સીયલ લોજીક સરકીટ ની સરખામણી કરો ૦૭
- 4- બીટ બાયનરી કાઉન્ટર લખી સમજાવો.
- બ D ફ્લીપ ફ્લોપ ઉપર ટ્રેક્નોંધ લખો. ૦૭

અથવા

- પ્રશ્ન. ૫ અ બાયનરી અપ ડાઉન કાઉન્ટર લખી ડાયાગ્રામ સાથે સમજાવો. ૦૭
- બ 4- બીટ બાયનરી કાઉન્ટર લખી સમજાવો. ૦૭
