

GUJARAT TECHNOLOGICAL UNIVERSITY
DIPLOMA ENGINEERING - SEMESTER- III • EXAMINATION – SUMMER • 2014

Subject Code: 3332404**Date: 21-06-2014****Subject Name: Element of Power Electronics****Time: 10:30 am - 01:00 pm****Total Marks: 70****Instructions:**

1. Attempt any five questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Each question carry equal marks (14 marks)

- Q.1** (a) What are the main differences between signal diode and power diode? Draw and explain I-V characteristics of power diode **07**
(b) Discuss advantages and disadvantages of power electronics converter. **07**
- Q.2** (a) Only Draw circuit symbol, static I-V characteristics and construction details of SCR. **07**
(b) List various power transistor used in power electronics converter. Draw and discuss in brief N-channel enhancement power MOSFET. **07**
OR
(b) Draw and explain in brief basic structure insulated gate bipolar transistor(IGBT) **07**
- Q.3** (a) List various turn-on methods of thyristor. Explain light triggering method in brief. **07**
(b) Explain design of simple snubber circuit across SCR. **07**
OR
(a) Explain gate triggering method for turn on thyristor. **07**
(b) What do you mean by commutation? Explain natural commutation in detail. **07**
- Q.4** (a) Draw and discuss in brief basic construction of gate turn of thyristor (GTO) **07**
(b) Draw and explain Triac firing circuit using diac. **07**
OR
(a) Draw and explain Resistance firing circuit for thyristors. **07**
(b) Draw and explain basic structure and its equivalent circuit of Unijunction transistor(UJT) **07**
- Q.5** (a) Classify power electronics converter in brief. **07**
(b) Explain single phase half wave phase controlled rectifier circuit with R load. **07**
OR
(a) Explain principle of chopper circuit with voltage and current waveform. **07**
(b) Explain single phase half wave AC voltage controller with R load. **07**

ગુજરાતી

- પ્રશ્ન. ૧ અ સિઝનલ ડાયોડ અને પાવર ડાયોડ વચે મુખ્ય તફાવત શું છે? પાવર ડાયોડ ની ૦૭
I-V લાક્ષણિકતા દોરી સમજાવો.
બ પાવર ઇલેક્ટ્રોનિક્સ ના ફાયદા અને ગેર ફાયદા વિષે ચર્ચા કરો. ૦૭
- પ્રશ્ન. ૨ અ SCR માટે નું પ્રતીક, સ્થિર I-V લાક્ષણિકતા, અને બંધારણ માહિતી ફક્ત દોરો. ૦૭
બ વિવિધ પાવર ટ્રાન્ઝિસ્ટર ની યાદી બનાવો. N-ચેનલ પાવર MOSFET દોરી અને ૦૭
તેના વિષે ચર્ચા કરો.

અથવા

- બ IGBT નું મૂળભૂત બંધારણ દોરો અને સમજાવો. ૦૭
- પ્રશ્ન. ૩ અ થાયરીસ્ટર ને ચાલુ કરવા માટે ની પદ્ધતિ ની યાદી બનાવો. લાઈટ ટ્રીગર ૦૭
પદ્ધતિ ને ટૂંક માં સમજાવો.
બ SCR માટે સાદી સ્નબર સર્કિટ ની રચના સમજાવો. ૦૭

અથવા

- પ્રશ્ન. ૩ અ થાયરીસ્ટર ને ચાલુ કરવા માટે ની ગેટ ટ્રીગર પદ્ધતિ સમજાવો. ૦૭
બ કોમ્યુટેસન એટલે શું? નેચરલ કોમ્યુટેસન સમજાવો. ૦૭
- પ્રશ્ન. ૪ અ GTO માટે નું મૂળભૂત બંધારણ દોરી ટૂંક માં સમજાવો. ૦૭
બ ડાયક ને ઉપયોગ માં લઈને બનાવેલી ટ્રાયક ફાયરિંગ સર્કિટ દોરી સમજાવો. ૦૭

અથવા

- પ્રશ્ન. ૪ અ થાયરીસ્ટર માટે રસિસ્ટન્સ ફાયરિંગ સર્કિટ દોરી સમજાવો. ૦૭
બ UJT માટે નું મૂળભૂત બંધારણ અને તેની સમકક્ષ સર્કિટ દોરી સમજાવો. ૦૭
- પ્રશ્ન. ૫ અ પાવર ઇલેક્ટ્રોનિક્સ કન્વર્ટર ને ટૂંક માં વર્ગીકૃત કરો. ૦૭
બ R લોડ સાથે ની સિંગલ ફેઝ હાફ વેવ ફેઝ કંટ્રોલ રેક્ટીફાયર સર્કિટ સમજાવો. ૦૭

અથવા

- પ્રશ્ન. ૫ અ ચોપર સર્કિટ નો મૂળભૂત સિદ્ધાંત વોલ્ટેજ અને કરંટ વેવ ફોર્મ સાથે સમજાવો. ૦૭
બ સિંગલ ફેઝ હાફ વેવ AC વોલ્ટેજ કંટ્રોલર R લોડ સાથે સમજાવો. ૦૭
