

**GUJARAT TECHNOLOGICAL UNIVERSITY**  
**DIPLOMA ENGINEERING – SEMESTER – III • EXAMINATION – SUMMER 2014**

**Subject Code: 3332405****Date: 24/06/2014****Subject Name: Linear Electronic Circuits****Time: 10:30 am – 1:00 pm****Total Marks: 70****Instructions:**

1. Attempt any five questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Each question carry equal marks (14 marks)

- Q.1** (a) Give classification of ICs according to package and temperature range. **07**  
(b) Describe the block diagram of Op-amplifier. **07**
- Q.2** (a) Define: 1. input offset voltage 2. input offset current. **07**  
(b) List any four characteristics of ideal op-amp. **07**
- OR
- (b) Define: 1. common mode rejection ratio 2. Supply voltage rejection ratio. **07**
- Q.3** (a) Derive equation for the closed loop voltage gain of negative voltage series feedback amplifier. **07**  
(b) Draw circuit diagram of Differential amplifier with one op-amp and derive the equation for the output. **07**
- OR
- Q.3** (a) Derive equation for the closed loop voltage gain of voltage shunt feedback amplifier. **07**  
(b) Draw circuit diagram of Differential amplifier with two op-amp and derive the equation for the output. **07**
- Q.4** (a) Draw and derive the equation of averaging amplifier. **07**  
(b) Prove that inverting terminal of voltage shunt feedback is at virtual ground with equation. **07**
- OR
- Q. 4** (a) Draw and derive the equation of summing amplifier. **07**  
(b) Differentiate between AC and DC amplifier. **07**
- Q.5** (a) Draw and derive the equation of integrator. **07**  
(b) Draw and explain Schmitt trigger with necessary sketches. **07**
- OR
- Q.5** (a) Describe the working of successive approximation type Analog to digital converter. **07**  
(b) Draw and derive the equation of differentiator. **07**

\*\*\*\*\*

## ગુજરાતી

- પ્રશ્ન. 1 અ ICs નુ વર્ગીકરણ તેના પેકેજ અને તાપમાન રેંજ ના આધારે કરો. 09  
બ ઓપરેશનલ એમ્પ્લીફાયર નો બ્લોક ડાયાગ્રામ સમજાવો. 09

- પ્રશ્ન. 2 અ વ્યાખ્યા આપો. ૧. ઇનપુટ ઓફસેટ વોલ્ટેજ ૨. ઇનપુટ ઓફસેટ કરંટ 09  
બ આદર્શ ઓપ-એમ્પ ની ગમે તે ચાર લાક્ષણીકતા આપો. 09

### અથવા

- બ વ્યાખ્યા આપો. ૧. કોમન મોડ રિજેક્શન રેશીયો ૨. સપ્લાય વોલ્ટેજ રિજેક્શન રેશીયો 09  
પ્રશ્ન. 3 અ નેગેટીવ વોલ્ટેજ સિરિઝ ફિડબેક એમ્પ્લીફાયર નો ક્લોસ્ડ લુપ વોલ્ટેજ ગેઇન નુ સુત્ર મેળવો. 09  
બ એક ઓપ-એમ્પ સાથે ના ડિફ્રેન્શિયલ એમ્પ્લીફાયર ની સર્કીટ દોરો. અને આઉટપુટ નુ સુત્ર મેળવો. 09

### અથવા

- પ્રશ્ન. 3 અ વોલ્ટેજ શંટ ફિડબેક એમ્પ્લીફાયર નો ક્લોસ્ડ લુપ વોલ્ટેજ ગેઇન નુ સુત્ર મેળવો. 09  
બ બે ઓપ-એમ્પ સાથે ના ડિફ્રેન્શિયલ એમ્પ્લીફાયર ની સર્કીટ દોરો. અને આઉટપુટ નુ સુત્ર મેળવો. 09  
પ્રશ્ન. 4 અ એવરેજ એમ્પ્લીફાયર દોરી તેનું સુત્ર મેળવો. 09  
બ વોલ્ટેજ શંટ ફિડબેક એમ્પ્લીફાયર નો ઇંવર્ટીંગ ટર્મીનલ વર્ચ્યુઅલ ગ્રાઉન્ડ હોય છે તે સુત્ર સાથે સાબિત કરો. 09

### અથવા

- પ્રશ્ન. 4 અ સમિંગ એમ્પ્લીફાયર દોરી તેનું સુત્ર મેળવો. 09  
બ AC અને DC એમ્પ્લીફાયર નો તફાવત આપો. 09  
પ્રશ્ન. 5 અ ઇન્ટીગ્રેટર દોરી તેનું સુત્ર મેળવો. 09  
બ સ્મિથ ટ્રીગર જરૂરી આકૃતિ સાથે દોરી સમજાવો. 09

### અથવા

- પ્રશ્ન. 5 અ સ્ક્રસેસીવ એપ્રોક્સીમેશન ટાઇપ એનાલોગ ટુ ડિજિટલ કંવર્ટર નુ કાર્ય સમજાવો. 09  
બ ડિફ્રેન્શિયલ દોરી તેનું સુત્ર મેળવો. 09

\*\*\*\*\*