

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY

M. E. Sem. – IInd - Examination – June/July- 2011

Subject code: 1722902

Subject Name: Modern Electric Drives

Date: 24/06/2011

Time: 10:30 am – 01:00 pm

Total Marks: 70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Notations used have usual meaning.

- Q.1** (a) Explain reference frame theory in brief. **07**
- (b) Explain various operating duty cycles for motor and discuss how rating of motor can be obtained. **07**

- Q.2** (a) Explain following terms with respect to the controlled converter. **07**
- (i) Harmonic Factor.
 - (ii) Displacement Factor.
 - (iii) Input Supply Power Factor.
- (b) The speed of a 10 kW, 230 V, 1200 rpm separately excited dc motor is controlled by a single phase full wave converter. If the armature resistance of the motor is 0.5 ohm, as supply voltage is 260 V, motor voltage constant $K\Phi$ is 0.182 V/rpm. Find **07**
- (i) The motor torque.
 - (ii) The speed of the motor.
 - (iii) The supply power factor.
- For firing angle $\alpha=30^\circ$

OR

- (b) The speed of a separately excited dc motor is controlled by a thyristorised buck chopper. The dc supply voltage being 120 V, armature resistance $R_a=0.3$ ohm, motor constant $K\Phi=0.05$ V/rpm, find the range of speed control and the range of duty cycle, provided the motor drives a constant torque load taking 25 A from the supply. Assume continuous armature current. **07**

Q.3 (a) Explain V/F control of induction motor with neat diagram. Also discuss, **07**
where this method is applicable?

(b) Discuss difference between CSI and VSI based control of induction motor **07**

OR

Q.3 (a) Explain stator voltage control method for speed control of induction motor. **07**
Also discuss why it is suitable for fan type load.

(b) Explain closed loop control of DC motor operated through chopper circuit. **07**

Q.4 (a) Discuss rotor resistance control of induction motor. Also draw its speed **07**
torque characteristics.

(b) In Time Ratio Control of buck chopper circuit supplying to the motor load, **07**
prove that the ripple in output current will be maximum for 50% duty
cycle. Assume motor draws continuous current.

OR

Q.4 (a) Discuss direct vector control method for induction motor. **07**

(b) A DC motor is operated through buck chopper circuit. Obtain an **07**
expression for maximum and minimum armature current. Assume motor
draws continuous armature current.

Q.5 (a) Explain Direct torque control method for induction motor **07**

(b) Explain Derating of induction motor due to Harmonics present in supply. **07**

OR

Q.5 (a) Explain self synchronous operation of synchronous motor drive **07**

(b) Compare speed control of DC motor based on chopper and phase control **07**
circuit.
