

GUJARAT TECHNOLOGICAL UNIVERSITY**M. E. - SEMESTER – II • EXAMINATION – SUMMER • 2013****Subject code: 1724205****Date: 05-06-2013****Subject Name: Analog and Mixed Signal VLSI Design****Time: 10.30 am – 01.00 pm****Total Marks: 70****Instructions:**


1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Draw small signal equivalent circuit of cascode amplifier and derive the formula of voltage gain, output resistance and -3dB bandwidth. **07**
- (b) Using the small signal diagram derive the voltage gain and -3dB frequency of Active pMOS load inverter **07**

- Q.2** (a) Explain MOSFET-Only Voltage Divider. **07**
- (b) Explain the significance of class AB CMOS amplifier. **07**

OR

 - (b) Assume that W/L ratios of Circuit shown in Fig. are $W_1/L_1 = 2 \mu\text{m}/1 \mu\text{m}$ and $W_2/L_2 = W_3/L_3 = W_4/L_4 = 1 \mu\text{m}/1 \mu\text{m}$. Find the dc value of V_{in} that will give a dc current in M1 of $110 \mu\text{A}$. Calculate the small signal voltage gain and output resistance. **07**



- Q.3** (a) Explain Diode Reference Self Biasing. **07**
- (b) Explain Two Stage Op-Amp and the significance of compensation in Op-Amp. **07**

OR

- Q.3** (a) Explain Analog Multiplier in detail. **07**
- (b) Explain in detail R-2R DAC Architecture. **07**

- Q.4** (a) Explain Differential amplifier with current mirror load. **07**
- (b) Explain the significance of transistor matching in case of current mirror and discuss different layout techniques. **07**

OR

- Q.4** (a) Discuss Differential Non-linearity and Integral non-linearity for DAC. **07**
- (b) Discuss Current Steering DAC. **07**

- Q.5** (a) Explain in detail Sense Amplifier. **07**
- (b) Explain the working of Pipelined ADC. **07**

OR

- Q.5** (a) Discuss Phased Frequency Detector. **07**
- (b) What is oversampling? Explain Sigma Delta ADC. **07**

Parameter Symbol	Parameter Description	Typical Parameter Value		Units
		n-Channel	p-Channel	
V_{th}	Threshold voltage ($V_{DS} = 0$)	0.7 ± 0.15	-0.7 ± 0.15	V
K'	Transconductance parameter (in saturation)	$110.0 \pm 10\%$	$50.0 \pm 10\%$	$\mu A/V^2$
γ	Bulk threshold parameter	0.4	0.57	$V^{1/2}$
λ	Channel length modulation parameter	$0.04 (L = 1 \mu m)$ $0.01 (L = 2 \mu m)$	$0.05 (L = 1 \mu m)$ $0.01 (L = 2 \mu m)$	V^{-1}
$2 \phi_F $	Surface potential at strong inversion	0.7	0.8	V