

**GUJARAT TECHNOLOGICAL UNIVERSITY**  
**M. E. - SEMESTER – II • EXAMINATION – WINTER 2012**

**Subject code: 1722901****Date: 29-12-2012****Subject Name: Advanced Power Converters and Control****Time: 10.30 am – 01.00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Notations used have usual meaning.

- Q.1** (a) Explain series loaded resonant DC-DC converter with discontinuous conduction mode. **07**  
(b) Discuss zero current switch topology for DC-DC buck converter. **07**

- Q.2** (a) Explain in brief, How switching stress can be reduced on Electronics switch using ZCS and ZVS topologies? **07**  
(b) Discuss ZVS clamped voltage topology for DC-DC converter with illustration. **07**

**OR**

- (b) Discuss current mode control of DC-DC converter. **07**

- Q.3** (a) What are the features of multi-level inverter circuits? Discuss cascaded multi-level inverter circuit. **07**  
(b) Explain diode clamped multi-level inverter with neat diagram. **07**

**OR**

- Q.3** (a) Discuss the basic concept of multi pulse converter. Explain how the number of pulses can be increased from available three phase supply. **07**  
(b) Discuss commutation and protection issues related to matrix converters. **07**

- Q.4** (a) Explain average modeling of DC-DC buck converter circuit. **07**  
(b) Explain control characteristics of converters used in HVDC transmission system. **07**

**OR**

- Q.4** (a) Discuss Bi-polar HVDC system along with its merits and demerits. **07**  
(b) What is need of small signal model? Explain small signal model of converter circuit. **07**

- Q.5** (a) Write brief note on reactive power drawn by the converters in HVDC system. **07**  
(b) Write brief note on Electronics switches used in matrix converters. **07**

**OR**

- Q.5** (a) Explain high frequency link integral half cycle converter with neat diagram. **07**  
(b) Discuss parallel resonant circuit for load resonant inverter. **07**

\*\*\*\*\*