

GUJARAT TECHNOLOGICAL UNIVERSITY
M. E. - SEMESTER – I • EXAMINATION – WINTER 2012

Subject code: 712902N**Date: 09/01/2013****Subject Name: Power Processing Circuits****Time: 02.30 pm – 05.00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Notations and symbols used have usual technical meaning.

- Q.1 (a)** Explain the “latching” phenomenon of SCR using two-transistor equivalent model. Also derive the equation for the anode current. **07**
- (b)** An SCR has V_g - I_g characteristics given as $V_g = 2 + 7I_g$. In a certain application, the gate voltage consists of rectangular pulses of 15V and of duration $60\mu s$ with 40% duty cycle. Determine the value of series resistor (R_g) in gate circuit to limit the peak power dissipation in the gate to 3.5W. Also calculate average power dissipation in the gate. **07**

- Q.2 (a)** Draw the schematic construction, circuit symbol and V-I characteristic of TRIAC. Enlist all the triggering modes of a TRIAC and explain only the most sensitive mode. **07**
- (b)** For an inverter controlled by single pulse width modulation technique; prove that selective harmonic (n) can be eliminated from the inverter output using this technique by adjusting firing angle (α) = $90^\circ/n$, using Fourier analysis. **07**

OR

- (b)** Neatly draw the output voltage (V_o) waveform from the description given below. Carry out Fourier analysis up to 17 harmonic components for the output voltage (V_o) waveform. Also calculate %THD. **07**

Positive half-cycle of output voltage (V_o) waveform:

θ (degree)	0	0	60	60	120	120	180	180
V_o (volt)	0	10	10	20	20	10	10	0

Negative half-cycle of output voltage (V_o) waveform:

θ (degree)	180	180	240	240	300	300	360	360
V_o (volt)	0	-10	-10	-20	-20	-10	-10	0

- Q.3 (a)** Explain complementary voltage commutation of SCR with necessary waveforms. **07**
- (b)** A 1-phase half-wave controlled rectifier is having a purely resistive load of 10Ω . Transformer secondary voltage is 100V (peak), 50Hz. Output voltage is controlled with firing angle (α) = 30° . Do as directed: **07**
- (i) Derive the equation of average output voltage and calculate the same.
 - (ii) Derive the equation of RMS output voltage and calculate the same.
 - (iii) Transformer utilization factor

OR

- Q.3 (a)** Explain the operation of fly-back converter with neat circuit diagram and **07**

- waveforms.
- (b) Discuss gate driver circuit for a Power MOSFET. **07**
- Q.4 (a)** Explain the operation of push-pull converter with neat circuit diagram and waveforms. **07**
- (b) Explain the operation of 3-phase bridge inverter with Y-connected resistive load in 180° conduction mode. Draw the waveforms of all the 6 gate pulses, any 1 pole voltage, common mode voltage, any 1 phase voltage and any 1 line voltage. **07**
- OR**
- Q.4 (a)** Explain bipolar switching scheme of a 1-phase sinusoidal PWM inverter with neat circuit diagram. Also draw the neat waveforms for over modulated switching mode ($A_r > A_c$). What is the relationship between carrier signal and the most significant harmonic component? **07**
- (b) What is Safe Operating Area (SOA)? Draw and explain SOA of a Power BJT. **07**
- Q.5 (a)** Explain Space Vector PWM (SVPWM) technique. **07**
- (b) Explain the operation 1-phase AC voltage controller working on the principle of ON-OFF control. Draw neat waveforms of input voltage, various gate pulses and output voltage. Also derive the expression for RMS value of output voltage in terms of duty cycle. **07**
- OR**
- Q.5 (a)** Explain dual converter with circulating current control mode. **07**
- (b) Explain center-tapped 1-phase to 1-phase cycloconverter with neat circuit diagram and waveforms for the conversion of 3 input cycles to 1 output cycle. **07**
