

GUJARAT TECHNOLOGICAL UNIVERSITY**M. E. - SEMESTER – I • EXAMINATION – WINTER 2012****Subject code: 712907N****Date: 10/01/2013****Subject Name: Power Devices & Applications****Time: 02.30 pm – 05.00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) List out & explain Various types of Power Converters. **06**
(b) Why silicon is preferred over germanium to make controlled rectifier. **03**
(c) Write a detailed note on various types of losses in practical switches. **05**

- Q.2** (a) 1. Why schotky diodes switch off much faster than p-n junction diode? **07**
2. A diode has a reverse recovery time of $2.5\mu\text{s}$. If di/dt is $17.5\text{ A}/\mu\text{s}$, find a stored charge & peak reverse current.
(b) Compare Various types of firing circuits. **07**

OR

- (b) Draw the structure, symbol & V-I characteristic of UJT. Also derive the equation for Periodic time T of UJT relaxation oscillator. **07**

- Q.3** (a) Define commutation. Explain Class B commutation with necessary diagram & design consideration. **07**
(b) What are the advantages of PUT? Design PUT-30 minute time delay circuit. **07**

OR

- Q.3** (a) What is the requirement of a snubber circuit? In an ac circuit using a thyristor having a dv/dt rating of $20\text{ V}/\mu\text{s}$, the source inductance is 0.5 mH . The rms value of supply voltage is 230V . If the damping factor is 0.75 , find out the value of R and C of the snubber circuit. **07**
(b) Compare SUS and SBS in tabular forms. **07**

- Q.4** (a) Describe different region of operation of a thyristor with the help of V-I characteristics. **07**
(b) Draw & explain types of UPS system. Also discuss applications of UPS systems. **07**

OR

- Q.4** (a) Discuss Utility of Latching & holding current. Write a detailed note on Gate characteristics of SCR. **07**
(b) Why battery charging needed? Draw & explain battery charging circuit. **07**

- Q.5** (a) Write a detailed note on Light-dimmer control. **07**
(b) What are the modes of operation of BJT? Show that the energy loss during turn on a power transistor is given by $(VI/6) T$ joules where V=off state voltage, I= on state current and T is turn on time. Assume voltage & current to be linear. **07**

OR

- Q.5** (a) Explain power circuit of ideal zero voltage switch with neat sketch. **07**
(b) What are the features of IGBT? Describe construction & working characteristics of IGBT with neat sketches. **07**
