

GUJARAT TECHNOLOGICAL UNIVERSITY**M.E-1st SEMESTER–EXAMINATION –JANUARY-2013****Subject code: 714201N****Date: 08/01/2013****Subject Name: Principles of VLSI Design****Time: 02:30 pm – 05:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.


- Q.1** (a) Explain the VLSI Design Flow. **07**
 (b) Draw and Explain the Fabrication Steps for NMOS. **07**

- Q.2** (a) Explain The Voltage Transfer Characteristic of Resistive Load NMOS Inverter. **07**
 (B) Explain The Significance of Photolithography and Multilevel Metallization in Fabrication. **07**

OR

- (B) What is Layout Design Rules? Explain in Detail. **07**

 - Q.3** (a) For the Inverter Given in figure1 Calculate V_{OH} , V_{OL} , V_{IL} and NM_L . **07**



- (b) Draw the Stick Diagrams For Following Logic Function. **07**
 I. $F = A'B + AB'$
 II. $F = (AB)'$
 III. $F = (A+B)'$

OR

- Q.3** (a) Explain the Delay Time T_{PHL} and T_{PLH} for CMOS Inverter. **07**
 (b) What is Scaling? Explain the Small Geometry Effects. **07**

- Q.4** (a) Draw and explain the CMOS Inverter with all paratactic capacitance and derive the equation of C_{Load} . **07**
 (b) Describe the Two Input NOR Gate with CMOS Inverter with Necessary Equations. **07**

OR

- Q.4** (a) Implement the Following Boolean Function by Using Transmission Gate. **07**
 I. $F = AS' + BS$
 II. $F = AB' + A'B$
 III. $F = AB + A'C' + AB'C$

- Q.4** (b) Describe the BiCMOS Inverter. **07**

- Q.5** **(a)** Draw and Explain the Depletion-Load NMOS SR Latch Circuit Based on NOR2 Gate. **07**
- (b)** Implement the D-Latch by Using CMOS and Explain in Detail **07**
- OR**
- Q.5** **(a)** Describe the Dynamic CMOS Logic. **07**
- (b)** Draw and Explain the AOI Based Clocked NOR Gate Based SR Latch Circuit. **07**
