

GUJARAT TECHNOLOGICAL UNIVERSITY**M. E. - SEMESTER – III • EXAMINATION – WINTER 2012****Subject code: 734501****Date: 30/12/2012****Subject Name: Application of Power Electronics to Power System****Time: 10.30 am – 01.00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) List the FACTS devices. Give a classification of series, shunt and Hybrid FACTS devices. Mention the advantages of FACTS devices over conventional compensating methods. **07**
- (b) Explain significance of reactive power control. Also Compare Series and Shunt Capacitor compensators. **07**
- Q.2** (a) With suitable diagram describe the Thyristor Controlled Reactor (TCR) also discuss its applications in the power system **07**
- (b) Explain the operating characteristic of TCR with voltage control and how under voltage problem can be resolved using FC - TCR. **OR** **07**
- (b) Explain V – I characteristic of TSC – TCR with and without voltage control **07**
- Q.3** (a) Compare P- δ curve as a parametric function of Series compensation provided by SSSC and Series capacitor **07**
- (b) Briefly describe the working of a Thyristor Controlled Transformer (TCT) **07**
- OR**
- Q.3** (a) Discuss Capability of SSSC to provide Real Power Compensation **07**
- (b) Explain the construction and working of a UPFC **07**
- Q.4** (a) Explain the "direct" output voltage control scheme based on internal voltage (magnitude and angle) control at a sustained dc capacitor voltage for implementation of STATCOM. Draw relevant schematic block diagram and waveforms. **07**
- (b) Show that for the operating load angle $\delta = 35^\circ$, the var rating of series compensator is around 10% of that required of a shunt compensator for the same change in power transfer. **07**
- OR**
- Q.4** (a) Explain the application of STATCOM for damping of power oscillations in a power system. Discuss the control strategy used. **07**
- (b) Using relevant phasor diagram and equations, explain how a shunt connected switching converter type var generator can be used as a bidirectional active-reactive power compensator based on the principle of operation of STATCOM. **07**
- Q.5** (a) Explain the principle of operation of basic Thyristor-Controlled Series Capacitor (TCSC) scheme. **07**
- (b) State and explain any one application of TCSC in power system. **07**
- OR**
- Q.5** (a) Draw and explain reactance (X_{TCSC}) vs thyristor firing delay angle (α) characteristics of TCSC. **07**
- (b) Draw and explain compensating voltage vs line current characteristics of TCSC in voltage control mode and reactance control mode. **07**
