

GUJARAT TECHNOLOGICAL UNIVERSITY
M.E. – SEMESTER – IV EXAMINATION – OCTOBER 2012

Subject code: 742901**Date: 25-10-2012****Subject Name: Harmonics and Filtration Methods****Time: 2:30 pm – 5:00 pm****Total Marks: 70**

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1 (a) Describe and compare non linear and linear load with suitable examples of each. 07
(b) Define following terms: 1. Total Demand Distortion 2. Displacement, Distortion and Total power factor. 3. Telephone Influence Factor 07
- Q.2 (a) With neat schematic diagram, describe three phase three wire shunt active filter. 07
(b) Describe three phase three wire shunt active filter using sinusoidal current control method. 07
- OR**
- (b) Write a short note on active filter for Harmonic propagation. 07
- Q.3 (a) Describe digital controller with necessary sketch for active filter. 07
(b) Give a comparison of hybrid and pure active filter. 07
- OR**
- Q.3 (a) Describe the basic configuration of UPQC with necessary block diagram. 07
(b) Discuss harmonics distortion limit for voltage and current in conformance with IEC limits. 07
- Q.4 (a) Write a short note on UPFC. 07
(b) Explain how increase of Short Circuit Ratio helps to reduce harmonics in power system. 07
- OR**
- Q.4 (a) Discuss the types harmonics generated in six pulse converter also discuss the conditions which are responsible to generate the non-linear characteristic harmonics in power converter. 07
(b) Discuss how harmonics affect the performance of rotating machines. 07
- Q.5 (a) Explain working and design aspects of single tuned passive filter and discuss its quality factors. 07
(b) Explain how network reconfiguration helps to reduce harmonics in power systems. 07
- OR**
- Q.5 (a) Describe various conditions of harmonics which are responsible for neutral conductor overloading with suitable example. 07
(b) Describe basic configuration of shunt active filter with necessary block diagram. 07
