

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY

M. E. - SEMESTER – II • EXAMINATION – WINTER • 2014

Subject code: 1724205

Date: 05-12-2014

Subject Name: Analog and Mixed Signal VLSI Design

Time: 02:30 pm - 05:00 pm

Total Marks: 70

Instructions:

- 1. Attempt all questions.**
- 2. Make suitable assumptions wherever necessary.**
- 3. Figures to the right indicate full marks.**

- Q.1 (a)** Discuss the different issues related to Analog VLSI CMOS Technology. **07**
(b) Explain the working of basic PLL with necessary figures and waveforms. **07**

- Q.2 (a)** Calculate the voltage gain and -3dB frequency of Active nMOS load inverter by using small signal diagram. **07**
(b) Describe the Short Channel Effects with respect to MOS. **07**

OR

- (b)** Describe the Basic MOS Models **07**

- Q.3 (a)** Explain the various second order effect related to MOSFET. **07**
(b) What is miller effect? Explain in detail for analog VLSI circuit. **07**

OR

- Q.3 (a)** Describe the characterizing of comparator. **07**
(b) With suitable figures and equations explain the working of analog multiplier. **07**

- Q.4 (a)** Explain Following Terms for analog to digital converter. **07**
I. Missing Codes.
II. Offset and Gain Errors.
III. INL.
IV. DNL.

- (b)** Draw the Current Steering DAC and explain its working. **07**

OR

- Q.4 (a)** List down the various performance parameters of OPAMP? Discuss any three in detail. **07**

- (b)** Draw and explain the Differential amplifier with current source load **07**

- Q.5 (a)** Draw the Pipelined ADC and explain its working. **07**

- (b)** What is Noise? Explain the Noise Spectrum for analog VLSI circuit. **07**

OR

- Q.5 (a)** With suitable figures and equations explain the working of basic configuration of an OTA. **07**

- (b)** Describe the closed loop sample and hold circuit. **07**
