

GUJARAT TECHNOLOGICAL UNIVERSITYPDDC 2ND Semester Examination – July- 2011

Subject code: X21102

Subject Name: Digital Logic Design

Date: 15/07/2011

Time: 10:30 am – 01:00 pm

Total Marks: 70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) What is the function of shift register? With the help of simple diagram explain its working. With block diagram and timing diagram explain the serial transfer of information from register A to register B. **07**
- (b) Define : Integrated Circuit and briefly explain SSI, MSI, LSI and VLSI **07**

- Q.2** (a) Convert the following Numbers as directed: **07**
- (i) $(1101.011)_2 = ()_{10}$
- (ii) $(266)_{10} = ()_8$
- (iii) $(724.63)_{10} = ()_6$
- (iv) $(AB6.13)_{16} = ()_2$
- (b) Explain with figures how NAND gate and NOR gate can be used as Universal gate. **07**

OR

- (b) Explain SOP and POS expression using suitable examples. **07**

- Q.3** (a) Reduce the expression: **07**
- (i) $AB + A(B+C) + B(B+C)$
- (ii) $AB + (AC)' + AB'C(AB + C)$
- (b) Design a 32:1 Multiplexer using four 8:1 Multiplexer and one 4:1 Multiplexer. **07**

OR

- Q.3** (a) Simplify the Boolean function: **07**
- (i) $F(w, x, y) = \sum m(0, 1, 5) + \sum d(4, 7)$
- (ii) $F(A, B, C, D) = \sum m(0, 1, 3, 7, 15) + \sum d(2, 11, 12)$
- (iii) $F(A, B, C, D) = \prod M(0, 2, 6, 8, 12) + \prod d(3, 4, 7, 10, 14)$
- (b) What is a Johnson Counter? Explain the working of 4-bit Johnson Counter. **07**

- Q.4** (a) Design a combinational circuit that converts 4-bit Gray code to 4-bit Binary number using EX-OR gates. **07**
- (b) Draw the J-K master-slave flip-flops and explain how to eliminate the race around condition? **07**

OR


- Q.4** (a) Explain the design of Arithmetic Logic Unit **07**
- (b) With simple diagram explain the working of control logic with sequence register and decoder. **07**

- Q.5** (a) (i) Demonstrate the De Morgan's theorems using truth tables. **04**
- (ii) Implement a two-input exclusive-OR gate using minimum number of NOR gates. **03**

- (b) Give classification of Logic Families and Compare CMOS and TTL Families. 07

OR

 - Q.5 (a) Design the clocked sequential circuit for the given state diagram shown in figure below. 07



- (b) Briefly explain Look-ahead Carry Adder. 07
