

GUJARAT TECHNOLOGICAL UNIVERSITY**Subject code: X21102****Subject Name: Digital Logic Design****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) (i) $(2AC5.D)_{16} = (\quad)_{10} = (\quad)_8 = (\quad)_2$ **03**
 (ii) $(432)_5 = (\quad)_7$ $(8620)_{10} = (\quad)_{BCD}$ **03**
 (iii) Determine the value of b if $(33)_{10} = (201)_b$ **01**
- (b) (i) Add and multiply following numbers in the given base without converting to decimal: $(1230)_4$ and $(23)_4$ **03**
 (ii) Using 2's complement perform $(11010)_2 - (10000)_2$ **02**
 (iii) Obtain 9's and 10's complement of $(13579)_{10}$ **02**
- Q.2** (a) (i) Demonstrate the validity of De Morgan's theorems by means of truth tables for three variables. **03**
 (ii) What is duality principle? Show that the dual of the Exclusive-OR is equal to its complement. **02**
 (iii) Define the parameters power dissipation, propagation delay, noise margin and fan-out for IC digital logic families. **02**
- (b) (i) Find the complement of the following Boolean function and reduce it to a minimum number of literals: $F(A,B,C,D) = (BC' + A'D)(AB' + CD')$ **03**
 (ii) What is difference between canonical form and standard form? **04**
 Simplify the following Boolean function using Karnaugh map:
 $F(A, B, C, D) = ABD + A'C'D' + A'B + A'CD' + AB'D'$
- OR**
- (b) What do you mean by the gray code? Simplify Boolean function $F(A, B, C, D) = \sum m(0, 2, 3, 6, 7, 8, 10, 12, 13)$ using tabulation method. **07**
- Q.3** (a) Design a combinational circuit whose input is a four bit number and whose output is 2's complement of the input number. **07**
- (b) (i) Obtain all basic operations using only NAND gates. Also Implement Exclusive-OR gate using only four NAND gates. **07**
 (ii) Construct Boolean function $F = A(B + CD) + BC'$ using only NOR gates.
- OR**
- Q.3** (a) Explain Full adder in brief. Design a 4-bit BCD adder using two 4-bit binary adders. **07**
- (b) (i) Explain 4-bit magnitude comparator. **05**
 (ii) Construct 4×16 decoder using 3×8 decoders. Use block diagram construction. **02**

- Q.4 (a)** Draw the schematic diagram of encoder and explain the working of Multiplexer in brief. Implement given function $F(A,B,C,D) = \sum m(0,1,3,4,7,10,12,14)$ using 8:1 Multiplexer. **07**
- (b)** Differentiate edge and level triggering of flip-flops. What is race around condition in flip flops? How can we remove it? **07**
- OR**
- Q.4 (a)** Define the terms State & State table with respect to sequential circuit. Design a counter with the following binary sequence: 0,1,3,7,6,4 & repeat. Use T flip-flops. **07**
- (b)** (i) What is universal shift register? Explain Shift Registers in brief. **05**
(ii) Differentiate Combinational logic and sequential logic circuits. **02**
- Q.5 (a)** Differentiate ripple counters and synchronous counters. Design a 4-bit binary ripple counter. **07**
- (b)** Classify the types of microoperations most often encountered in digital systems and explain interregister-transfer microoperations in brief. **07**
- OR**
- Q.5 (a)** (i) Explain Status Register. **05**
(ii) Give differences between fixed-point data and floating point data. **02**
- (b)** What is the difference between hard-wired control and microprogram control? What are the advantages and disadvantages in each method? **07**
