

GUJARAT TECHNOLOGICAL UNIVERSITY**PDDC - SEMESTER-III • EXAMINATION – WINTER • 2014****Subject Code: X31101****Date: 24-12-2014****Subject Name: Advance Electronics****Time: 10:30 am - 01:30 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Draw and explain the circuit for dual input balanced output differential amplifier circuit. 07
Derive formula of differential gain A_d in terms of h-parameters.
- (b) Explain the operation of a 4 bit R-2R type DAC and derive the expression for the output voltage. Find the output voltage and resolution if the digital input is 1101. Assume $V_R = 10$ V and $R = R_f = 10k\Omega$. 07
- Q.2** (a) Classify the amplifiers based on position of operating point and also explain the distortion in amplifiers. 07
- (b) Draw the small signal high-frequency CE model of a transistor. Derive the formula for Input conductance $g_{b'e}$ and the base spreading resistor $r_{bb'}$. 07
- OR**
- (b) Write short note on: Validity of Hybrid- π model. 07
- Q.3** (a) (a) Sketch the response of an amplifier to a low-frequency square wave. (b) Define rise time. How is the rise time related to the high 3-dB frequency f_H . (c) Define tilt. How is the tilt related to the low 3-dB frequency f_L . 07
- (b) What is the negative feedback system? List the general characteristics of the negative feedback amplifier and explain any two of them with necessary equation. 07
- OR**
- (a) Draw and explain RC coupled amplifier. Explain effect of emitter bypass capacitor on low frequency response of RC coupled amplifier. 07
- (b) List the steps required to carry out the analysis of a feedback amplifier. Find A_f for an emitter follower using the feedback method of analysis. 07
- Q.4** (a) Describe the operation of successive approximation ADC with neat sketch. 07
- (b) Describe the principle of crystal oscillator along with its equivalent circuit. 07
- OR**
- Q.4** (a) Explain working of dual slope ADC with neat sketch. List its advantages and disadvantage. 07
- (b) Explain Wien bridge oscillator with neat sketch. What determines the frequency of oscillation? 07
- Q.5** (a) Draw block diagram of an op-amp and briefly explain each block. List characteristics of an ideal op-amp. 07
- (b) Draw two input TTL NAND gate with totem-pole output. Explain its working. 07
- OR**
- Q.5** (a) Define slew rate and CMRR of an OP-AMP. Show the circuit and explain how to measure slew rate and CMRR of an OP-AMP. 07
- (b) Draw NOR gate circuit using RTL logic. Explain its operation and list disadvantages. 07
